

Analog Signal Processing**Thursday, February 20, 8:45-10pm****Exam I**

Full Name (First Last): (all capital letters)	
---	--


UIN:		netID:	
-------------	--	---------------	--

Course: (circle one) Section to return exam: (circle one)	ECE210	ECE211	
	10AM	11AM	1PM 2PM

<p>Clearly PRINT your name in CAPITAL LETTERS.</p> <p>This is a closed book and closed notes exam.</p> <p>Calculators are not allowed.</p> <p>To get full credit, please SHOW all your work and simplify your answers.</p> <p>Write your final answers in the spaces provided.</p> <p>All answers should INCLUDE UNITS whenever appropriate.</p> <p>The exam is printed double-sided.</p>	<p style="text-align: center;">DO NOT write in these spaces.</p> <p>Problem 1 (25 points):_____</p> <p>Problem 2 (20 points):_____</p> <p>Problem 3 (30 points):_____</p> <p>Problem 4 (25 points):_____</p> <p>Total: (100 points):_____</p>
--	--

1. (25 pts) The two parts of this problem are unrelated.

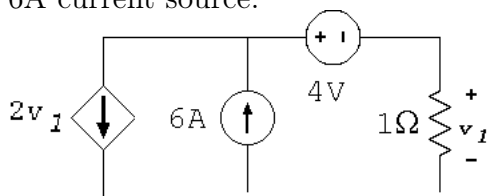- (a) [10 pts] For the circuit below, determine v_1 and the power absorbed or delivered by the 6A current source.




$$v_1 = \underline{\hspace{2cm}}$$

$$P_{6A} = \underline{\hspace{2cm}}$$

$\underline{\hspace{2cm}}$ absorbed $\underline{\hspace{2cm}}$ delivered

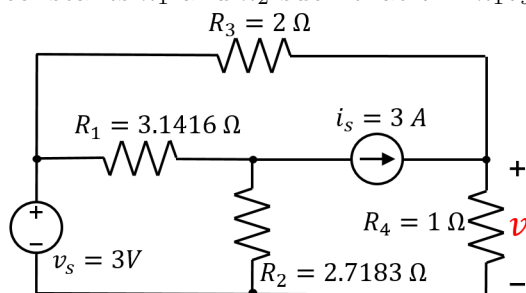
- (b) [15 pts] Consider the circuit below. Use the superposition method to determine the constants k_1 and k_2 such that $v = k_1 v_s + k_2 i_s$.



$$k_1 = \underline{\hspace{2cm}}$$

$$k_2 = \underline{\hspace{2cm}}$$

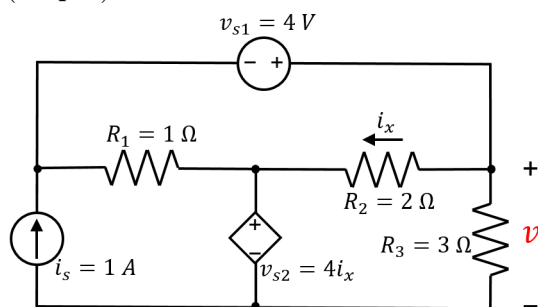
2. (20 pts) Consider the circuit below. Use the node-voltage method to determine v .



$v =$ _____

3. (30 pts) The two parts of this problem are unrelated.

(a) [20] Consider the circuit below.

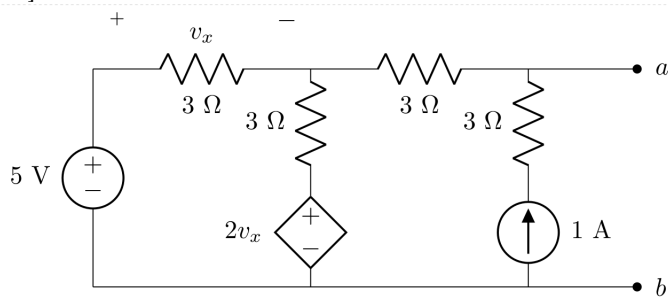


i. [10 pts] Determine the Thevenin equivalent voltage, V_T , between nodes a and b .

ii. [10 pts] Determine the Thevenin equivalent resistance, R_T , between nodes a and b . $V_T = \underline{\hspace{2cm}}$

$R_T = \underline{\hspace{2cm}}$

(b) [10 pts] Consider the circuit below.

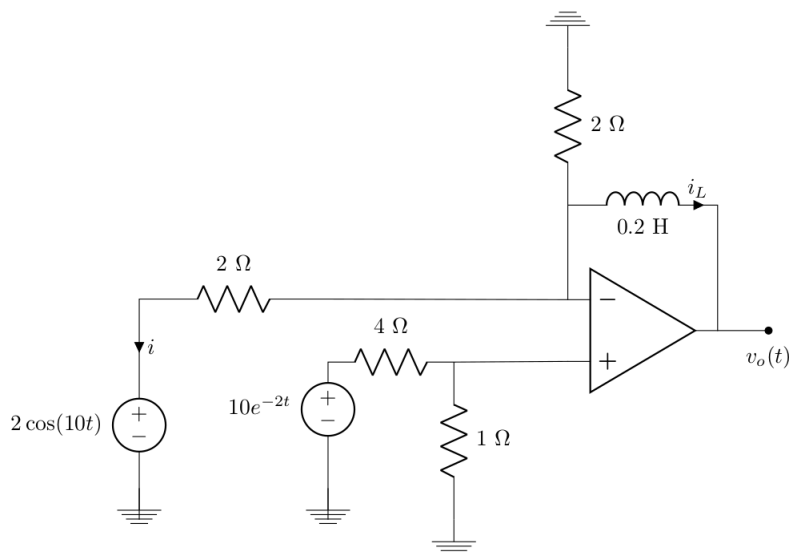


i. [07 pts] Determine the current through the inductor, i_L .

ii. [03 pts] Determine the output voltage, v_o .

$i_L =$ _____

$v_o =$ _____

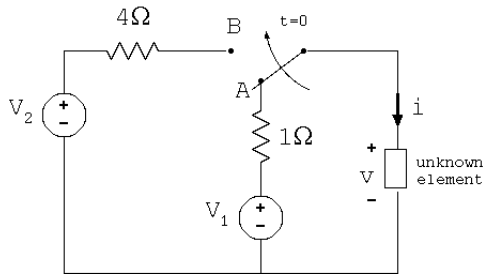4. (25 pts) Consider the circuit below. The switch is originally in position A it switches over to position B at time $t = 0$.



- (a) [03 pts] If it is known that that $v(0^-) = 5\text{V}$, $i(0^-) = 5\text{A}$, $v(0^+) = 4\text{V}$ and $i(0^+) = 4\text{A}$, is the unknown element a resistor, an inductor or a capacitor? Explain why.

_____ resistor _____ inductor _____ capacitor

Explain: _____

- (b) [06 pts] If the unknown element is an inductor, and it is known that $v(1) = -20e^{-2}\text{V}$, determine the value of the inductance, L .

$L =$ _____

- (c) [16 pts] Assume the unknown element is a 0.01F capacitor and that the switch was in position A for a long time. Determine the constants a , K_1 , K_2 and K_3 , such that $v(t) = K_1 + K_2e^{-at} + K_3t$, for $t > 0$. You may leave your answers in terms of V_1 and V_2 .

$K_1 =$ _____

$K_2 =$ _____

$K_3 =$ _____

$a =$ _____

You may use this sheet for additional calculations but **do not** separate this sheet from the rest of the exam.

You may use this sheet for additional calculations but **do not** separate this sheet from the rest of the exam.

You may use this sheet for additional calculations but **do not** separate this sheet from the rest of the exam.

You may use this sheet for additional calculations but **do not** separate this sheet from the rest of the exam.