

- Dissipative systems

- A *dissipative system* has a transient zero-input response

$$y_{zi}(t) \rightarrow 0 \quad t \rightarrow \infty$$

$\sin x = \cos(x - \pi/2)$
 $\rightarrow \cos \text{ or } \sin$


- In a dissipative system, the steady-state response to a cosinusoidal input applied at $t = -\infty$ will be a cosinusoidal independent of the initial state:

$$y(t) = Ae^{-at} + \underbrace{H\cos(\omega t + \psi)}_{y_{ss}(t)}$$

$\rightarrow 0 \text{ as } t \rightarrow \infty$

- n-th order LTI systems

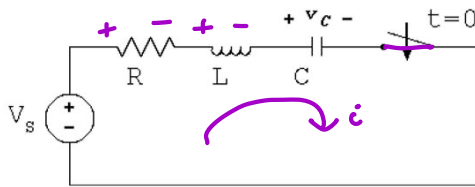- Determine the ODE governing the capacitor voltage in the following circuit:



Exo

$$i = C \frac{dv_c}{dt}$$

$$-V_s + V_R + v_L + v_c = 0$$

$$-V_s + i \cdot R + L \frac{di}{dt} + v_c = 0$$

$$-V_s + R \left(C \frac{dv_c}{dt} \right) + L \frac{d}{dt} \left(C \frac{dv_c}{dt} \right) + v_c = 0 \quad / : LC$$

$$\boxed{\frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = \frac{V_s}{LC}}$$

2nd order ODE with constant.
coeff.

- n-th order LTI systems-cont

- In general

$$\frac{d^n y}{dt^n} + a_1 \frac{d^{n-1} y}{dt^{n-1}} + \dots + a_n y = f(t)$$

where n - number of ^{energy} storage elements (L, C)


- Solution is

$$y(t) = y_p(t) + y_h(t)$$

if $p_1 = p_2$

$$A_1 e^{-p_1 t} + t A_2 e^{-p_2 t} + \dots$$

$$+ A_n e^{-p_n t} = y_h(t)$$

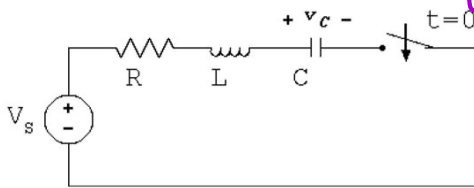


$$\cancel{y_h(t) = A e^{-at}}$$

same as in 1st order ODE
(same shape as input)
going to change

• Example #23:

- For $t > 0$, obtain $v_c(t)$ in the following circuit if $v_s = 0V$, $R = 0\Omega$, $i_L(0^-) = 0A$, $v_c(0^-) = 1V$, $L = 1H$ and $C = 1F$:

" $i_c(0^+) = i_c(0^-)$
series circuit"

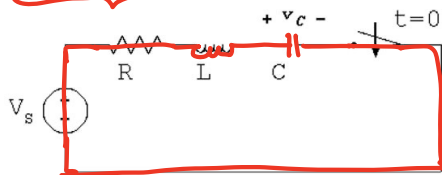

- Recall

Solution:

$\frac{d^2 v_c}{dt^2} + v_c = 0$
homogeneous ODE
 $y_h(t) = e^{st}$

$$s^2 e^{st} + e^{st} = 0$$

$$s^2 + 1 = 0$$

$$s = \pm \sqrt{-1} = \pm j$$

$$y_h = A_1 e^{-jt} + A_2 e^{jt}$$

$$\frac{V_s}{LC} = \frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{v_c}{LC} = 1$$

$$0 = \frac{d^2 v_c}{dt^2} + v_c \Rightarrow v_c(t) = \frac{1}{2} e^{jt} + \frac{1}{2} e^{-jt} =$$

$= \cos(t) \rightarrow$ zero-input response
is not transient \Rightarrow system is non-dissipative

$$i_c(t) = C \frac{dv_c}{dt} = -\sin(t)$$

Find A_1 and A_2 :

$$v_c(0^-) = v_c(0^+) = 1$$

$$1 = A_1 + A_2 \quad (1)$$

$$i_c(0^+) = 0$$

$$i_c(t) = C \frac{dv_c}{dt} = -jA_1 e^{-jt} + jA_2 e^{jt}$$

$$i_c(0^+) = -jA_1 + jA_2 = 0 \quad (2)$$

$$\text{Solving (1) and (2)} \Rightarrow A_1 = A_2 = \frac{1}{2} \Rightarrow v_c(t) = \frac{1}{2} e^{jt} + \frac{1}{2} e^{-jt}$$

$$\cos \varphi = \frac{e^{j\varphi} + e^{-j\varphi}}{2}$$

Chapter objectives

- Apply ideal op-amp approximation to do signal processing
- Understand zero-input and zero-state responses
- Understand what is linearity and how to test if a system is linear
- Understand what is time-invariance and how to test if system is TI
- Analyze first order RC and RL circuits with constant inputs:
 - How to obtain particular and homogeneous solutions
 - How to obtain zero-state and zero-input solutions
 - How to obtain transient and steady-state solutions
 - Understand the effect of the time-constant in the solution
- Analyze first order RC, RL circuits with time-varying inputs
 - How to obtain particular and homogeneous solutions
 - How to obtain zero-state and zero-input solutions
 - How to obtain transient and steady-state solutions
- Be familiar with n -th order LTI systems