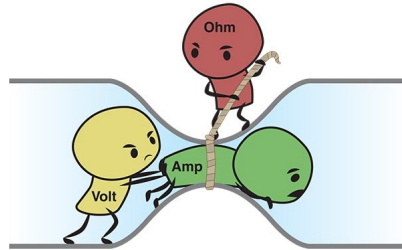


ECE 210 (AL2) - ECE 211 (E)

## Chapter 1

### Circuit Fundamentals




Olga Mironenko  
University of Illinois  
Spring 2022
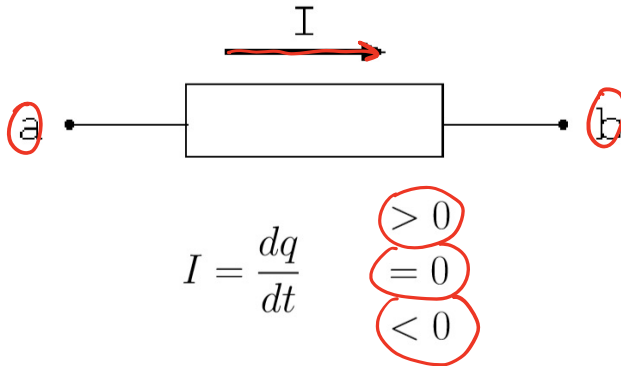
# Outline


- Current and voltage
- Series and parallel configurations, SRS
- Kirchhoff's voltage and current laws (KVL and KCL)
- Ideal Resistors, Ohm's law
- Independent and dependent sources
- Absorbed power
- Ideal Capacitors and inductors
- Obtain voltages, currents and absorbed power in basic circuits using KVL, KCL and Ohm's law

- **Current:** amount of net electrical charge per unit time passing in the direction of arrow.



- **Units:** Amperes (A) =  $\frac{\text{Coulomb (C)}}{\text{second (s)}}$

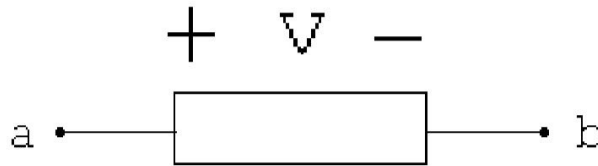- **Voltage:** energy gain per Coulomb moved from "-" terminal to "+" terminal, or energy loss per Coulomb moved from "+" terminal to "-" terminal.




$$V = \frac{dW}{dq}$$

$$\begin{aligned} & > 0 \\ & = 0 \\ & < 0 \end{aligned}$$

- energy gain from "-" to "+"  
- energy loss from "-" to "+"

- **Units:** Volts (V) =  $\frac{\text{Joule (J)}}{\text{Coulomb (C)}}$

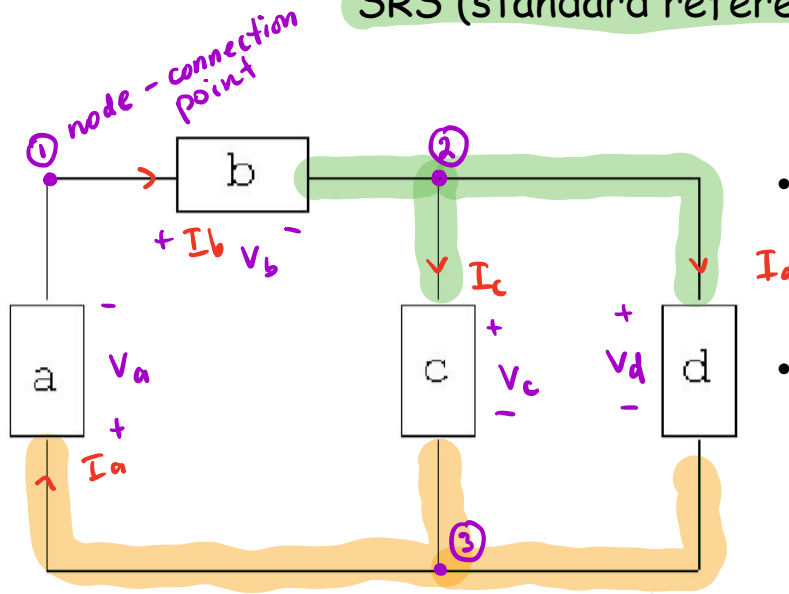- Example #1: assignment of polarities and current directions, SRS (standard reference system)




### • Series vs Parallel:

- Series : same current  
( $I_a = I_b$ )

- Parallel : connected to the same two nodes  $\Rightarrow$  same voltage, e.g.  
 $V_c = V_d$

SRS: current goes into "+" terminal

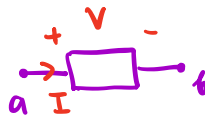

- **Node voltage:** energy gain per Coulomb moved from a reference node to a specific node.

