
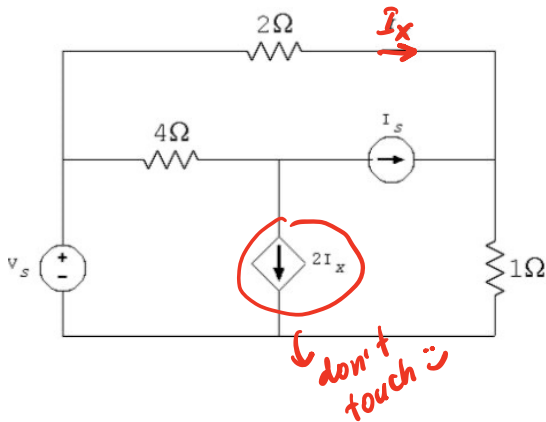


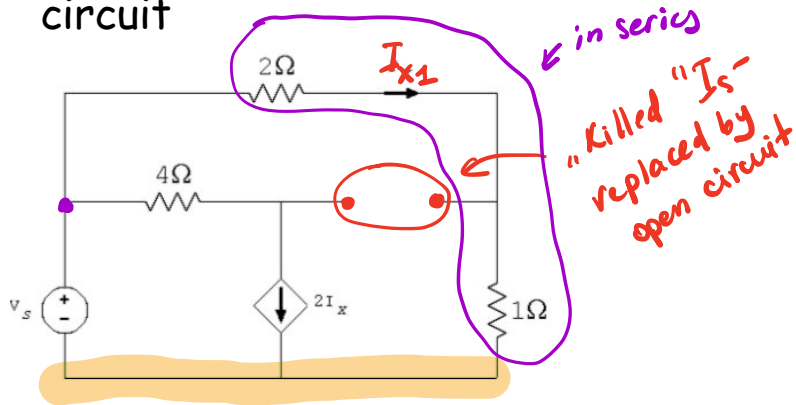- **Example #8-cont:** Use superposition to determine I_x in this circuit



- 1) Keep V_s
- 2) Keep I_s

- **Example #8-cont:** Use superposition to determine I_{x_1} in this circuit



$I_{x_1} - ?$

a) 0

b) V_s


c) $\frac{1}{3} V_s$

d) $\frac{2}{3} V_s$

V_s is in parallel with series of 2Ω and $1\Omega \Rightarrow$

$$I_{x_1} = \frac{V_s}{2+1} = \frac{1}{3} V_s \Rightarrow \text{contribution to } I_x \text{ from } V_s.$$

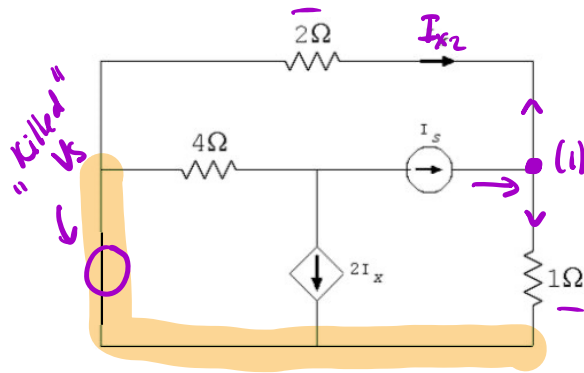- **Example #8-cont:** Use superposition to determine I_x in this circuit



"killed" $V_s \rightarrow$ replace by short-circuit
 2Ω and 1Ω are in parallel \Rightarrow
 can do current division,

$$-I_{x2} = I_s \left(\frac{1}{1+2} \right) \Rightarrow$$


need to take $-I_{x2}$, since I_{x2} is
 coming into the node (1)

$$I_{x2} = -\frac{1}{3} I_s \text{ -contribution from } I_s$$

$$\Rightarrow I_x = I_{x1} + I_{x2} = \frac{1}{3} V_s - \frac{1}{3} I_s$$

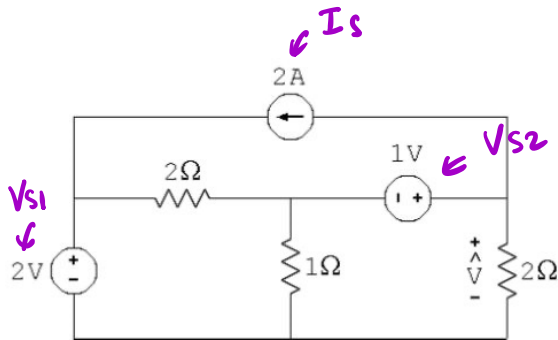
- **Example #9:** Use superposition to determine \hat{V} in this circuit

$$\hat{V} = k_1 V_{s1} + k_2 I_s + k_3 V_{s2}$$




- **Example #9-cont:** Use superposition to determine \hat{V}_1 in this circuit

keep only 2V source:

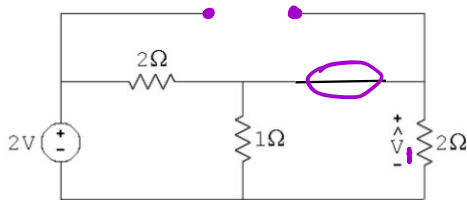

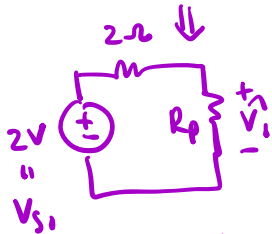in parallel $\Rightarrow R_p = \frac{1 \cdot 2}{1+2} = \frac{2}{3} \Omega$




↓ Voltage division: $\hat{V}_1 = V_{s1} \left(\frac{\frac{2/3}{2/3 + 2}} \right) = \underbrace{\frac{1}{4}}_{k_1} \cdot V_{s1} = \frac{1}{2} V$

Contribution from 2V source
↓

- Example #9-cont: Use superposition to determine \hat{V}_2 in this circuit

Keep only 2A source :

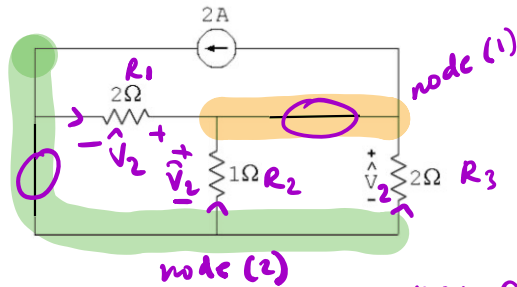

$$\text{KCL @ (2): } 2 = I_{R1} + I_{R2} + I_{R3}$$

$$-\frac{\hat{V}_3}{R_1} - \frac{\hat{V}_2}{R_2} - \frac{\hat{V}_2}{R_3} = 2$$

$$\hat{V}_2 = -1V$$

∴ contribution
from 2A source