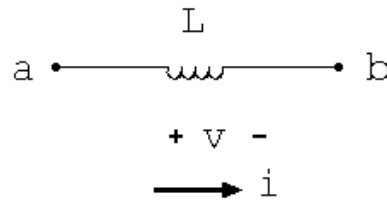


Lecture 11, Monday, February 7, 2022

- Differentiators and integrators

– *Inductor:*




$$* v(t) = L \frac{di}{dt} \rightarrow i(t) = \frac{1}{L} \int_{-\infty}^t v(s) ds$$

* current in inductor is continuous for practical sources

$$\rightarrow i(t) = i(t^-) = i(t^+)$$

– *Capacitor:*

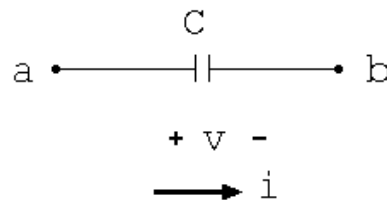

$$* i(t) = C \frac{dv}{dt} \rightarrow v(t) = \frac{1}{C} \int_{-\infty}^t i(s) ds$$

* voltage in capacitor is continuous for practical sources

$$\rightarrow v(t) = v(t^-) = v(t^+)$$

- *Zero-state* linearity: in a zero-state linear system, a weighted sum of inputs produces a similarly weighted sum of corresponding *zero-state* outputs, consistent with superposition:

$$\mathbf{f}_1(\mathbf{t}) \rightarrow \boxed{\text{zero-state linear}} \rightarrow \mathbf{y}_{\text{zs},1}(\mathbf{t}), \text{ and}$$

$$\mathbf{f}_2(\mathbf{t}) \rightarrow \boxed{\text{zero-state linear}} \rightarrow \mathbf{y}_{\text{zs},2}(\mathbf{t}), \text{ then}$$

$$\mathbf{f}_3(\mathbf{t}) = \mathbf{k}_1 \mathbf{f}_1(\mathbf{t}) + \mathbf{k}_2 \mathbf{f}_2(\mathbf{t}) \rightarrow \boxed{\text{zero-state linear}} \rightarrow \mathbf{y}_{\text{zs},3}(\mathbf{t}) = \mathbf{k}_1 \mathbf{y}_{\text{zs},1}(\mathbf{t}) + \mathbf{k}_2 \mathbf{y}_{\text{zs},2}(\mathbf{t})$$

continued on next page....

Lecture 11, continued from previous page...

- Basically a linear combination of inputs gives the same linear combination of their individual outputs
- Sometimes you can determine by inspection: if you plot y as a function of f , is it a line through the origin?
- *Zero-input linearity* : in a zero-input linear system, a weighted sum of initial states produces a similarly weighted sum of corresponding *zero-input* outputs, consistent with the superposition principle.
- *Linearity*: a system is linear if it is zero-state linear, zero-input linear and the output is the sum of the zero-state response (output if you force the initial state to be zero) and the zero-input response (output if you force the input to be zero).

$$\mathbf{y}(\mathbf{t}) = \mathbf{y}_{\text{zs}}(\mathbf{t}) + \mathbf{y}_{\text{ZI}}(\mathbf{t})$$