
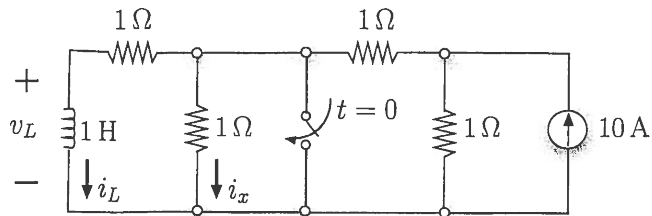


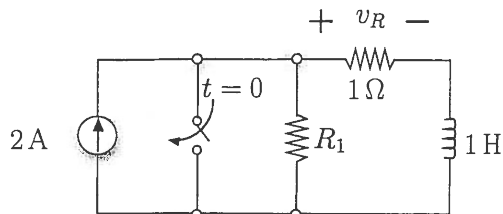
2. Assume the switch has been open for a long time and it closes at time $t = 0$ s. Find and sketch $i_L(t)$, $v_L(t)$, and $i_x(t)$.




3. Assume the switch has been open for a long time and it closes at time $t = 0$ s. Find the value of R_1 such that $v_R(1\text{ s}) = \frac{1}{2}e^{-1}$ V.



4. Assume the switch has been in the A position for a long time, it moves to the B position at time $t = 0$ s, and it moves back to the A position at time $t = 3$ s. Find the values of R_1 and R_2 such that $v(1\text{ s}) = 1 - e^{-1/3}$ V and $v(4\text{ s}) = (1 - e^{-1})e^{-1/4}$ V.

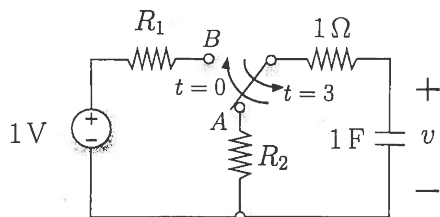

Problem 5

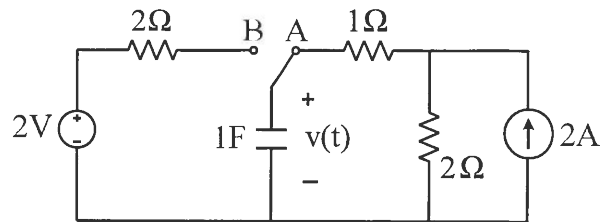

Assume the switch has been in position A for a long time. It moves to position B at $t = 0$.

a) (5 points) Write the 1st order ODE of $v(t)$ for $t > 0$.

b) (3 points) Find the initial value of $v(t)$ at $t = 0^-$.

$$v(0^-) = \underline{\hspace{2cm}}$$

c) (8 points) Solve $v(t)$ for $t > 0$.

$$v(t) = \underline{\hspace{2cm}}$$

d) (3 points) What is the zero input component of $v(t)$?

$$V_{z-i}(t) = \underline{\hspace{2cm}}$$

Problem 5 (cont.)

e) (3 points) What is the zero state component of $v(t)$?

$$V_{z-s}(t) = \underline{\hspace{10cm}}$$