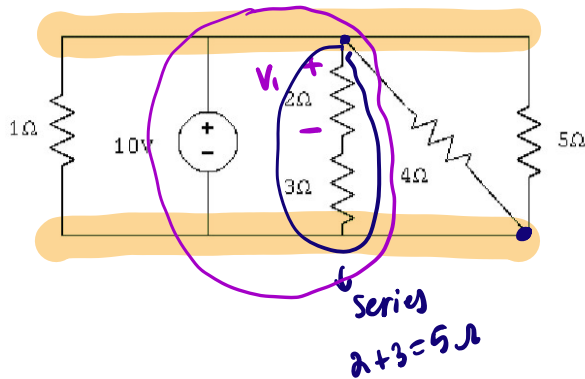


### • Example #1:

- Simplify the following circuit into a voltage source in parallel with a single resistor,  $R_{eq}$ . What is the value of  $R_{eq}$ ?
- Determine the voltage at the  $2\Omega$  resistor.



Voltage division:

$$V_1 = V \frac{2}{2+3} = 4V$$

$R_{eq} - ?$

a)  $\frac{45}{59} \Omega$

b)  $\frac{33}{13} \Omega$

c)  $\frac{10}{7} \Omega$





**d)  $\frac{20}{33} \Omega$**

e) None


$$\frac{1}{R_{eq}} = 1 + \frac{1}{5} + \frac{1}{4} + \frac{1}{5} =$$

$$= \frac{33}{20} \Rightarrow R_{eq} = \frac{20}{33} \Omega$$

- Source combinations

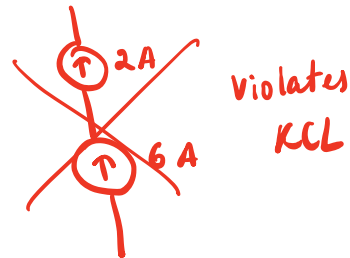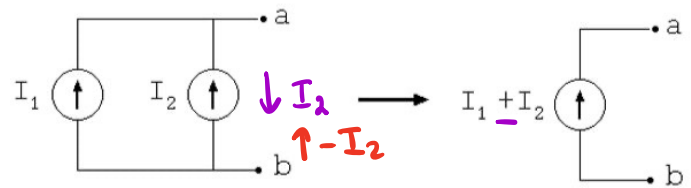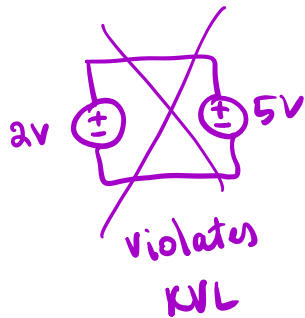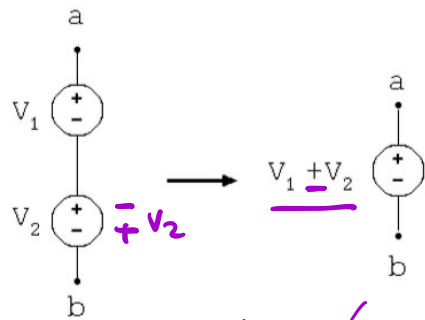

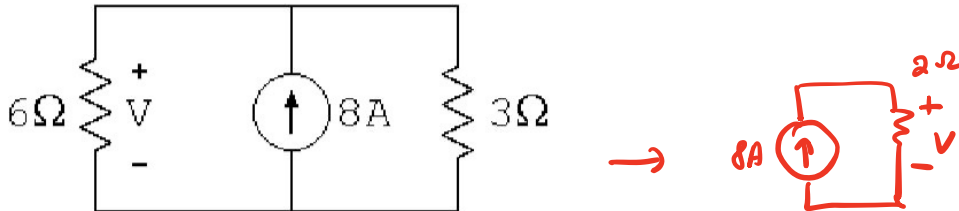
- **Example #2:** Determine the voltage  $V$  in the following circuit



- Approach 1:

- $R_p = \frac{6 \cdot 3}{6 + 3} = \frac{18}{9} = 2\Omega$
- $V = R \cdot I = 2 \cdot 8 = 16V$

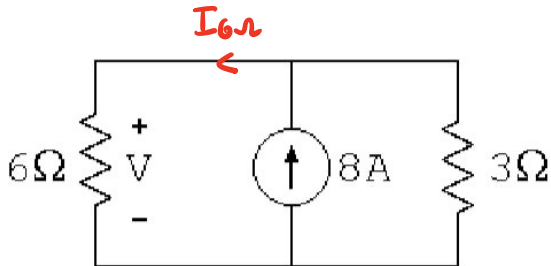
- Example #2-cont: Determine the voltage  $V$  in the following circuit



- Approach 2: current division

- $I_{6\Omega} = I \left( \frac{3}{3+6} \right) = 8 \left( \frac{3}{9} \right) = \frac{8}{3} \text{ A}$
- $V = I_{6\Omega} \cdot R = \frac{8}{3} \cdot 6 = 16 \text{ V}$


- Source transformations

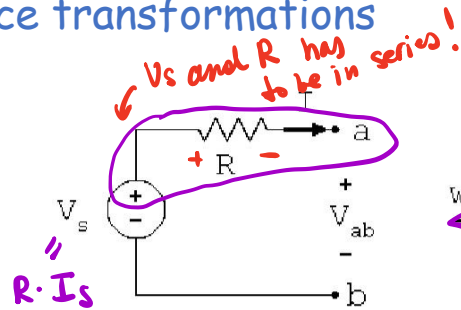

KVL:  $-V_s + I \cdot R + V_{ab} = 0$

$V_s = V_{ab} + I \cdot R$

want

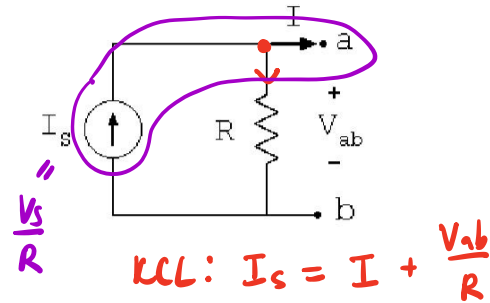

KCL:  $I_s = I + \frac{V_{ab}}{R}$

$R I_s = I \cdot R + V_{ab}$




$V_s = R \cdot I_s$


or

$I_s = \frac{V_s}{R}$

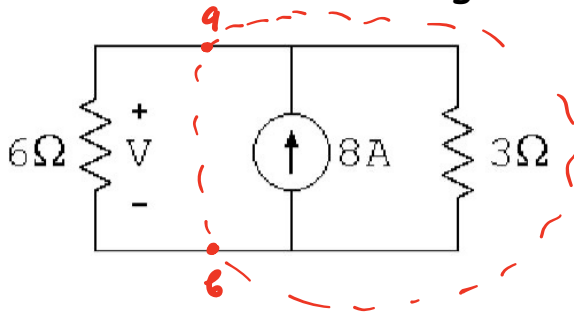- **Example #2-cont:** Determine the voltage  $V$  in the following circuit using source transformations



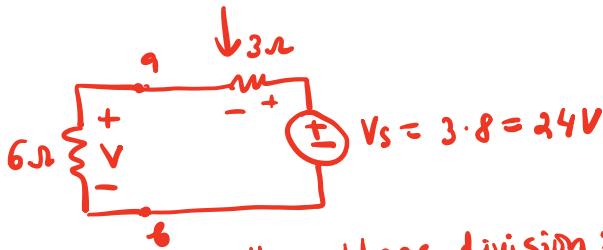
*Note: don't transform parts of the circuit you are interested in !*



$\Downarrow$  voltage division:

$$V = 24 \left( \frac{6}{6+3} \right) = 16V$$

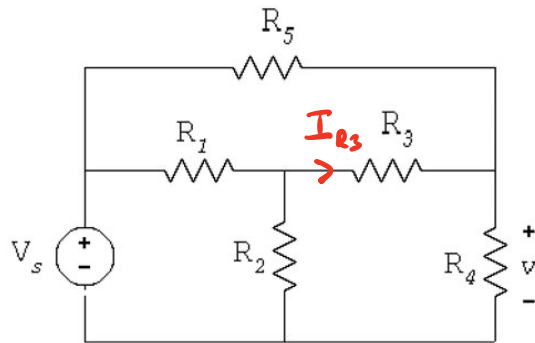- **Example #4:** Determine  $V_{R4}$  and  $I_{R3}$  in the following circuit




HOW?



- Node-voltage method

- Step #1:

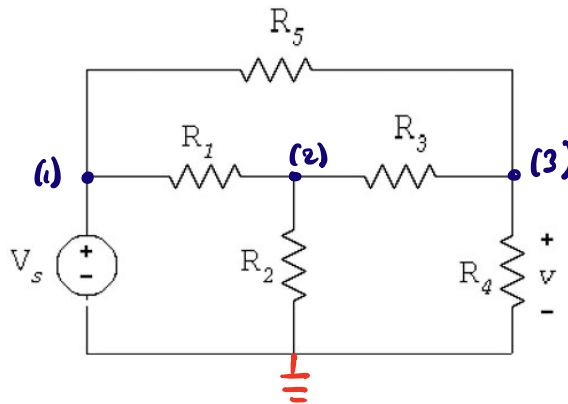Identify all nodes and label their node voltages  $V_1, V_2, \dots, V_n$  plus a reference.






- Node-voltage method

- Step #2:

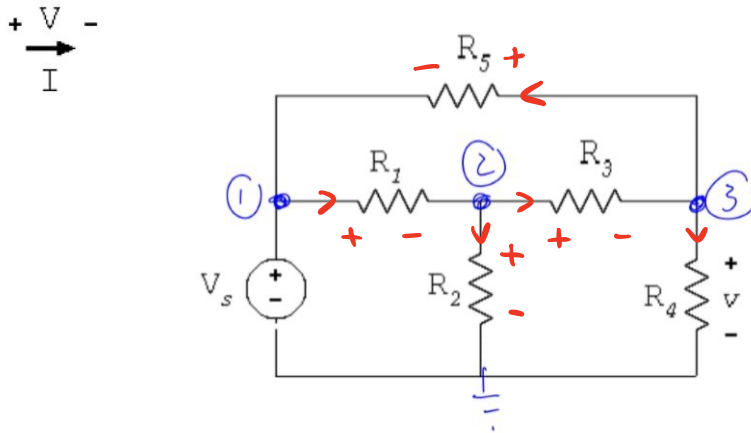Assign current directions and polarities to all elements (use SRS for simplicity).




- Node-voltage method


- Step #3:

*simple*

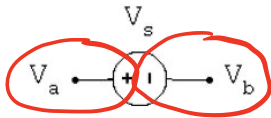Use voltage sources to obtain equations between their node voltages



$$V_s = V_a - V_b$$

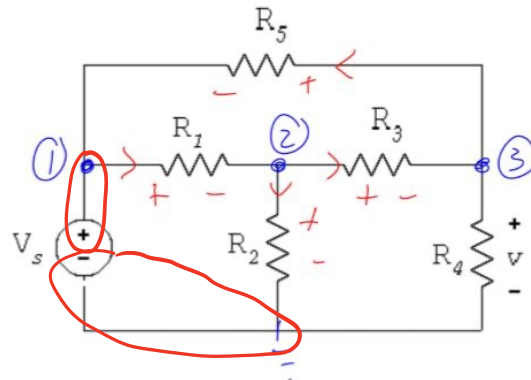



$$V_s = V_1 - 0 \quad (1)$$

- Node-voltage method

- Step #4:

Use KCL on remaining nodes to get a total of  $n$  equations in terms of the node voltages.

→ total number of nodes - reference .

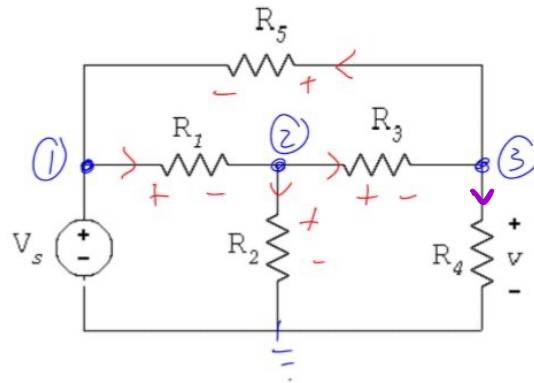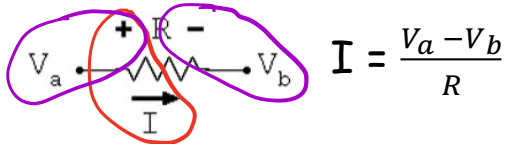

$$V_s = V_1 \quad (1)$$

$$\text{KCL @ (2)} : \frac{V_1 - V_2}{R_1} =$$


$$= \frac{V_2 - 0}{R_2} + \frac{V_2 - V_3}{R_3} \quad (2)$$

$$\text{KCL @ (3)} : \frac{V_2 - V_3}{R_3} = \frac{V_3 - 0}{R_4} +$$

$$+ \frac{V_3 - V_1}{R_5} \quad (3)$$

- Node-voltage method

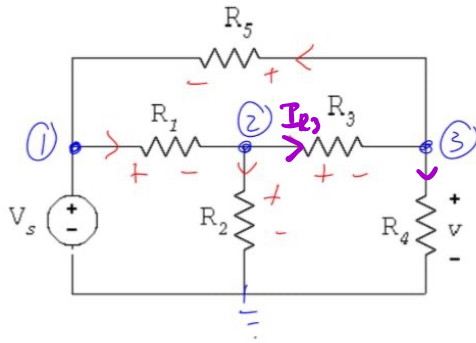- Step #5:  $V_{R4}$  and  $I_{R3}$  - ?  
Solve equations



$$V = V_3 - 0 = \frac{1}{2} V$$

$$I_{R3} = \frac{V_2 - V_3}{R_3} = 0 A$$

$$1 = 3V_2 - V_3 \Rightarrow V_3 = 3V_2 - 1$$

$$1 = -V_2 + 3V_3$$

$$V_2 = \frac{1}{2} V$$

$$V_3 = \frac{1}{2} V$$

Assume :  $R_i = 2 \Omega$  for all  $i$   
 $V_s = 1 V$

$$1 = V_1 \quad (1)$$

$$\frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3}$$

$\Downarrow$

$$0 = -\frac{1}{2} V_1 + \frac{3}{2} V_2 - \frac{1}{2} V_3 \quad (2) \quad (\times 2)$$


$$\frac{V_2 - V_3}{R_3} = \frac{V_3}{R_4} + \frac{V_3 - V_1}{R_5}$$

$\Downarrow$


$$0 = -\frac{1}{2} V_1 - \frac{1}{2} V_2 + \frac{3}{2} V_3 \quad (3) \quad (\times 2)$$

## • Node-voltage method: summary

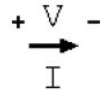
1. Identify all nodes and label their node voltages  $V_1, V_2, \dots, V_n$  plus a reference
2. Assign current directions and polarities to all elements (use SRS for simplicity)



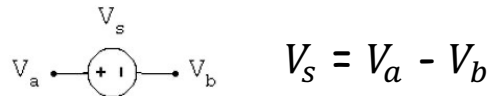3. Use voltage sources to obtain equations between their node voltage




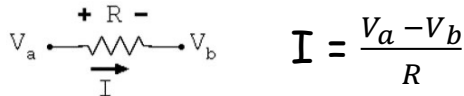4. Use KCL on remaining nodes to get a total of  $n$  equations in terms of the node voltages



5. Solve equations

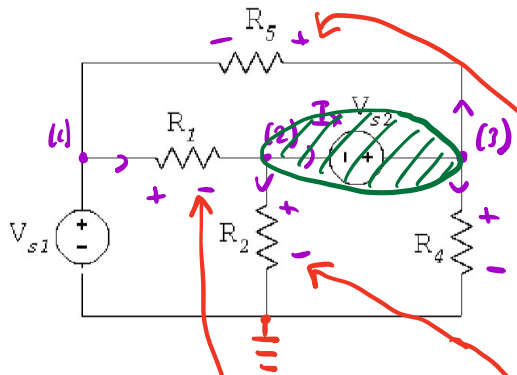- **Example #5:** Use the node-voltage method to determine all node voltages in this circuit



$$V_{s1} = V_1 - 0 \quad (1)$$

$$V_{s2} = V_3 - V_2 \quad (2)$$

$$\text{KCL @ (2): } \frac{V_1 - V_2}{R_1} = \frac{V_2 - 0}{R_2} + I_x \quad (3)$$

$$\text{KCL @ (3): } I_x = \frac{V_3 - 0}{R_4} + \frac{V_3 - V_1}{R_5} \quad (4)$$

$$\frac{V_1 - V_2}{R_1} = \frac{V_2 - 0}{R_2} + \frac{V_3 - 0}{R_4} + \frac{V_3 - V_1}{R_5}$$

Supernode (2-3): combine KCL @ (2) and (3).

Works only with voltage sources  
between 2 nodes.