

## Lecture 15, Friday, February 11, 2022

- For a general resistive circuit with just one capacitor:

$$v_c(t) = V_T + (v_c(0^-) - V_T) e^{-\frac{t}{R_T C}}$$

- A simple way to solve for  $v_c(t)$  for  $t > 0$  is to consider

- \*  $v_c(t) = B + A e^{-\frac{t}{\tau}}$

- \*  $v_c(\infty) = V_T = B$

- \*  $v_c(0^+) = v_c(0^-) = B + A$

- \*  $\tau = R_T C$

- \*  $V_T$  and  $R_T$  are the Thevenin equivalent from the capacitor's perspective.

- General first order ODE with constant coefficients and constant input:

- A simple way to separate the ZI and ZS responses is to not substitute the value of  $K$  nor  $y(0^+)$  while solving the equations.

- That way, the expression for  $y(t)$  will clearly show  $K$  and  $y(0^+)$

$$y(t) = \frac{K}{a} (1 - e^{-at}) + y(0^+) e^{-at}$$

- To get  $y_{ZI}(t)$  simply set  $K = 0$

- To get  $y_{ZS}(t)$  simply set  $y(0^+) = 0$

**continued on next page....**

## Lecture 15, continued from previous page...

- For a general resistive circuit with just one inductor:

$$i_L(t) = I_N + (i_L(0^-) - I_N) e^{-\frac{R_T}{L}t}$$

– A simple way to solve for  $i_L(t)$  for  $t > 0$  is to consider

$$* i_L(t) = B + Ae^{-\frac{t}{\tau}}$$

$$* i_L(\infty) = I_N = B$$

$$* i_L(0^+) = i_L(0^-) = B + A$$

$$* \tau = \frac{L}{R_T}$$

\*  $I_N$  and  $R_T$  are the Norton equivalent from the capacitor's perspective.