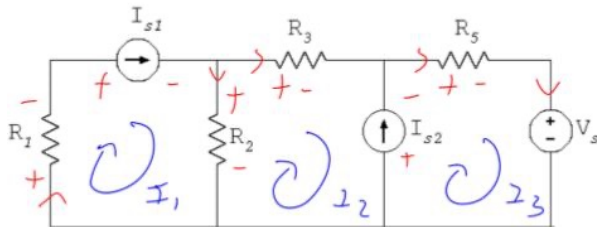


- **Example #6-cont:** Use the loop-current method to obtain all loop currents



Assume  $R_i = 2\Omega$  for all  $i$

$$V_s = 4V$$

$$I_{s1} = 2A$$

$$I_{s2} = 6A$$

$$2 = I_1 \quad (1)$$

$$6 = I_3 - I_2 \quad (2)$$


$$4 = 2I_1 - 4I_2 - 2I_3 \quad (3)$$

:

$$I_2 = -2A$$

$$I_3 = 4A$$

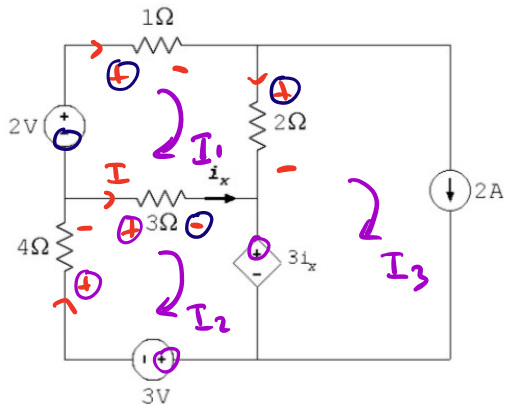- **Example #7:** Use the loop-current method to obtain all loop currents



From the current source:  $I_3 = 2 \text{ A}$

KVL on loop 2:

$$+4(I_2) + 3(I_2 - I_1) + 3i_x + 3 = 0$$

KVL on loop 1:

$$-2 + 1(I_1) + 2(I_1 - I_3) - 3(I_2 - I_1) = 0$$

$$i_x = I_2 - I_1$$

;


solving...

$$I_3 = 2 \text{ A}$$

$$I_2 = \frac{6}{14} \text{ A}$$

$$I_1 = \frac{17}{14} \text{ A}$$

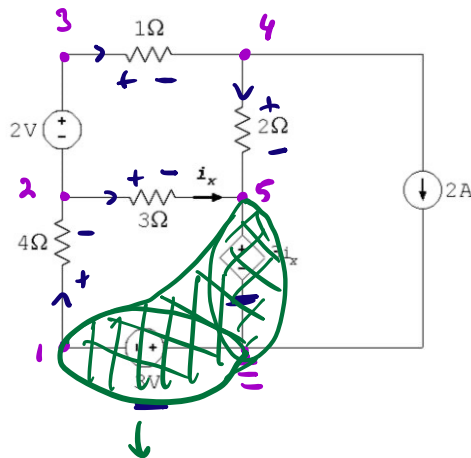- **Example #7-cont:** Use the node-voltage method to determine all node voltages in this circuit



$$2 = V_3 - V_2 \quad (1)$$

$$3 = 0 - V_1 \quad (2)$$

$$3i_x = V_5 - 0 \quad (3)$$

KCL @ (4):

$$\frac{V_3 - V_4}{1} = \frac{V_4 - V_5}{2} + 2 \quad (4)$$

$$i_x = \frac{V_2 - V_5}{3}$$

Supernode 5-0-1:

$$\frac{V_1 - V_2}{4} = \frac{V_2 - V_5}{3} + \frac{V_4 - V_5}{2} + 2$$


$$V_1 = -3V$$

$$V_2 = -\frac{33}{7}V$$


$$V_3 = -\frac{19}{7}V$$

$$V_5 = -\frac{33}{14}V$$

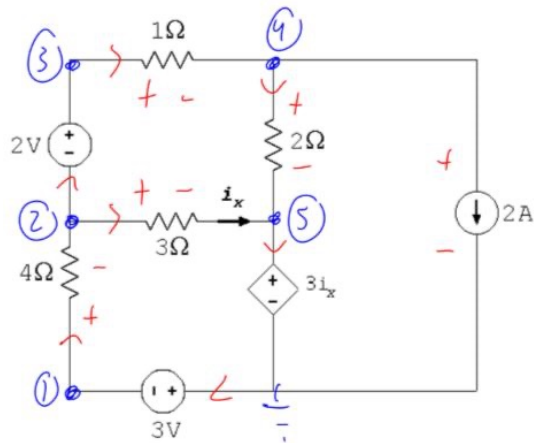- **Example #7-cont:** Use the node-voltage method to determine all node voltages in this circuit



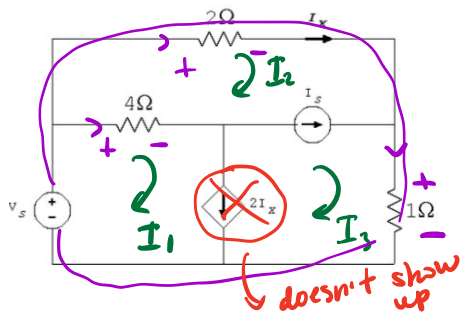- Superposition
- **Example #8:** Use the loop-current method to determine all loop currents in this circuit



Simplifying equations:

$$I_s = -I_2 + I_3$$

$$0 = I_1 - 2I_2 - I_3$$

$$V_s = 2I_2 + I_3$$

$$I_s = I_3 - I_2 \quad (1)$$

$$2I_x = I_1 - I_3 \quad (2)$$

KVL on outer loop:

$$-V_s + 2I_2 + 1 \cdot I_3 = 0 \quad (3)$$

$$I_x = I_2$$

Solution:

$$I_1 = V_s$$

$$I_2 = \frac{1}{3}V_s - \frac{1}{3}I_s$$

$$I_3 = \frac{1}{3}V_s + \frac{2}{3}I_s$$

} linear combination of independent sources

↓  
can look at effect of each source individually

## • Superposition principle

Let  $V_{s1}, V_{s2}, \dots, V_{sn}, I_{s1}, I_{s2}, \dots, I_{sm}$  be the complete set of independent sources in a resistive circuit.


Then, any electrical response  $y$  in the circuit (v or i) can be expressed as

$$y = k_1 V_{s1} + k_2 V_{s2} + \dots + k_n V_{sn} + \widehat{k}_1 I_{s1} + \widehat{k}_2 I_{s2} + \dots + \widehat{k}_m I_{sm},$$

where the constants  $k_1, \dots, k_n, \widehat{k}_1, \dots, \widehat{k}_m$  are unique to each response  $y$ .


- weighted linear superposition of independent sources
- can look at effect of each source individually without effect of the other sources by making other sources 0 (to leave one active source at a time)
- current source  $\rightarrow$  open circuit
- voltage source  $\rightarrow$  short circuit

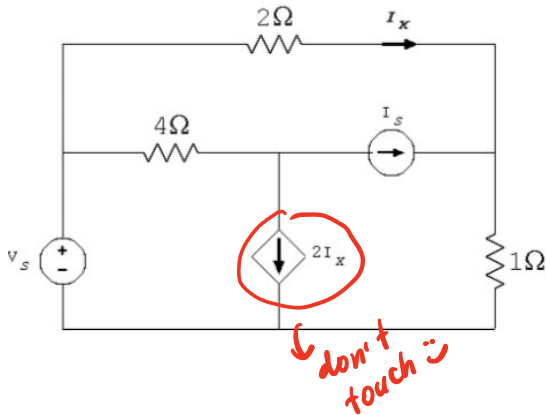- **Example #8-cont:** Use superposition to determine  $I_x$  in this circuit



- 1) Keep  $V_s$
- 2) Keep  $I_s$

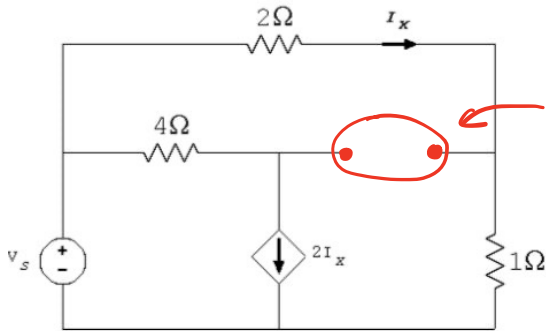- **Example #8-cont:** Use superposition to determine  $I_2$  in this circuit



*"Killed"  $I_s$  replaced by open circuit*