

Spring 2022

Lab 3: Frequency Response and Fourier Series

In this lab you will build an active bandpass filter circuit with two capacitors and an op-amp, and examine the response of the circuit to periodic inputs over a range of frequencies. The same circuit will be used in Lab 4 in your AM radio receiver system as an intermediate frequency (IF) filter, but in this lab our main focus will be on the frequency response $H(\omega)$ of the filter circuit and the Fourier series of its periodic input and output signals. In particular we want to examine and gain experience about the response of linear time-invariant circuits to periodic inputs.

1 Prelab

- Determine the compact-form Fourier series of the periodic square wave signal, $f(t)$ shown in Figure 1, with a period T and amplitude A . That is, find c_n and θ_n such that

$$f(t) = \frac{c_0}{2} + \sum_{n=1}^{\infty} c_n \cos(n\omega_o t + \theta_n), \text{ where } \omega_o = \frac{2\pi}{T}.$$

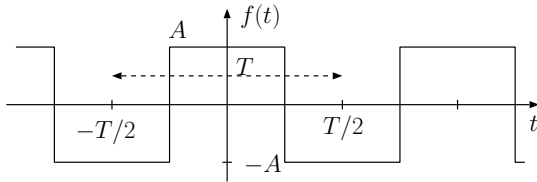
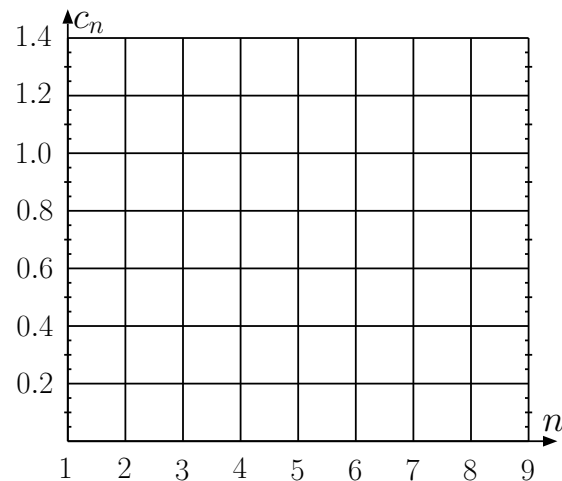


Figure 1: Square wave signal for prelab.

Notice $\frac{c_0}{2} = 0$. How could you have determined that without any calculation?

(____/2)

Show your work.(____/3)

 $F_n =$ _____ (____/2) $c_n =$ _____ (____/2) $\theta_n =$ _____ (____/2)With $A = 1$, plot c_n over n ($n \in [1, 9]$) (____/2)

(____/11)

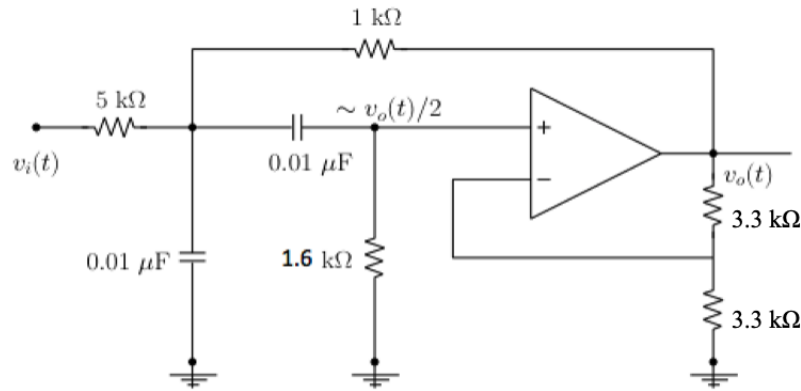


Figure 2: Circuit for analysis in prelab and lab.

2. Consider the circuit in Figure 2 where $v_i(t)$ is a co-sinusoidal input with some radian frequency ω .

- (a) What is the phasor gain $\frac{V_o}{V_i}$ in the circuit as $\omega \rightarrow 0$? (Hint: How does one model a capacitor at DC — open or short?)

Show your work

(____/3)

- (b) What is the gain $\frac{V_o}{V_i}$ as $\omega \rightarrow \infty$? (Hint: think of capacitor behavior in $\omega \rightarrow \infty$ limit)

Show your work

(____/3)

- (c) In view of the answers to part (a) and (b), and the fact that the circuit is 2nd order (it contains two energy storage elements), try to guess what kind of a filter the system frequency response $H(\omega) \equiv \frac{V_o}{V_i}$ implements — lowpass, highpass, or bandpass? The amplitude response $|H(\omega)|$ of the circuit will be measured in the lab.

Give your answer and explain your reasoning.

(____/2)

3. Decibels (dB) is a unit of measurement widely used in science and engineering to compare power or intensity quantities. A decibel (dB) is one-tenth of a Bel (B), which is the name given to $\log_{10} \left(\frac{P_1}{P_0} \right)$, where \log_{10} is the base 10 logarithm, and $\frac{P_1}{P_0}$ is the ratio of two power quantities. The formula for calculating decibels is : $10 \log_{10} \left(\frac{P_1}{P_0} \right)$. and for comparing voltages we can use: $20 \log_{10} \left(\frac{V_1}{V_0} \right)$, which is derived from $10 \log_{10} \left(\frac{V_1^2/R}{V_0^2/R} \right)$. Complete the following table of useful ratios: (use accuracy of 1 decimal in dB row)

P_1/P_0	1000	100	10	8	4	2	1	$\frac{1}{2}$	$\frac{1}{4}$	$\frac{1}{10}$	$\frac{1}{100}$	$\frac{1}{1000}$
V_1/V_0	$\sqrt{1000}$	10	$\sqrt{10}$			$\sqrt{2}$						$\frac{1}{\sqrt{1000}}$
Decibels (dB)	30	20				3						-30

(____/2)

4. In the case of the Fourier analysis, the oscilloscope compares the signals with a reference of $V_{\text{rms}} = 1 \text{ V}$. Recall that a sine wave with rms (root mean square) amplitude of $V_{\text{rms}} = 1 \text{ V}$ corresponds to a sine wave with a peak amplitude of $\sqrt{2} \text{ V}$, which is to say a peak-to-peak amplitude of $2\sqrt{2} \text{ V}$. To specify that the reference is $V_{\text{rms}} = 1 \text{ V}$, the decibel symbol is modified with the suffix “V” becoming “dBV”. Convert the voltages in the table below to dBV units (use accuracy of 1 decimal).

v	$V_{\text{rms}} = 1 \text{ V}$	$V_{\text{rms}} = 2 \text{ V}$	$V_{\text{rms}} = \sqrt{10} \text{ V}$	$V_{\text{rms}} = \sqrt{2} \text{ V}$	$V_{\text{rms}} = 1/10 \text{ V}$	$2\sqrt{2} \text{ V peak-to-peak}$	$4\sqrt{5} \text{ V peak-to-peak}$	2 V peak-to-peak	$\frac{2\sqrt{2}}{\sqrt{10}} \text{ V peak-to-peak}$
$v \text{ (dBV)}$	0.0								

(____/2)