

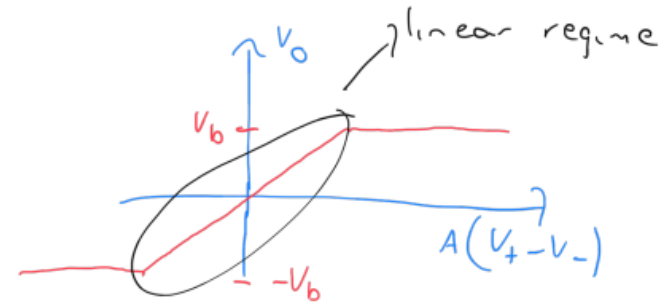


# Lecture 10, Wednesday, February 2, 2022

- Operational amplifier (op-amp)

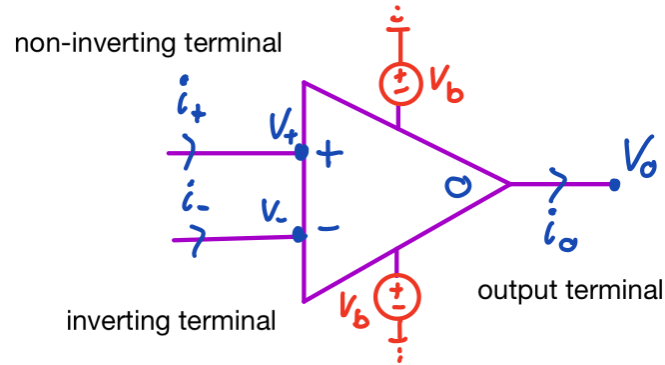

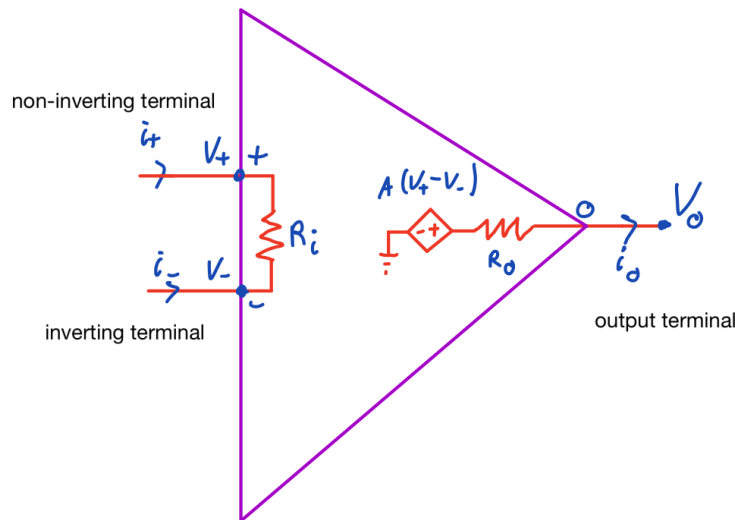– Want to operate in the linear regime, where the op-amp can be modeled as:



\*  $|V_+ - V_-|$  is very small ( $< 10\mu V$ )

\*  $R_i$  is very large ( $> M\Omega$ )

\*  $R_o$  is very small ( $< 10\Omega$ )

\*  $A$  is very large ( $> 10^6$ )

Can further approximate to

\* ***Ideal op-amp conditions:***

·  $i_+ = i_- = 0$ , within  $pA$

·  $V_+ = V_-$ , within  $\mu V$

continued on next page....

## Lecture 10, continued from previous page...

- It is a good idea to do KCL at inverting terminal
- It is a good idea to trace  $V_o$  back to  $V_s$
- It is a good idea to see where  $V_+$  and  $V_-$  are connected
- **never** do a KCL at ground when there is an op-amp
- **do not** assume  $i_o = 0$
- if you know the bias voltage  $v_b$ , make sure that  $|v_o| < v_b$