

Analog Signal Processing**Thursday, September 23, 8:45-10pm****Exam I**

Last Name (capitalized):	Solutions
-----------------------------------------	-----------

First Name:	
------------------------	--


UIN:	
-------------	--

netID:	
---------------	--

<p>Clearly PRINT your name in CAPITAL LETTERS.</p> <p>This is a closed book and closed notes exam.</p> <p>Calculators are not allowed.</p> <p>To get credit, please SHOW all your work and simplify your answers.</p> <p>Write your final answers in the spaces provided.</p> <p>All answers should INCLUDE UNITS whenever appropriate.</p> <p>The exam is printed double-sided.</p>	<p style="text-align: center;">DO NOT write in these spaces.</p> <p>Problem 1 (25 points):_____</p> <p>Problem 2 (25 points):_____</p> <p>Problem 3 (25 points):_____</p> <p>Problem 4 (25 points):_____</p> <p>Total: (100 points):_____</p>
---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

1. (25 pts) The two parts of this problem are unrelated.

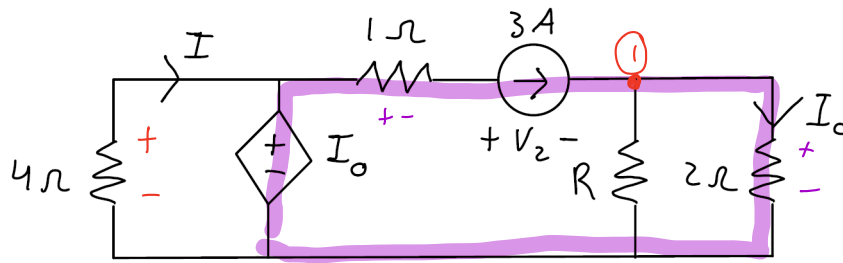- (a) [20 pts] Consider the circuit below. It is desired for the output current, $I_o = 1\text{A}$. Determine the value of R , I , V_2 , and the absorbed power at the current source, P_{I_s} .



$$R = \underline{1\Omega}$$

$$I = \underline{-1/4\text{ A}}$$

$$V_2 = \underline{-4\text{ V}}$$

$$P_{I_s} = \underline{-12\text{ W}}$$

3A are divided @ node (1) into the two resistors:

$$I_o = 3 \frac{R}{R+2} \rightarrow 1 = \frac{3R}{R+2} \rightarrow R+2 = 3R \rightarrow 2 = 2R \rightarrow R = 1$$

$V_{4\Omega} = I_o$ because in parallel

$$-4I = I_o \rightarrow I = -\frac{I_o}{4} = -\frac{1}{4}$$

KVL on purple loop: $-I_o + (1)(3) + V_2 + 2I_o = 0$

$$\rightarrow V_2 = -3 - 2I_o = -3 - 1 = -4$$

$$P_{I_s} = V_2 I = -4(1) = -12$$

- (b) [5 pts] Determine the magnitude and phase of the complex number $Z = \frac{e^{j\pi/2}}{e^{-j\pi/4} + e^{j\pi/4}}$.

Recall from Euler's: $\frac{e^{j\theta} + e^{-j\theta}}{2} = \cos \theta$


$$\rightarrow Z = \frac{e^{j\frac{\pi}{2}}}{2\cos(\frac{\pi}{4})} = \frac{e^{j\frac{\pi}{2}}}{2\frac{\sqrt{2}}{2}} = \frac{1}{\sqrt{2}} e^{j\frac{\pi}{2}} = \frac{\sqrt{2}}{2} e^{j\frac{\pi}{2}}$$

$$|Z| = \underline{\sqrt{2}/2}$$

$$\angle Z = \underline{\pi/2 \text{ rad}}$$

2. (25 points) Parts a and b are unrelated.

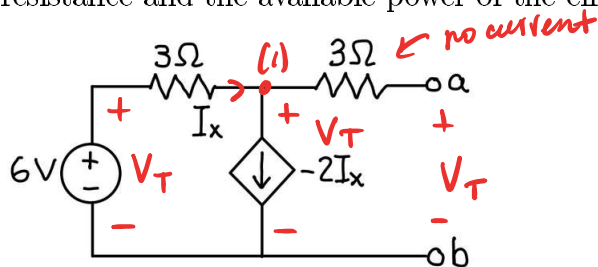(a) [10 pt] In the following circuit between a and b determine Thevenin's voltage, Thevenin's resistance and the available power of the circuit.



$$V_T = \underline{6V}$$

$$R_T = \underline{4\Omega}$$


$$P_a = \underline{9/4 W}$$

Find V_T :

$$\text{KCL @ (1): } I_x = -2I_x$$

$$I_x = 0 \Rightarrow V_T = 6V$$

Find R_T : test signal method:

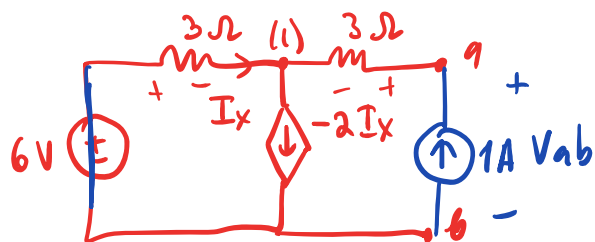

$$\text{KCL @ (1): } I_x + 1 = -2I_x$$

$$3I_x = -1$$

$$I_x = -1/3 A$$

$$\text{KVL: } 3I_x - 3 \cdot 1 + V_{ab} = 0$$


$$V_{ab} = -3 \cdot (-1/3) + 3 = 4V$$

$$R_T = 4\Omega$$

Find P_a :

$$P_a = \frac{V_T^2}{4R_T} = \frac{36}{4 \cdot 4} = \frac{36}{16} = \frac{9}{4} W$$

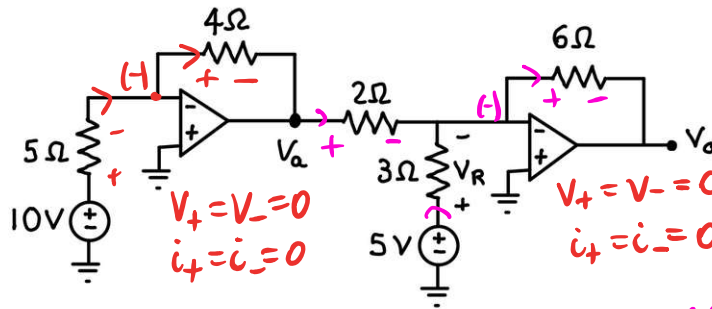- (b) [15 pts] Consider the ideal op amp circuit shown below: Assuming ideal op amp approximations, determine V_a , V_R and V_o .



$$V_a = \underline{-8V}$$

$$V_R = \underline{5V}$$

$$V_o = \underline{14V}$$

$$\text{KCL @ (-): } \frac{10 - V_-}{5} = \frac{V_- - V_a}{4}$$

$$\frac{10}{5} = -\frac{V_a}{4} \Rightarrow V_a = -8V$$

$$V_R = 5 - V_- = 5V$$



KCL @ (-):

$$\frac{V_a - V_-}{2} + \frac{5 - V_-}{3} = \frac{V_- - V_o}{6}$$

$$3V_a + 10 = -V_o$$

$$V_o = -3 \cdot (-8) - 10 = 14V$$

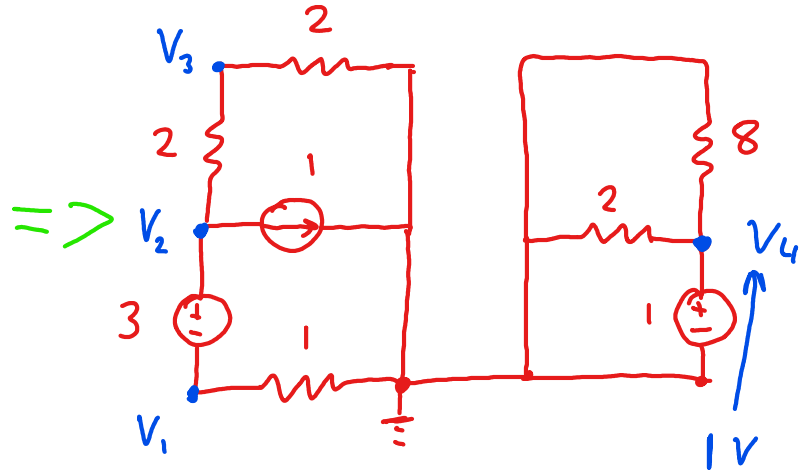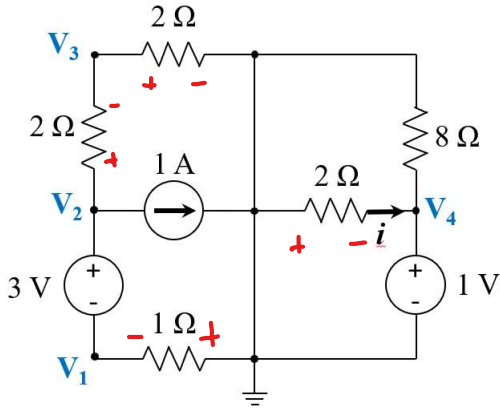3. (25 pts) Consider the following circuit.



(a) [20 pts] Use the node-voltage method to obtain the node voltages V_1 , V_2 , V_3 and V_4 .

$$3V = V_2 - V_1; \quad V_1 = V_2 - 3V$$

$$1V = V_4 - 0 = V_4$$

$$\text{KCL @ } \hat{V}_2: \frac{0 - V_1}{1} - 1 - \frac{V_2 - V_3}{2} = 0 \quad \text{KCL @ } \hat{V}_3: \frac{V_2 - V_3}{2} = \frac{V_3 - 0}{2}$$

$$-V_1 - 1 - \frac{V_2 - V_3}{2} = 0$$

$$-2V_3 + 3 - 1 - V_3 + \frac{V_3}{2} = 0$$

$$-3V_3 + \frac{V_3}{2} = -2$$

$$-\frac{5}{2}V_3 = -2$$

$$V_3 = \frac{4}{5}$$

$$V_2 = \frac{8}{5}$$

$$V_1 = -\frac{7}{5}$$

$$V_2 - V_3 = V_3$$

$$V_2 = 2V_3$$

$$V_1 = 2 \cdot V_3 - 3V$$

$$V_1 = -\frac{7}{5} V$$

$$V_2 = \frac{8}{5} V$$

$$V_3 = \frac{4}{5} V$$

$$V_4 = 1 V$$

(b) [5 pts] Determine i .


KVL (right bottom square)

$$i \cdot 2\Omega + 1V = 0$$

$$i = -\frac{1V}{2\Omega} = -\frac{1}{2} A$$

$$i = -\frac{1}{2} A$$

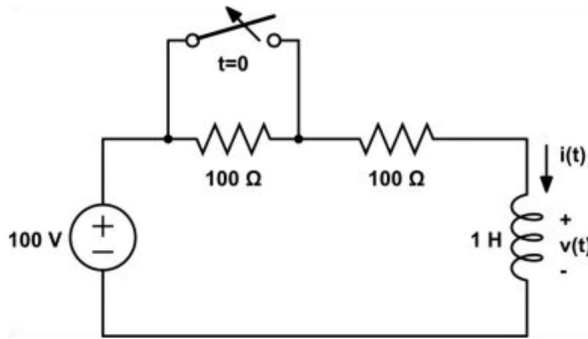4. (25 pts) In the circuit above, the switch has been closed for a very long time prior to $t = 0$.



- (a) ¹²~~22~~ pts] Determine an expression for $i(t)$ for $t > 0$, and identify its zero-state and zero-input parts.

KVL: $100 = R_T i(t) + L \frac{di}{dt}$

for $t > 0$ $\frac{100}{L} = \frac{di}{dt} + \frac{R_T}{L} i(t)$ $\tau = \frac{L}{R_T} = \frac{1}{200} = 5ms$

$i(t) = B + A e^{-t/\tau}$

$i(\infty) = B = 0.5A = I_N = f$
 $1A = i(0^+) = i(0^-) = B + A$
 $A = i(0^+) - B$

Simple solution method:
 $i(t) = 0.5 + 0.5 e^{-t/\tau}, \tau = 0.005s$

$i(t) = f + (i(0^+) - f) e^{-t/\tau}$

$i(0^+) = 0 \rightarrow i_{zs}(t) = f - f e^{-t/\tau} = 0.5 - 0.5 e^{-t/\tau}$
 $f = 0 \rightarrow i_{zi}(t) = i(0^+) e^{-t/\tau} = e^{-t/\tau}$
 $\tau = 0.005s$

$i_{ZI}(t) = e^{-t/\tau} A$

$i_{ZS}(t) = 0.5 - 0.5 e^{-t/\tau} A$

$i(t) = 0.5 + 0.5 e^{-t/\tau} A \quad \tau = 0.005s$

- (b) ³ [2.7 pts] Determine an expression for $v(t)$ for $t > 0$, and identify its zero-state and zero-input parts.

$$v(t) = L \frac{di(t)}{dt}$$

$$L = 1$$


$$\tau = \frac{1}{200} \text{ s} = 5 \text{ ms}$$

$$v_{ZI}(t) = \frac{di_{ZI}}{dt} = -\frac{1}{\tau} e^{-t/\tau} = -200 e^{-t/\tau}$$

$$v_{ZS}(t) = \frac{di_{ZS}}{dt} = -\frac{1-0.5}{\tau} e^{-t/\tau} = 100 e^{-t/\tau}$$

$$v(t) = v_{ZI}(t) + v_{ZS}(t) = -100 e^{-t/\tau}$$

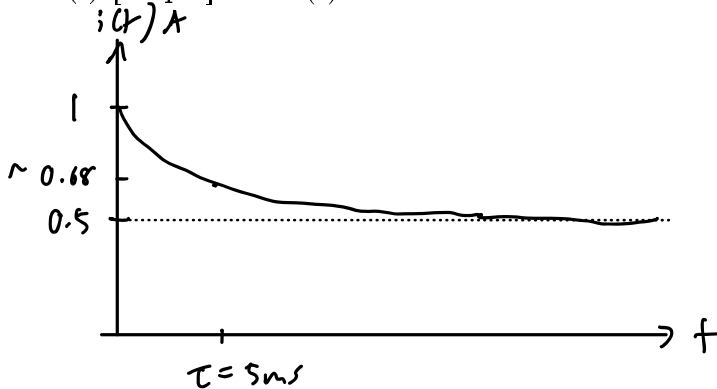- (c) ³ [2.7 pts] Plot $i(t)$ for $t > 0$.



- (d) ³ [2.7 pts] Plot $v(t)$ for $t > 0$.

