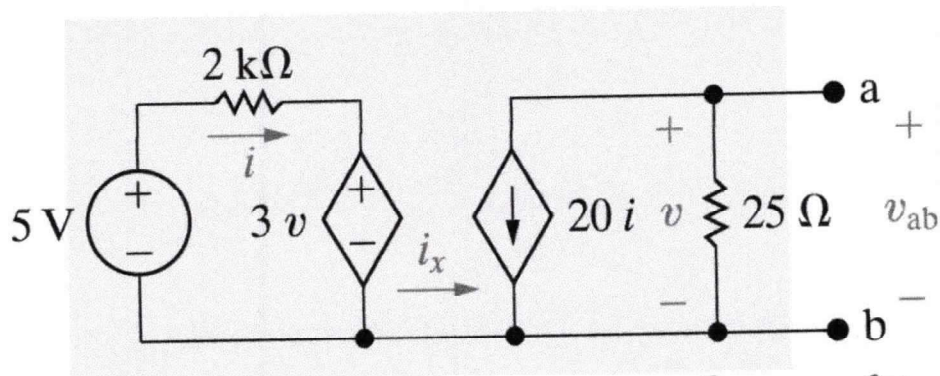



## Problem 1

Find the Thévenin equivalent for the circuit containing dependent sources shown below:



$$i_x = 0 \Rightarrow V_{Th} = v_{ab} = (-20i)(25) = -500i \quad i = \frac{5-3v}{2000} = \frac{5-3V_{Th}}{2000} \Rightarrow 2000i = -4V_{Th} = 5-3V_{Th} \Rightarrow \boxed{V_{Th} = -5V}$$


Next find short-circuit circuit

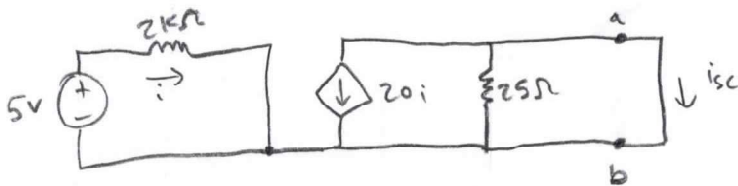

$$i_{sc} = -20i \quad i = \frac{5}{2000} = 0.0025 \Rightarrow i_{sc} = -20(0.0025) = -0.050$$


$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{-5}{-0.050} = 100\Omega$$

Thus,

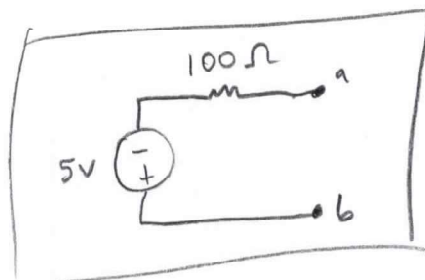
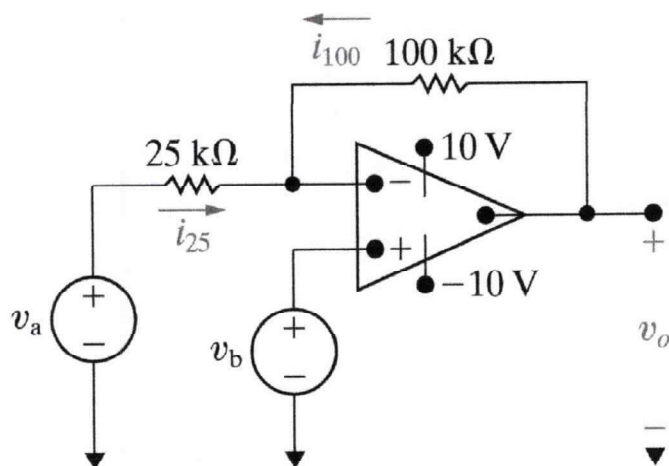
### Problem 3

The op amp shown is ideal. Calculate  $v_o$  if  $v_a = 1V$  and  $v_b = 0V$ . Repeat for  $v_a = 1V$  and  $v_b = 2V$ . If  $v_a = 1.5V$ , specify the range of  $v_b$  that avoids amplifier saturation.



$$\frac{0 - v_o}{100000} + \frac{0 - 1}{25000} = 0 \Rightarrow \frac{v_o}{100} = -\frac{1}{25} \Rightarrow \boxed{v_o = -4V}$$

$$\frac{2 - v_o}{100000} + \frac{2 - 1}{25000} = 0 \Rightarrow \frac{2}{100} - \frac{v_o}{100} + \frac{1}{25} = 0 \Rightarrow \frac{3}{50} = \frac{v_o}{100} \Rightarrow \boxed{v_o = 6V}$$

$$\frac{v_b - 1.5}{25000} + \frac{v_b - v_o}{100000} = 0 \Rightarrow v_b \left( \frac{1}{25} + \frac{1}{100} \right) = \frac{1.5}{25} + \frac{v_o}{100}$$

$$v_b = \frac{4}{5} \cdot \frac{3}{2} + \frac{v_o}{5} = \frac{1}{5}(6 + v_o)$$

$$5v_b - 6 = v_o$$

$$-10 \leq v_o \leq 10$$


$$-10 \leq 5v_b - 6 \leq 10$$

$$-4 \leq 5v_b \leq 16$$

$$\boxed{-0.8 \leq v_b \leq 3.2}$$
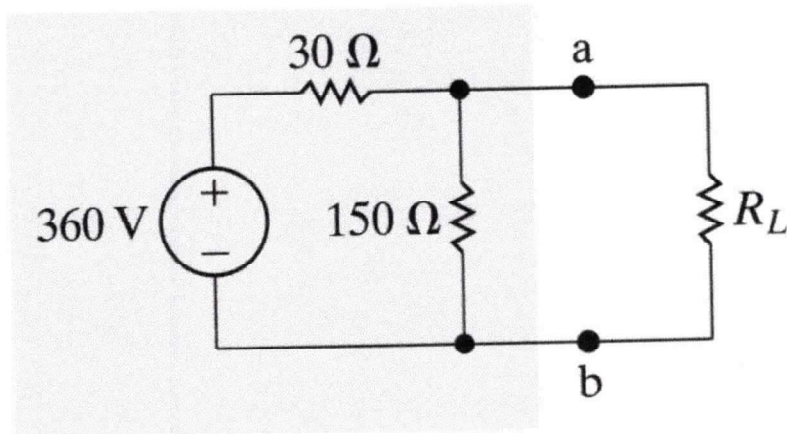
## Problem 4


For the circuit shown below, find the value of  $R_L$  that results in maximum power being transferred to  $R_L$ . Calculate the maximum power that can be delivered to  $R_L$ . When  $R_L$  is adjusted for maximum power transfer, what percentage of the power delivered by the 360V source reaches  $R_L$ ?



$V_{Th}$  for shaded part of circuit  $V_{Th} = \frac{150}{150+30} (360) = 300V$


$R_{Th} = \frac{150 \cdot 30}{150+30} = 25\Omega$

Now we have

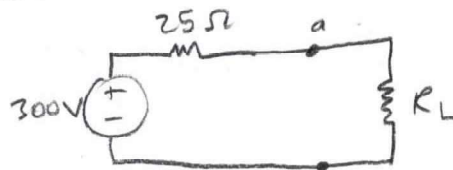


$R_L$  must equal  $R_{Th}$  for max power transfer  $\Rightarrow \boxed{R_L = 25\Omega}$

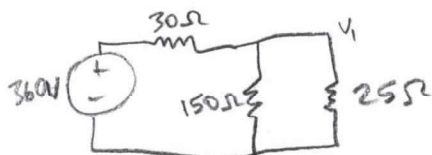$P_{max} = \frac{V_{Th}^2}{4R_L} = \frac{300^2}{100} = \boxed{900W}$



$\frac{150 \cdot 25}{150+25} = \frac{150}{7}$

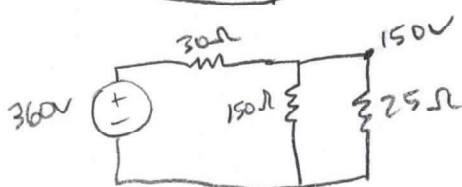
$\Rightarrow V_L = \frac{\frac{150}{7}}{30 + \frac{150}{7}} \cdot 360 = 150$



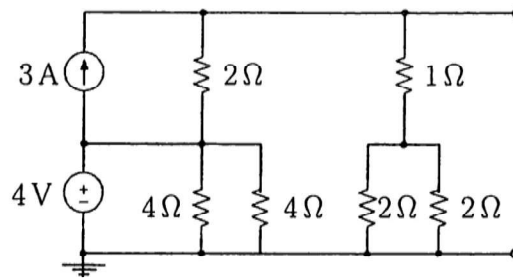
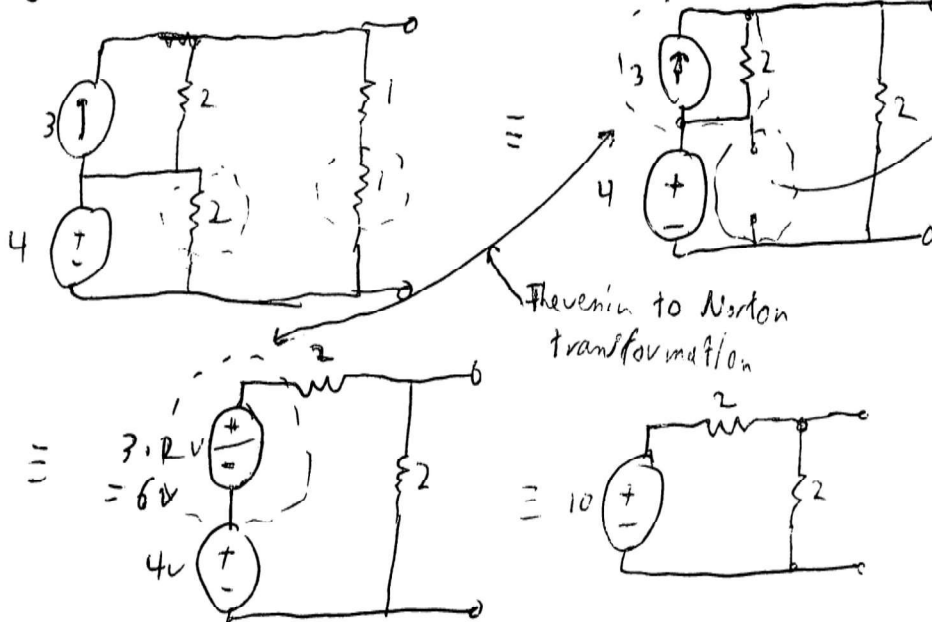
Total power is  $\frac{(360-150)^2}{30} + \frac{150^2}{150} + \frac{150^2}{25} = 1470 + 150 + 900$

Percentage in  $R_L$  is  $\frac{900}{2520} \cdot 100 = \boxed{35.71\%}$

(d) (10 pt) Reduce the following circuit to its Thevenin Equivalent, that is find  $V_T$ ,  $R_T$ .



  $R \parallel R = R/2$  since  $R_{||} = \frac{1}{\frac{1}{R} + \frac{1}{R}} = \frac{1}{\frac{2}{R}} = \frac{R}{2}$ , so the circuit above simplifies to



This resistor does not affect output at all, because it's in parallel with a voltage source that will maintain a fixed voltage and current across it regardless!

$$V_{\text{open circuit}} = \frac{2}{2+2} \cdot 10\text{V} = 5\text{V} \quad (\text{voltage divider})$$


$$R_{\text{Thev}} \rightarrow \text{replace independent voltage source with short circuit} \rightarrow 2 \parallel 2 = \frac{1}{\frac{1}{2} + \frac{1}{2}} = \frac{1}{1} = 1$$

replace independent voltage source with short circuit

$$V_T = 5\text{V}$$

$$R_T = 1\Omega$$

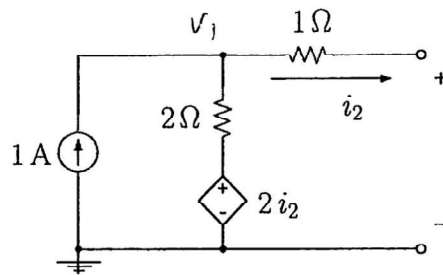
(b) (15pt) Find the Thevenin Equivalent Circuit.



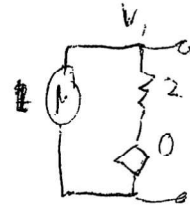
(i)  $V_{\text{open circuit}} = V_{\text{Thev}}$

$i_2 = 0$  so  $V_1 = V_{\text{oc}}$

$$1 = \frac{V_1}{2} \rightarrow V_1 = 2 = V_{\text{oc}} = \boxed{V_{\text{Thev}} = 2}$$



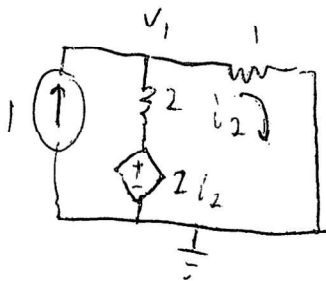(ii)  $i_{\text{short circuit}} = i_{\text{sc}}$



$i_2 = i_{\text{sc}} = \frac{V_1}{1} = V_1$

KCL at  $V_1$ :


$$1 = \frac{V_1 - 2i_2}{2} + \frac{V_1}{1} = \frac{V_1 - 2V_1}{2} + \frac{V_1}{1} = -\frac{V_1}{2} + V_1 = \frac{V_1}{2}$$

$V_1 = 2 \cdot 1 = 2$

$i_{\text{sc}} = \frac{2}{1} = \boxed{2 = i_N}$

(iii)  $R_{\text{Thev}} = \frac{V_{\text{oc}}}{i_{\text{sc}}} = \frac{2}{2} = \boxed{1\Omega = R_{\text{Thev}}}$

Alternatively, use test method

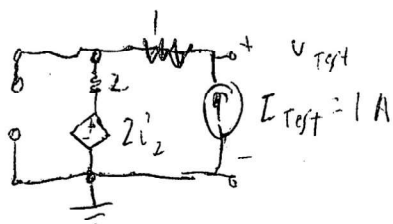


$i_2 = -1\text{A}$


So dependent source

$V_{\text{test}} = 1 \cdot I_{\text{test}} + 2 \cdot I_{\text{test}} - 2I_{\text{test}} = I_{\text{test}} = 1$

$R_{\text{Thev}} = \frac{1}{1} = 1$

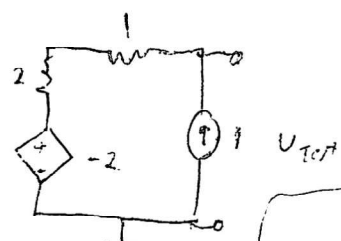


Thevenin equivalent circuit

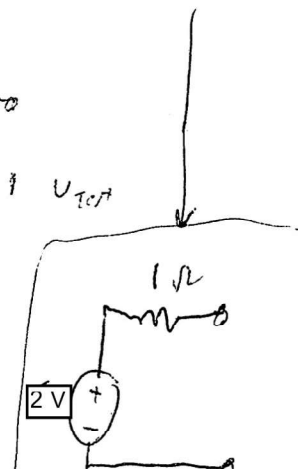

### 3. Problem 3 (25 points)

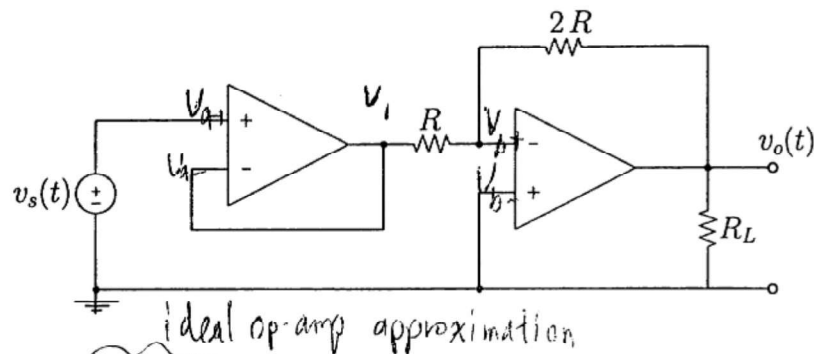- (a) (19 pt) Analyze the following circuit and find  $v_o/v_s$ . Use the ideal op-amp approximations.



Step 1: find  $v_1$ :  $v_{a+} = v_{a-} = v_s(t)$

But  $v_1 = v_{a-} \rightarrow v_1 = v_s(t)$

Step 2:  $v_{b-} = 0 = v_{b+}$

KCL at  $v_{b-}$  gives

$$\frac{v_1}{R} = \frac{0 - v_o(t)}{2R} = \frac{v_s}{R} \quad \text{so} \quad \frac{v_o}{v_s} = \frac{-2R}{R} = -2$$

$$\frac{v_o}{v_s} = -2$$

- (b) Find the power absorbed/supplied in  $R_L$  if

i. (2pt)  $R_L = 3 \Omega$

$$p_L = v_o(t) i_L(t) = \frac{v_o^2(t)}{R_L} = \frac{(2v_s(t))^2}{3} = \frac{4}{3} v_s^2(t)$$

$$p = \frac{4}{3} v_s^2(t)$$

ii. (2pt)  $R_L = 0 \Omega$

$v_o(t) = 0$  [overrules from ideal op-amp approximations]  
Power consumed internally across  $R_{b,out}$

so  $v_o(t) i_L(t) = 0$ ;  $i_L(t) = 0$

$$p = 0$$

iii. (2pt)  $R_L = \infty \Omega$


$$v_o(t) = 2v_s(t), \quad i_L(t) = \frac{2v_s(t)}{\infty} = 0$$

$$p = 0$$

$$p = v \cdot i = v \cdot 0 = 0$$

**Problem 2 (25 points)**

Analyze the following bridge circuit

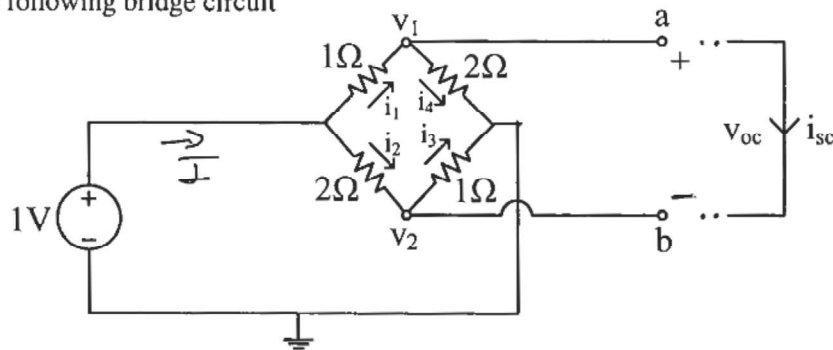

(a) The terminal  $v_1$  and  $v_2$  are open. Calculate  $v_1$ ,  $v_2$ , and  $v_{oc}$ .

$$v_1 = \frac{1}{3} \cdot 2 = \frac{2}{3} \quad v_2 = \frac{1}{3} \cdot 1$$

$$v_{oc} = v_1 - v_2$$

$$\begin{aligned} v_1 &= \frac{2}{3} \\ v_2 &= \frac{1}{3} \\ v_{oc} &= \frac{1}{3} \end{aligned}$$

(b) The terminals  $v_1$  and  $v_2$  are shorted together calculate  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$ , and  $i_{sc}$ .

$$I = \frac{1}{\frac{2}{3} + \frac{2}{3}} = \frac{3}{4}$$

$$\begin{aligned} i_1 &= \frac{3}{4} \cdot \frac{2}{3} = \frac{1}{2} \\ i_2 &= \frac{3}{4} \cdot \frac{1}{3} = \frac{1}{4} \\ i_3 &= \frac{1}{2} \\ i_4 &= \frac{1}{4} \end{aligned}$$


$$\begin{aligned} i_1 &= \frac{1}{2} \\ i_2 &= \frac{1}{4} \\ i_3 &= \frac{1}{2} \\ i_4 &= \frac{1}{4} \\ i_{sc} &= i_1 - i_4 = \frac{1}{2} - \frac{1}{4} = \frac{1}{4} \end{aligned}$$

(c) Compute the Thevenin resistance of the circuit between a and b.

$$R_T = \frac{V_T}{I_{sc}} = \frac{\frac{1}{3}}{\frac{1}{4}} = \frac{4}{3}$$


$$R_T = \frac{4}{3}$$

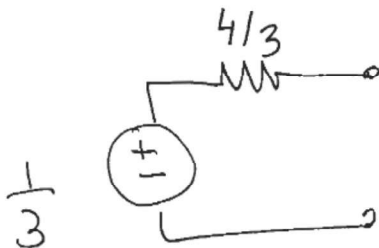(d) Draw and label Thevenin and Norton equivalent circuits between a and b.



### Problem 3 (25 points)

Consider the following op-amp circuit.

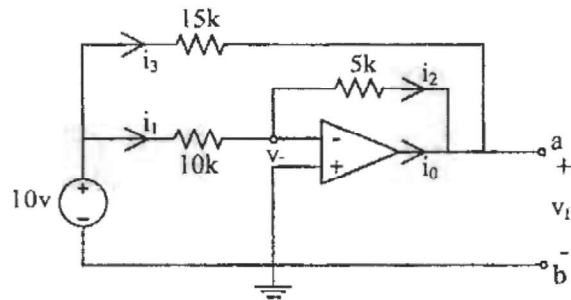

(a) Find  $v_-$ ,  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_o$ , and  $v_o$ .

$$v_+ = v_- = 0V \text{ (given)}$$

$$\therefore I_1 = \frac{10V - 0}{10k\Omega} = 1mA$$

$$\therefore I_2 = I_1 = 1mA \text{ (because current cannot enter input of op amp)}$$

$$\therefore \text{For } 5K \text{ resistor, } \frac{0 - V_{out}}{5K} = I_2 = 1mA$$


$$\therefore V_{out} = -5V$$

$$\therefore \text{For } 15K \text{ resistor, } \frac{10V - (-5V)}{15K} = 1mA = I_3$$

$$\text{Finally, } I_o = I_2 + I_3 = -2mA$$

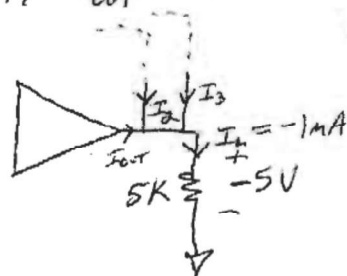(b) If you connect  $R_L = 5k\Omega$  between a and b, what is  $v_o$  and  $i_o$ ?

connection of a  $5k\Omega$  load does not affect  $I_1$  &  $I_2$ .  
 $\therefore V_{out}$  remains at  $-5V$ . Neither does  $I_3$  change.



$\therefore$  with the load,

$$\begin{aligned} I_{out} &= -(I_2 + I_3 - I_L) \\ &= -(1mA + 1mA - (-1mA)) \\ &= -3mA \end{aligned}$$

$$i_o = -3mA \text{ (+3)}$$


$$v_o = -5V \text{ (+4)}$$



(Problem 3 cont'd)

(b) In the following circuit, assuming linear operation and ideal op-amp approximation, determine the node voltages  $v_0$ ,  $v_1$ , and the currents  $i_0$ ,  $i_1$ .

10 pts

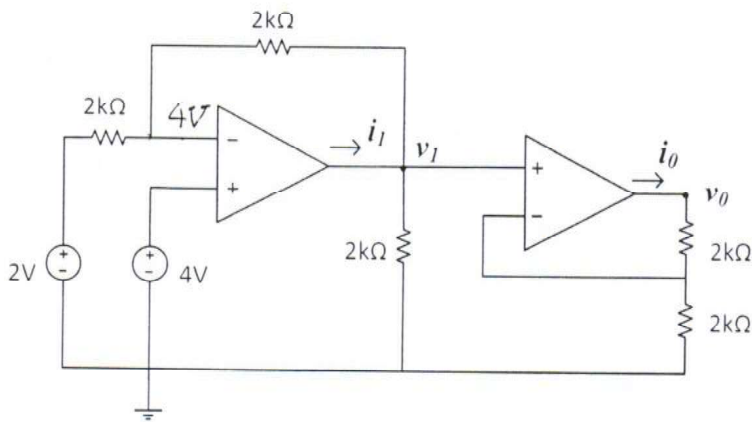

$$v_0 = \underline{12\text{ V}}$$

$$v_1 = \underline{6\text{ V}}$$

$$i_0 = \underline{3\text{ mA}}$$

$$i_1 = \underline{4\text{ mA}}$$

Apply KCL at the "-" input of the first op-amp.

$$\frac{4-2}{2k} = \frac{v_1-4}{2k} \rightarrow v_1 = 6\text{ V}$$

Apply KCL at the output of the first op-amp.

$$i_1 = \frac{v_1}{2k} + \frac{v_1-4}{2k} = 4\text{ mA}$$

Apply KCL at the "-" input of the second op-amp.

$$\frac{v_0-v_1}{2k} = \frac{v_1}{2k} \rightarrow v_0 = 2v_1 = 12\text{ V}$$

Apply KCL at the output of the second op-amp

$$i_0 = \frac{v_0}{4k} \rightarrow i_0 = 3\text{ mA}$$