

ECE 210 (AL2) - ECE 211 (E)

Chapter 5


Frequency Response $H(\omega)$ of LTI Systems

Olga Mironenko
University of Illinois
Spring 2022

Chapter objectives

- Understand the meaning and application of an LTI system's frequency response
- Be able to obtain the frequency response of an LTI system
- Know the properties of the frequency response of an LTI system
- Use the frequency response of an LTI system obtain the system's response to co-sinusoidal inputs
- Use the frequency response of an LTI system obtain the system's response to multifrequency co-sinusoidal inputs

• Example #1

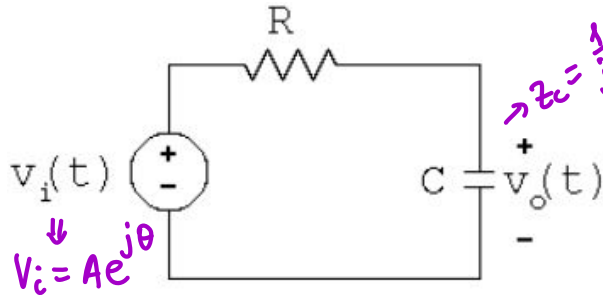

- Let $v_i(t) = A \cos(2t + \theta)$
- Determine $v_o(t)$

$$\rightarrow Z_C = \frac{1}{j\omega C} = \frac{1}{j2C}$$


$$V_o = V_i \frac{\frac{1}{j2C}}{R + \frac{1}{j2C}} = V_i \frac{1}{j2RC + 1} =$$

$$= \frac{|V_i| e^{j\angle V_i}}{\sqrt{1^2 + (2RC)^2} e^{j \tan^{-1}(\frac{2RC}{1})}}$$

$$V_o = \frac{|V_i|}{\sqrt{1 + 4R^2C^2}} e^{j(\angle V_i - \tan^{-1}(2RC))}$$

$$v_o(t) = \frac{A}{\sqrt{1 + 4R^2C^2}} \cos(2t + \theta - \tan^{-1}(2RC))$$

• Example #1

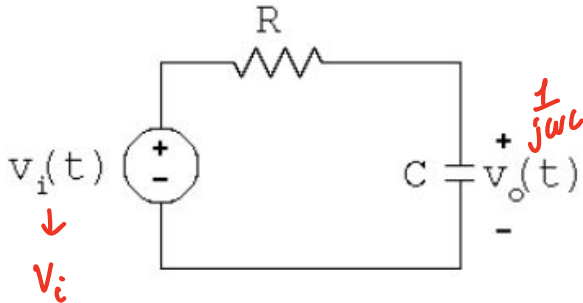

$$V_o = \frac{V_i \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = V_i \frac{1}{j\omega RC + 1} = V_o$$

$H(\omega)$ frequency response

- What if we change the frequency of the input?

$$V_o = \frac{|V_i|}{\sqrt{1 + \omega^2 R^2 C^2}} e^{j(\phi V_i - \tan^{-1}(\omega RC))}$$

$$v_{o,ss}(t) = \frac{|V_i|}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi V_i - \tan^{-1}(\omega RC)) V$$

phase response $\phi H(\omega)$

$$H(\omega) = |H(\omega)| e^{j\phi H(\omega)}$$

↓ amplitude response $|H(\omega)|$

- Frequency response of LTI systems

$$V_o = V_i H(\omega)$$

\swarrow output phasor
 \nwarrow input phasor

- Frequency response $H(\omega)$

$$V_i = |V_i| e^{j\angle V_i}$$

$$V_o = |V_i| |H(\omega)| e^{j(\angle V_i + \angle H(\omega))}$$

real signal \rightarrow LTI \rightarrow real signal

$$|V_i| |H(\omega)| \cos(\dots)$$

$$v_i(t) = |V_i| \cos(\omega t + \angle V_i)$$

$$v_o(t) = |V_i| |H(\omega)| \cos(\omega t + \angle V_i + \angle H(\omega))$$

Note: works the same way if an input is a sin \sim

• Frequency response of LTI systems-cont

$$v_o(t) = |V_i| |H(\omega)| \cos(\omega t + \angle V_i + \angle H(\omega))$$


• Amplitude response $|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

• Phase response $\angle H(\omega)$

$$\frac{e^{j0}}{e^{j \tan^{-1}(\omega RC)}}$$
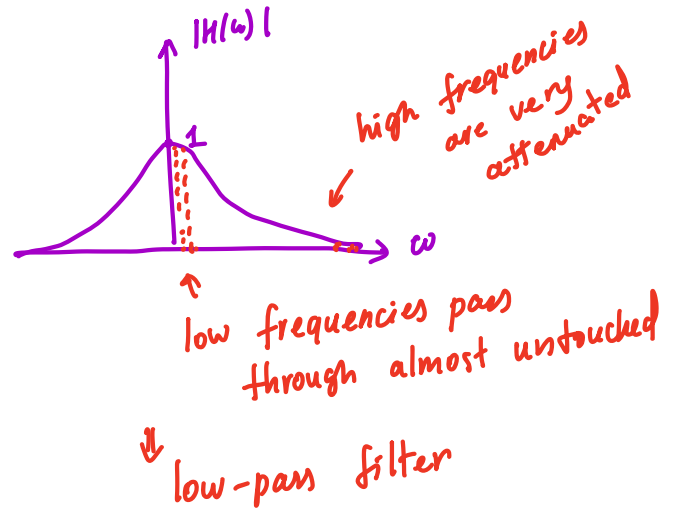
$$\angle H(\omega) = -\tan^{-1}(\omega RC)$$



• Example #1-cont

- Recall

$$|H(\omega)| = \frac{1}{\sqrt{1+(\omega RC)^2}}$$

$$\angle H(\omega) = -\tan^{-1}(\omega RC)$$

- Determine $v_o(t)$ if $v_i(t) = 2 \cos(3t + \frac{\pi}{3})$

$$v_o(t) = 2 \cdot |H(3)| \cos(3t + \frac{\pi}{3} + \angle H(3)) = 2 \frac{1}{\sqrt{1+9R^2C^2}} \cos(3t + \frac{\pi}{3} - \tan^{-1}(3RC)) \text{ V}$$

- Determine $v_o(t)$ if $v_i(t) = 3 \sin(6t + \frac{\pi}{6}) = 3 \cos(6t + \frac{\pi}{6} - \frac{\pi}{2})$

$$v_o(t) = 3 \cdot |H(6)| \cos(6t + \frac{\pi}{6} - \frac{\pi}{2} + \angle H(6)) =$$

$$= 3 \cdot |H(6)| \sin(6t + \frac{\pi}{6} + \angle H(6))$$

$$v_o(t) = 3 \cdot |H(6)| \sin(6t + \frac{\pi}{6} + \angle H(6))$$

• Frequency response of LTI systems-cont

- More generally, for LTI systems with

input $f(t) = \text{Re} \{ F e^{j\omega t} \}$
 output $y(t) = \text{Re} \{ Y e^{j\omega t} \}$

We have:

output phasor
input phasor

$$Y = FH(\omega)$$

$$F = |F| e^{j(\angle F)}$$

$$Y = |F| |H(\omega)| e^{j(\angle F + \angle H(\omega))}$$

$$f(t) \rightarrow \boxed{\text{LTI}} \rightarrow y(t)$$

$$\downarrow$$

$$F \rightarrow \boxed{H(\omega)} \rightarrow Y = F \cdot H(\omega)$$


$$\Downarrow$$

$$\boxed{H(\omega) = \frac{Y}{F}}$$

$$f(t) = |F| \cos(\omega t + \angle F)$$

$$y(t) = |F| |H(\omega)| \cos(\omega t + \angle F + \angle H(\omega))$$

• Example #2

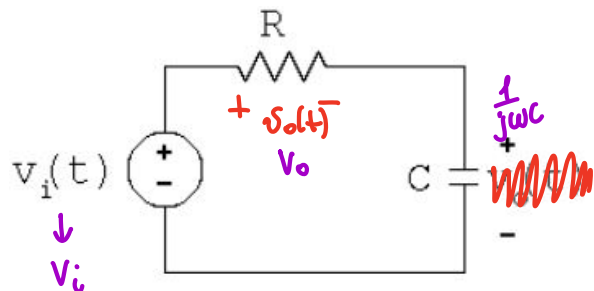


$$V_o = V_i \frac{R}{R + \frac{1}{j\omega C}} = V_i \frac{j\omega RC}{j\omega RC + 1} H(\omega)$$

$$Y = F \cdot H(\omega)$$

- Let $v_i(t) = A \cos(\omega t + \theta)$
- Determine $H(\omega)$, $|H(\omega)|$ and $\angle H(\omega)$


$$|H(\omega)| = \frac{|\omega| RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$
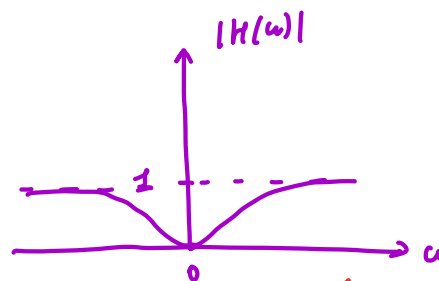
$$\angle H(\omega) = \begin{cases} \pi/2 - \tan^{-1}(\omega RC) & \text{if } \omega > 0 \\ -\pi/2 - \tan^{-1}(\omega RC) & \text{if } \omega < 0 \\ 0 & \text{if } \omega = 0 \end{cases}$$



↑ high frequencies pass through almost untouched
 ↓ high-pass filter

• Example #3

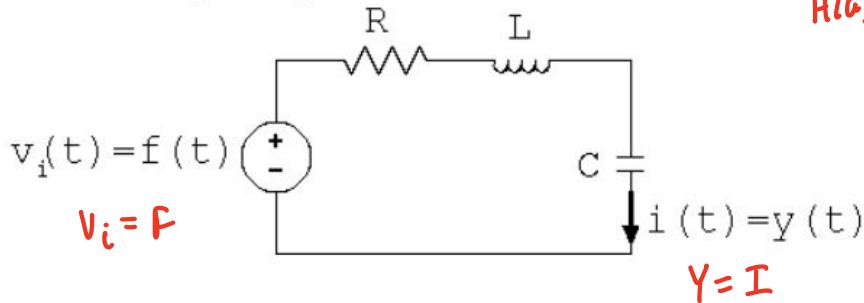

$$H(\omega) = \frac{Y}{F} = \frac{I}{V_i}$$


$$I = \frac{V_i}{R + j\omega L + \frac{1}{j\omega C}} =$$

$$= \frac{j\omega C V_i}{j\omega RC - \omega^2 LC + 1}$$

$H(\omega)$

- Let $v_i(t) = A \cos(\omega t + \theta)$
- Determine $H(\omega)$, $|H(\omega)|$ and $\angle H(\omega)$

$$|H(\omega)| = \frac{|\omega| C}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

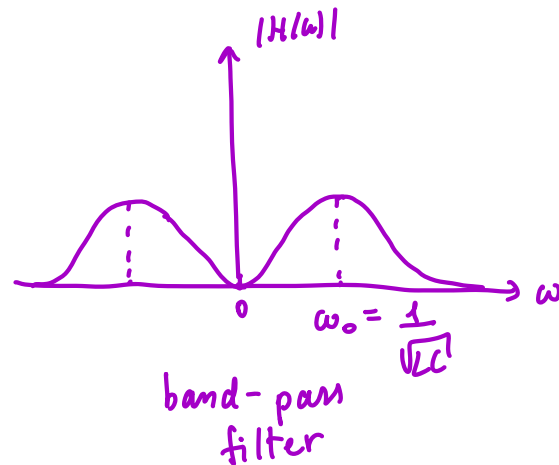

• Example #4

- Consider the ODE

$$\frac{dy}{dt} + y = 3f(t)$$

- Let $f(t) = A \cos(\omega t + \theta)$
- Determine $H(\omega)$, $|H(\omega)|$ and $\angle H(\omega)$

$$H(\omega) = \frac{Y}{F} = \frac{3}{1+j\omega}$$


$$|H(\omega)| = \frac{3}{\sqrt{1+\omega^2}}$$

$$\angle H(\omega) = 0 - \tan^{-1}(\omega) = -\tan^{-1}(\omega)$$

↓ phasors

$$j\omega Y + Y = 3F$$

$$Y = \frac{3F}{j\omega + 1}$$

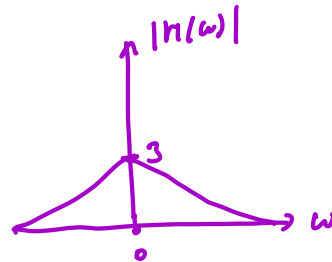

low-pass filter

• General first-order filters

- Low-pass *and second*

$$|H(0)| = 1$$

$$|H(\infty)| = 0$$

$$|H(\omega)| \approx \frac{1}{\sqrt{1+\omega^2}}$$

- High-pass

$$|H(0)| = 0$$

$$|H(\infty)| = 1$$

$$|H(\omega)| \approx \frac{\omega}{\sqrt{1+\omega^2}}$$

- Band-pass

$$|H(0)| = 0$$

$$|H(\infty)| = 0$$

in between $\neq 0$

$$|H(\omega)| \approx \frac{\omega}{\sqrt{\omega^2 + (1-\omega^2)^2}}$$

- $H(\omega)$ is only meaningful for **dissipative** LTI systems

- Properties of $H(\omega)$ for real-valued LTI systems

- Conjugate symmetry

$$H(\omega) = H^*(-\omega)$$

$$j\omega L \quad (j(-\omega)L)^* = -j \cdot (-\omega)L = j\omega L$$

- Even amplitude response

$$|H(\omega)| = |H(-\omega)|$$

- Odd phase response

$$\angle H(\omega) = -\angle H(-\omega)$$


$$-\angle H(\omega) = \angle H(-\omega)$$

- Properties of $H(\omega)$ -cont

- Real-valued DC response

$$H(0) \in \mathbb{R}$$

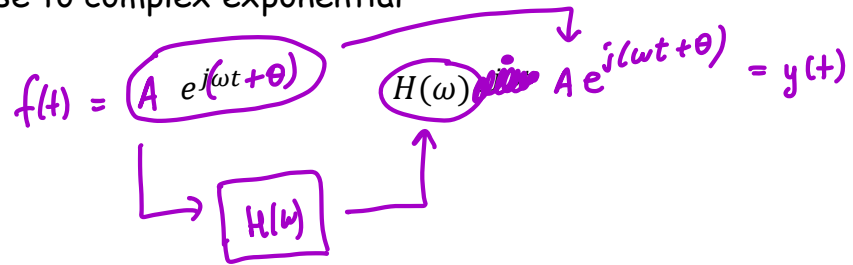- Steady-state response to complex exponential



• Example #5

- What if there are multiple frequencies?

- Let $f(t) = \cos\left(\frac{1}{2}t\right) + 3 \cos\left(2t + \frac{\pi}{4}\right) + 2 \sin(3t)$

be the input to the LTI system with input-output rule

- Determine $y_{ss}(t)$

① $H(\omega)$, $|H(\omega)|$, $\angle H(\omega)$

$$H(\omega) = \frac{Y}{F} = j\omega$$

$$|H(\omega)| = |\omega|$$

$$\angle H(\omega) = \begin{cases} \pi/2 & \omega > 0 \\ -\pi/2 & \omega < 0 \\ 0 & \omega = 0 \end{cases}$$

$$y(t) = \frac{d}{dt}f(t)$$

↓ phase shift

$$Y = j\omega F$$

• Example #5-cont

$$f(t) = \underbrace{1 \cos\left(\frac{1}{2}t\right)}_{\omega_1} + \underbrace{3 \cos\left(2t + \frac{\pi}{4}\right)}_{\omega_2} + \underbrace{2 \sin(3t)}_{\omega_3}$$

$$y(t) = \frac{d}{dt} f(t)$$

- Determine $y_{ss}(t)$

$$y_{ss}(t) = 1 \cdot |H(\omega_1)| \cos\left(\frac{1}{2}t + \angle H(\omega_1)\right) +$$

$$+ 3 \cdot |H(\omega_2)| \cos\left(2t + \frac{\pi}{4} + \angle H(\omega_2)\right) +$$

$$+ 2 \cdot |H(\omega_3)| \sin\left(3t + \angle H(\omega_3)\right) =$$

$$= 1 \cdot \frac{1}{2} \cos\left(\frac{1}{2}t + \frac{\pi}{2}\right) + 3 \cdot 2 \cos\left(2t + \frac{\pi}{4} + \frac{\pi}{2}\right) + 2 \cdot 3 \sin\left(3t + \frac{\pi}{2}\right)$$


$$|H(\omega)| = |\omega|$$

$$\angle H(\omega) =$$

$$\begin{cases} \pi/2 & \omega > 0 \\ -\pi/2 & \omega < 0 \\ 0 & \omega = 0 \end{cases}$$

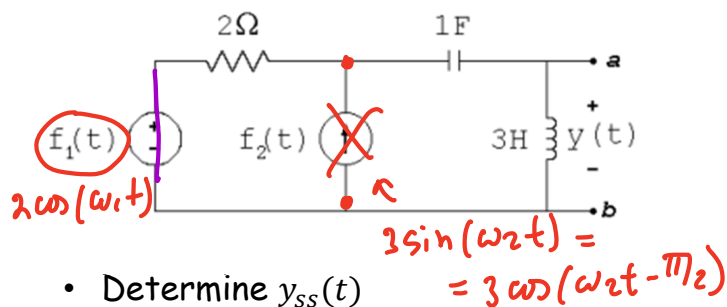
• Example #6

Consider the circuit below, where $f_1(t) = 2 \cos\left(\frac{1}{3}t\right)$ V and $f_2(t) = 3 \sin(t)$ A.




- Determine $y_{ss}(t)$

Only $f_1(t)$:

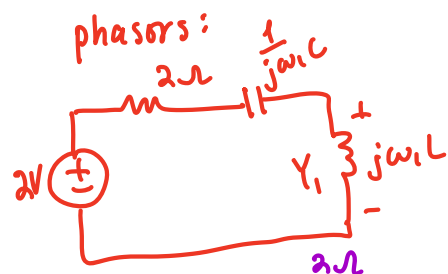

Only f_2 :

phasors:

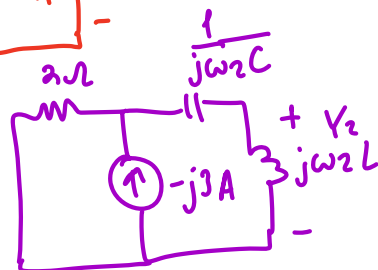

$$\omega_1 = \frac{1}{3} \text{ rad/s}$$

$$\omega_2 = 1 \text{ rad/s}$$

look at effect of each source individually, and add in time domain!

$$y_{ss}(t) = y_{ss1}(t) + y_{ss2}(t)$$

$$Y_1 = \frac{1}{\sqrt{2}} e^{j\frac{3\pi}{4}} \rightarrow y_{ss1}(t) = \dots$$

$$Y_2 = \frac{9}{\sqrt{2}} e^{-j\pi/4} \rightarrow y_{ss2}(t) = \dots$$

$$y_{ss}(t) = y_{ss1}(t) + y_{ss2}(t)$$

- In general

- What if there are multiple frequencies?

$$f(t) = \sum_n c_n \cos(\omega_n t + \theta_n) + \sum_m F_m e^{j\omega_m t} + \sum_k b_k \sin(\omega_k t + \psi_k)$$

$$f(t) \rightarrow \boxed{H(\omega)} \rightarrow y(t) = \sum_n |H(\omega_n)| c_n \cos(\omega_n t + \theta_n + \angle H(\omega_n)) +$$

$$+ \sum_m H(\omega_m) F_m e^{j\omega_m t} + \sum_k |H(\omega_k)| b_k \sin(\omega_k t + \psi_k + \angle H(\omega_k))$$

- Decibel amplitude response

$$|H(\omega)|_{dB} = 10 \log_{10}(|H(\omega)|^2) = 20 \log |H(\omega)|$$

- Small differences are emphasized

$$\text{if } |H(\omega)| = \begin{cases} \frac{1}{\sqrt{2}} \\ 1 \\ \sqrt{2} \\ 2 \end{cases} \quad \begin{array}{l} \text{then } |H(\omega)|_{dB} = -3\text{dB} \\ \text{then } |H(\omega)|_{dB} = 0\text{dB} \\ \text{then } |H(\omega)|_{dB} = 3\text{dB} \\ \text{then } |H(\omega)|_{dB} = 6\text{dB} \end{array}$$

Chapter objectives

- Understand the meaning and application of an LTI system's frequency response
- Be able to obtain the frequency response of an LTI system
- Know the properties of the frequency response of an LTI system
- Use the frequency response of an LTI system obtain the system's response to co-sinusoidal inputs
- Use the frequency response of an LTI system obtain the system's response to multifrequency co-sinusoidal inputs