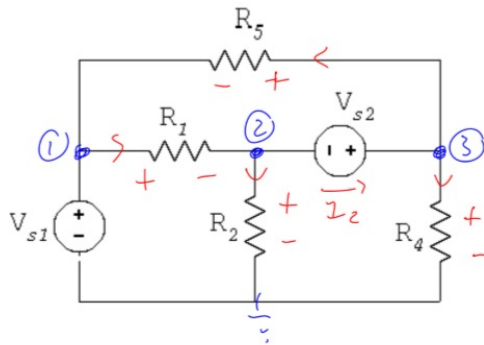


- **Example #5-cont:** Use the node-voltage method to determine all node voltages in this circuit



Assume : $R_i = 2\Omega$ for all i

$$V_{s1} = 1V$$

$$V_{s2} = 2V$$

$$1 = V_1 \quad (1)$$

$$2 = V_3 - V_2 \quad (2)$$

$$0 = -V_1 + V_2 + V_3 \quad (3)$$

:


$$V_3 = \frac{3}{2}V$$

$$V_2 = -\frac{1}{2}V$$

- Loop-current method

- Step #1:


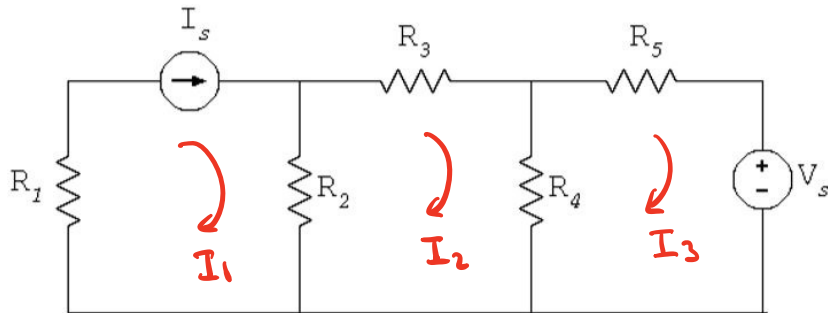
Assign loop currents I_1, I_2, \dots, I_n .



- Loop-current method

- Step #2:

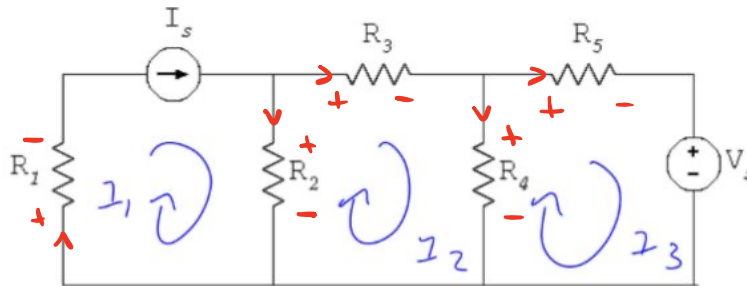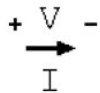
Assign current directions and polarities to all elements (use SRS for simplicity).



- Loop-current method

- Step #3:

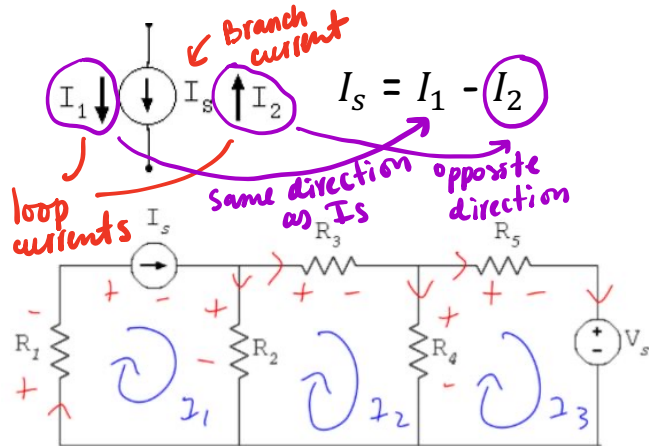Use current sources to obtain equations between their loop currents



Branch current vs loop current


Branch current: net current through an element in a direction of arrow.

It might consist of multiple loop currents, some in the same direction, some in the opposite direction.

- Loop-current method

- Step #4:

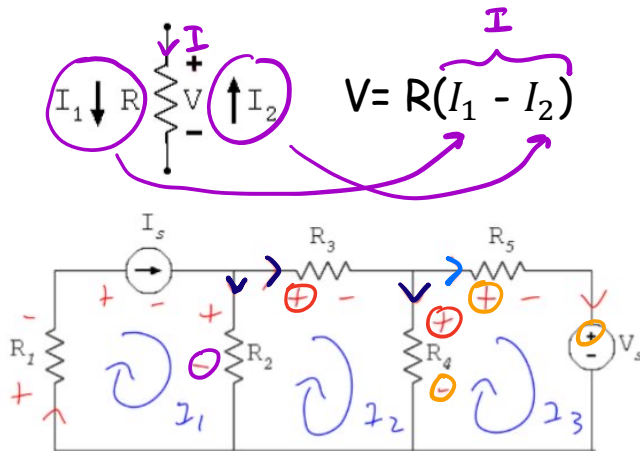Use KVL on remaining loops to get a total of n equations in terms of the loop currents.



$$I_s = I_1 \quad (1)$$


$$\text{KVL @ (2)}: -R_2(I_1 - I_2) + R_3(I_2)$$

$$+ R_4(I_2 - I_3) = 0 \quad (2)$$

$$\text{KVL @ (3)}: -R_4(I_2 - I_3) + R_5(I_3)$$

$$+ V_s = 0 \quad (3)$$

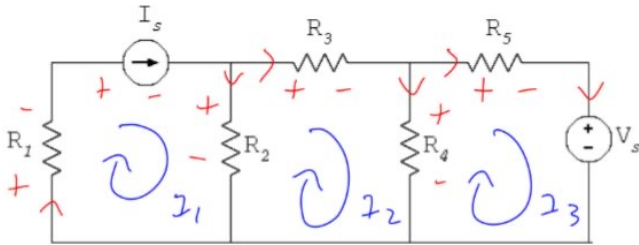- Loop-current method
- Step #5:
Solve equations



Assume $R_i = 2\Omega$ for all i

$$I_s = 2A$$

$$V_s = 4V$$

$$2 = I_1 \quad (1)$$

$$0 = 2I_1 - 6I_2 + 2I_3 \quad (2)$$

$$4 = 2I_2 - 4I_3 \quad (3)$$

;

$$I_2 = \frac{2}{5} A$$


$$I_3 = -\frac{4}{5} A$$

• Loop-current method: summary


1. Assign loop currents I_1, I_2, \dots, I_n .
2. Assign current directions and polarities to all elements (use SRS for simplicity)



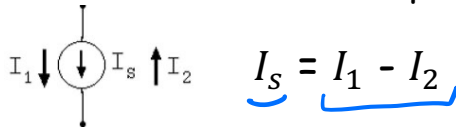3. Use current sources to obtain equations between their loop currents




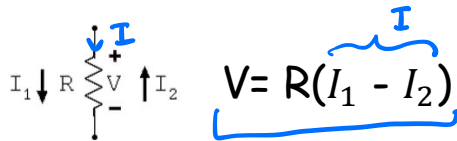4. Use KVL on remaining loops to get a total of n equations in terms of the loop currents



5. Solve equations

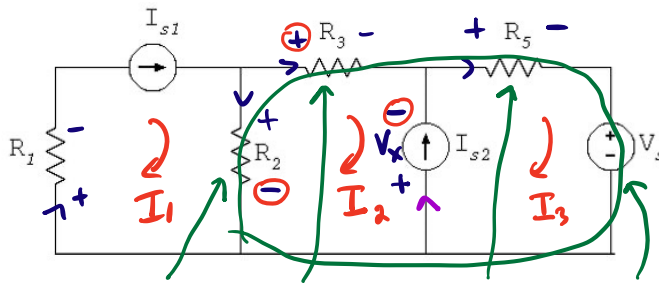- **Example #6:** Use the loop-current method to obtain all loop currents



$$I_{s1} = I_1 \quad (1)$$

$$I_{s2} = I_3 - I_2 \quad (2)$$

KVL on loop 2:

$$-R_2(I_1 - I_2) + R_3(I_2) + V_s = 0$$

$$-R_2(I_1 - I_2) + R_3 \cdot I_2 + R_5 \cdot I_3 + V_s = 0$$

Superloop 2-3: combines loops 2 and 3 into a single loop KVL bypassing the I_{s2} current source. Superloop is formed around loops sharing common boundary that includes a current source.

$$-V_x = 0 \quad (3)$$

KVL on loop 3:

$$V_x + R_5 \cdot I_3 + V_s = 0 \quad (4)$$