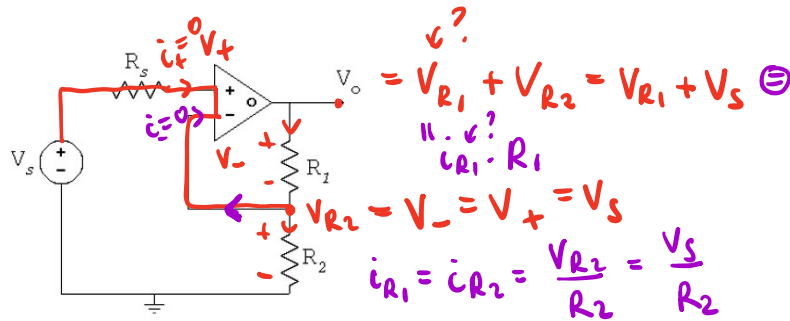


• Example #2: non-inverting amplifier

- Obtain V_o in the following circuit assuming the ideal op-amp approximation



$$\boxed{V_+ = V_-}$$

$$\boxed{i_+ = i_- = 0}$$

$$\Leftrightarrow \left(\frac{V_s}{R_2}\right) \cdot R_1 + V_s =$$

$$= V_s \left(1 + \frac{R_1}{R_2}\right) = V_o$$


Recall: $i_o \neq 0$ (in general).

Recall: Never do KCL @
ground in op-amp circuit!

↑
 V_o has the same
polarity as V_s .

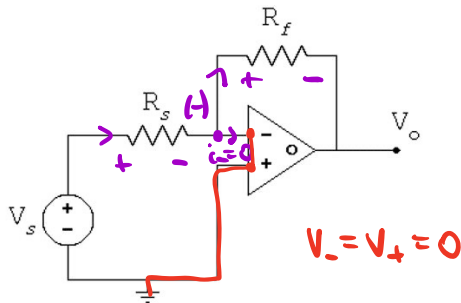• Example #3: inverting amplifier

- Obtain V_o in the following circuit assuming the ideal op-amp approximation



KCL @ $(-)$:


$$V_+ = V_- \\ i_+ = i_- = 0$$

$$\frac{V_s - V_-}{R_s} = \frac{V_- - V_o}{R_f} + 0$$

$$\begin{aligned} \frac{V_s}{R_s} &= -\frac{V_o}{R_f} \Rightarrow V_o = -\frac{V_s}{R_s} R_f = \\ &= -\left(\frac{R_f}{R_s}\right) V_s \end{aligned}$$

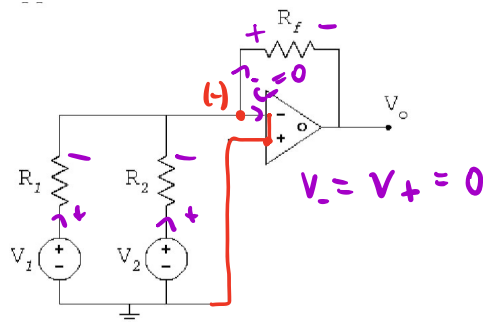• Example #4: **adder**

- Obtain V_o in the following circuit assuming the ideal op-amp approximation



KCL @ (-):

$$\frac{V_1 - V_-}{R_1} + \frac{V_2 - V_-}{R_2} = \frac{V_- - V_o}{R_f}$$

$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right)$$

Find V_o - ?

a) $- \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right)$

b) $\frac{R_2}{R_1} (V_1 + V_2)$


c) $\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right)$

d) 0

Note: could do superposition on V_1 and V_2 to get same circuit as in ex 3.

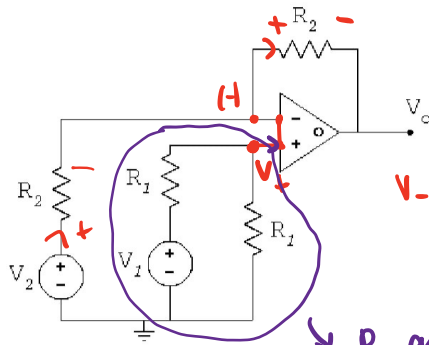• Example #5: subtractor

- Obtain V_o in the following circuit assuming the ideal op-amp approximation



KCL @ (-): $\frac{V_2 - V_-}{R_2} = \frac{V_- - V_o}{R_2} \Rightarrow$

$V_- = V_+ - ?$


$V_o = 2V_- - V_2 =$
 $= V_1 - V_2$

\Downarrow
 voltage division:
 $V_+ = V_1 \left(\frac{R_1}{R_1 + R_1} \right) = \frac{V_1}{2} = V_-$

- Example #6: Obtain V_o in the following circuit assuming the ideal op-amp approximation

$$V_+ = V_-$$

$$i_+ = i_- = 0$$

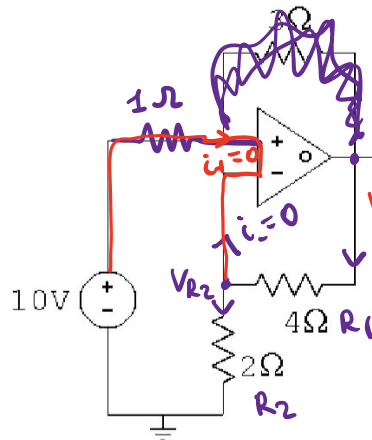


$$V_o = V_{R1} + V_{R2} = i_{R1} \cdot R_1 + 10 = 5 \cdot 4 + 10 = 30V$$

$$V_{R2} = V_- = V_+ = 10V$$

$$i_{R1} = i_{R2} = \frac{V_{R2}}{R_2} = \frac{10}{2} = 5A$$

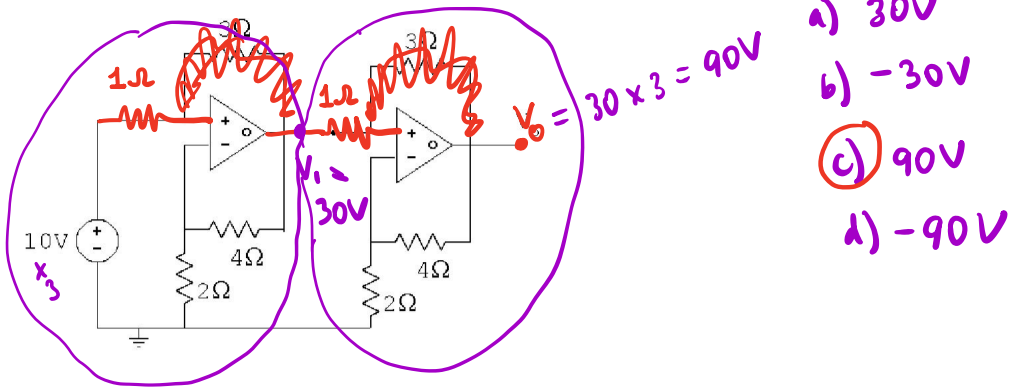- **Example #7:** Obtain V_o in the following circuit assuming the ideal op-amp approximation



- a) 30V
- b) -30V
- c) 90V
- d) -90V