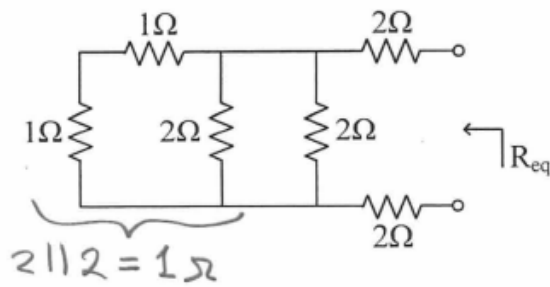


(a) Find the R_{eq} in the following circuit.




$$R_{eq} = 2 + 2 + 2 \parallel 1$$

$$= 4 + \frac{2 \cdot 1}{2+1} = \frac{14}{3} \Omega$$

$$R_{eq} = \underline{\underline{\frac{14}{3} \Omega}}$$

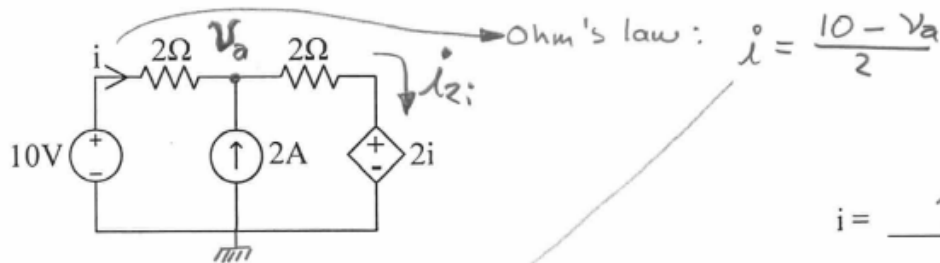(b) In the following circuit, find i and the power absorbed or delivered by $2i$ dependent source.



$$i = \underline{\underline{1 A}}$$

$$P = \underline{\underline{6 W}}$$

KCL @ v_a

$$2 = \frac{v_a - 10}{2} + \frac{v_a - 2i}{2}$$

$$4 = v_a - 10 + v_a - 2 \left(\frac{10 - v_a}{2} \right)$$

$$4 = 2v_a - 10 - 10 + v_a$$

$$24 V = 3v_a$$

$$\boxed{v_a = 8 V}$$

$$\therefore i = \frac{10 - 8}{2} = 1 A$$

Absorbed:

$$P_{2i} = (2i)(i_{2i})$$

$$i_{2i} = \frac{v_a - 2i}{2} = \frac{8 - 2 \left(\frac{10 - 8}{2} \right)}{2} = \frac{8 - 10 + 8}{2} = 3 A$$

$$P_{2i} = (2V)(3A) = 6 W \quad (\text{absorbed})$$


Absorbed ~~X~~ Delivered

(a) (4 pts) A complex number Z is given as

(i) $Z = (1+j)^3$ find $|Z| = 2\sqrt{2}$ $\angle Z = 135^\circ$
 $= (\sqrt{2}e^{j45^\circ})^3 = 2\sqrt{2} \angle 135^\circ$

(ii) $Z = (1-j)e^{-j\pi/4}$ find $|Z| = \sqrt{2}$ $\angle Z = -90^\circ$
 $= \sqrt{2}e^{-j45^\circ} \cdot e^{-j45^\circ} = \sqrt{2} \angle -90^\circ$

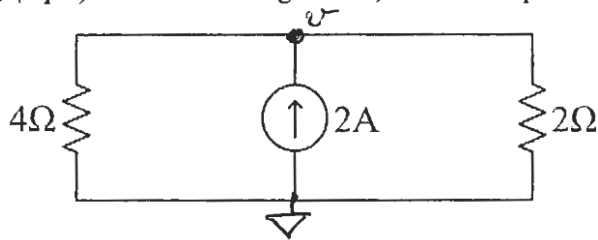(d) (5 pts) In the following circuit, how much power is supplied by 2A source.




$$\frac{v}{4\Omega} + \frac{v}{2\Omega} = 2A$$

$$\frac{3}{4}v = 2A \Rightarrow v = \frac{8}{3}V$$


$$P(\text{supplied}) = (2A)(v) = \frac{16}{3}W$$

$$P = \underline{\underline{\frac{16}{3}W}}$$

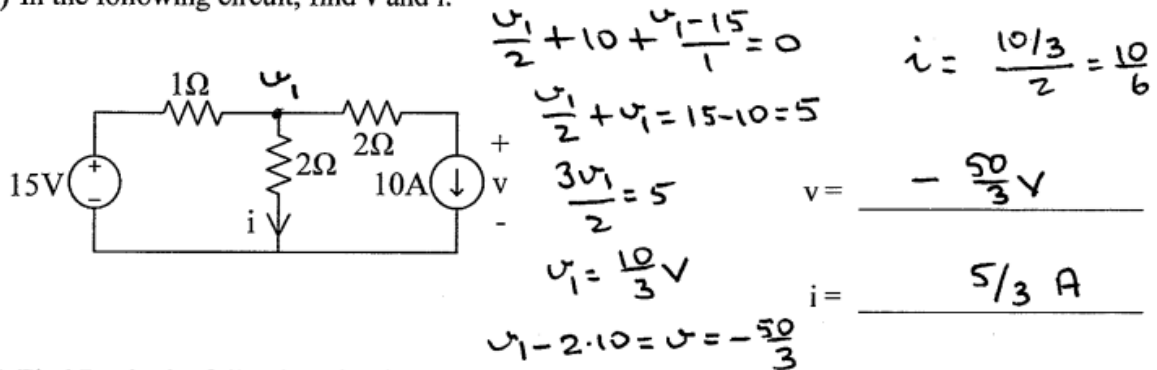
(a) In the following circuit, find v and i .



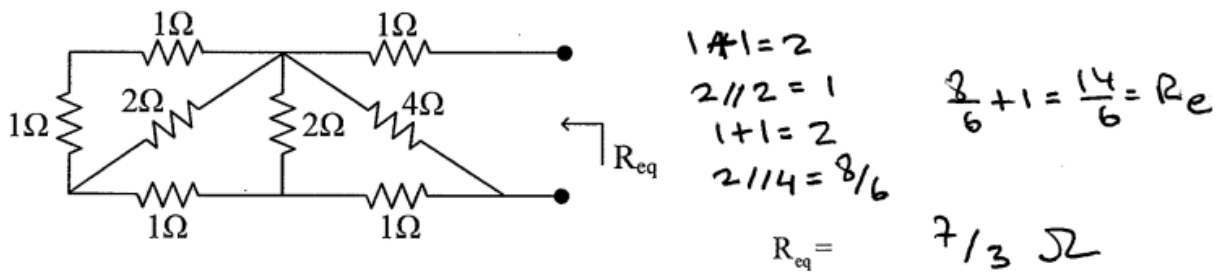
(b) Find R_{eq} in the following circuit.



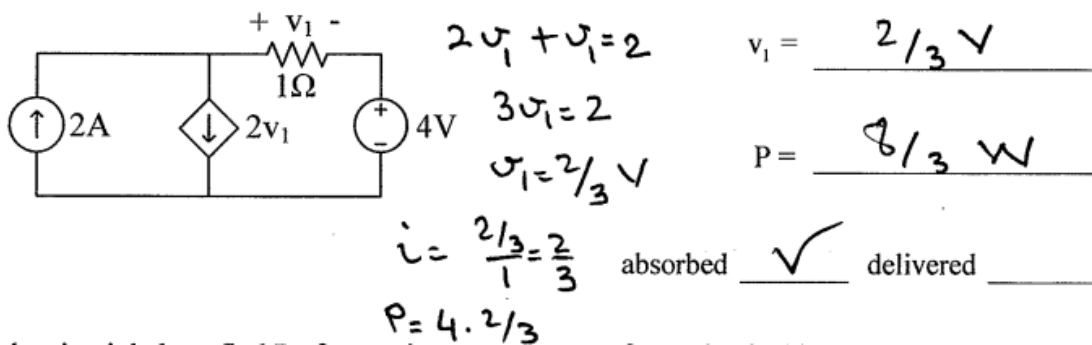(c) For the circuit below, find v_1 and the power, absorbed or delivered by 4V source.



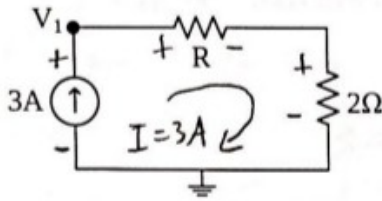- (a) Consider the circuit below. Determine the value of the resistance R and of the node voltage V_1 if the absorbed power by that resistor R is $3W$.




$$P_R = R I^2 = R (3)^2 = 9R = 3 \Rightarrow R = \frac{3}{9} = \frac{1}{3}$$

$$\begin{aligned} \text{KVL: } V_1 &= V_R + V_{2\Omega} = RI + 2I = (R+2)I \\ &= (R+2)3 = \left(\frac{1}{3}+2\right)3 = 7 \end{aligned}$$

$$R = \frac{1}{3} \Omega$$

$$V_1 = 7 \text{ V}$$

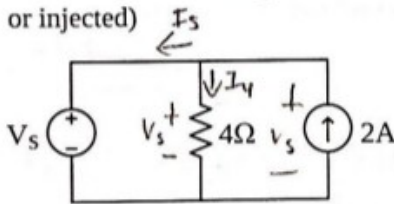- (b) Consider the circuit below. Determine the value of V_s and the absorbed power at the voltage source if the absorbed power at the current source is $6W$. (indicate if this power is absorbed or injected)



$$\begin{aligned} P_{2A} &= VI = V_s (-2) = -2V_s = 6 \Rightarrow V_s = -\frac{6}{2} \\ &= -3 \end{aligned}$$

because non
SAS \rightarrow

$$\text{need } I_s \text{ for } P_s = V_s I_s$$

$$\begin{aligned} \text{KCL: } 2 &= I_s + I_4 = I_s + \frac{V_s}{4} \\ \Rightarrow I_s &= 2 - \frac{V_s}{4} = 2 - \frac{(-3)}{4} = \frac{8+3}{4} = \frac{11}{4} \end{aligned}$$

$$V_s = -3 \text{ V}$$

$$P_s = -33/4 \text{ W}$$

$$\Rightarrow P_s = V_s I_s = -3 \left(\frac{11}{4}\right) = -\frac{33}{4}$$

☐ absorbed ☒ injected because < 0

- (c) Determine the magnitude and phase of the complex number $Z = 2 + j6 + (1 + j)^6$.

$$1+j = \sqrt{1^2+1^2} e^{j \tan^{-1}(1)} = \sqrt{2} e^{j \frac{\pi}{4}}$$

$$\Rightarrow Z = 2 + j6 + (\sqrt{2} e^{j \pi/4})^6 = 2 + j6 + 2^3 e^{j \frac{6\pi}{4}} \quad |Z| = 2\sqrt{2}$$

$$= 2 + j6 + 8(-j) = 2 + j6 + 8(-j)$$

$$= 2 - 2j = \sqrt{2^2 + (-2)^2} e^{j \tan^{-1}(-2/2)} = 2\sqrt{2} e^{-j \pi/4} \quad \angle Z = -\pi/4 \text{ rad}$$

