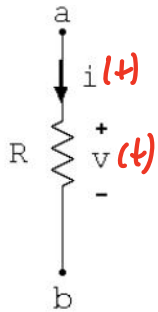


- LTIC circuits

- How to analyze circuits in the s-domain?

- Consider a resistor:




$$v(t) = R \cdot i(t)$$

↓ \mathcal{L}

$$\hat{V} = R \cdot \hat{I}$$

• LTIC circuits-cont


- Consider an inductor:

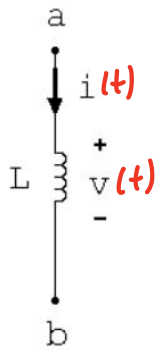

$$v(t) = L \frac{di}{dt}$$


$\downarrow \mathcal{L}$
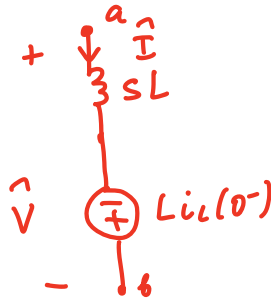
$$\hat{V} = L(s\hat{I} - i_L(0^-)) = \underbrace{(L \cdot s) \cdot \hat{I}}_{\text{" } z\text{-}s\text{-domain impedance}} - \underbrace{L i_L(0^-)}$$



• LTIC circuits-cont

- Consider a capacitor:

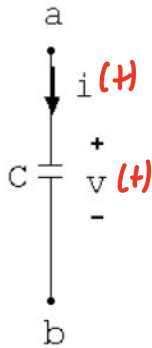


$$i(t) = C \frac{dv}{dt}$$

↓ \mathcal{L}

$$\hat{I} = C (s\hat{V} - v_c(0^-)) = \underbrace{Cs\hat{V}}_{\hat{V}/Z} - C v_c(0^-)$$

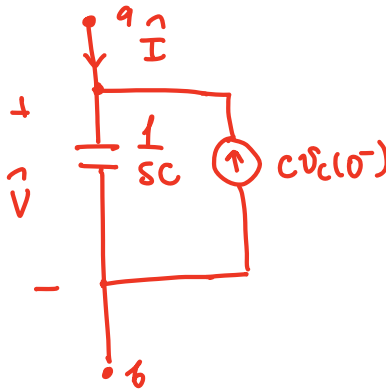
$$\frac{\hat{V}}{Z} \Rightarrow Z = \frac{1}{sC}$$



$$Z = \begin{cases} R & \text{resistor} \\ sL & \text{inductor} \\ \frac{1}{sC} & \text{capacitor} \end{cases}$$

• LTIC circuits in the s-domain - Example # 19

- Consider the following LTIC circuit

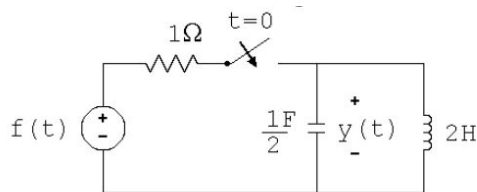


where

- $f(t) = e^{3t}V$
- $v_c(0^-) = 1V$
- $i_L(0^-) = 0A$


- ✓ • Determine the s-domain equivalent circuit for $t > 0$.
- ✓ • Determine $\hat{H}(s)$ and $h(t)$, as well as if the system is BIBO stable.
- ✓ • Determine the characteristic poles and characteristic modes of the system.

• LTIC circuits in the s-domain - Example # 19-cont


- Consider the following LTIC circuit

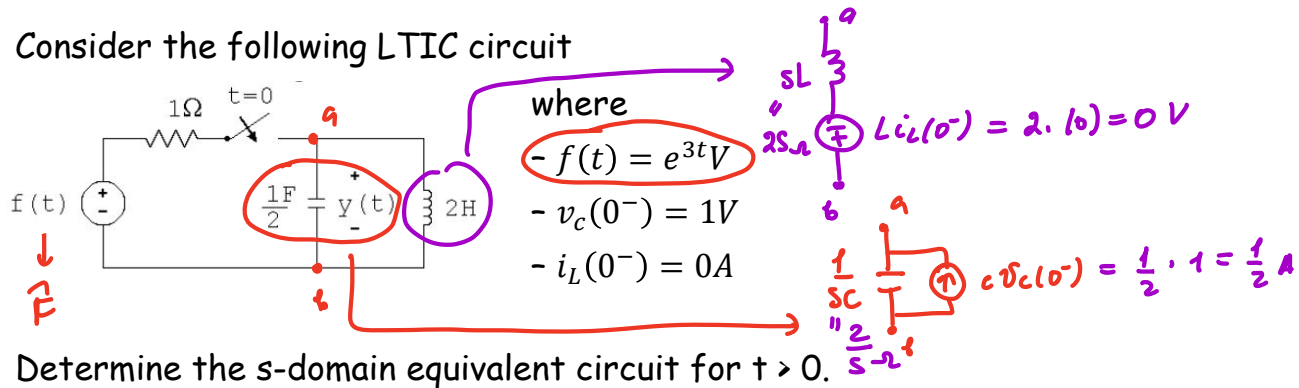

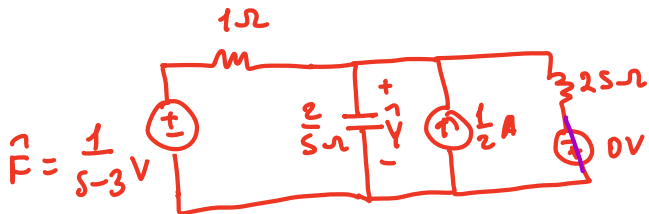
- Determine the s-domain equivalent circuit for $t > 0$.



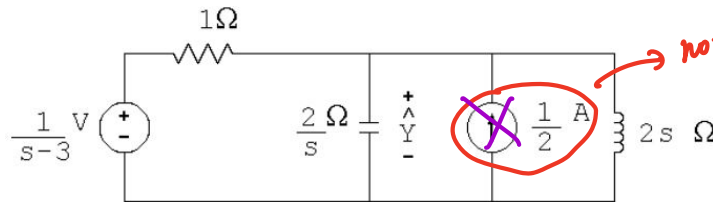• LTIC circuits in the s-domain - Example # 19-cont



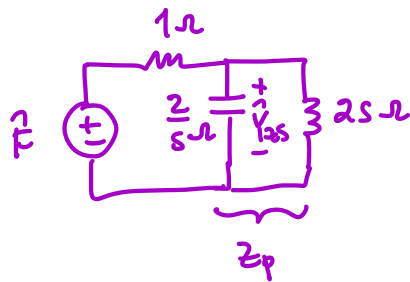- Determine $\hat{H}(s)$, as well as if the system is BIBO stable.



$$= \hat{F} \left(\frac{\frac{2s}{s^2+1}}{\frac{2s}{s^2+1} + 1} \right)$$

Solve for \hat{Y}_{2s} :

Voltage division:


$$\hat{Y}_{2s} = \hat{F} \left(\frac{\hat{Z}_p}{\hat{Z}_p + 1} \right) =$$

$$\hat{F} \left(\frac{2s}{(s+1)^2} \right)$$

\hat{H} poles @ $s = -1, -1$

$$\hat{F} \rightarrow \boxed{\hat{H}} \rightarrow \hat{Y}_{2s} = \hat{F} \cdot \hat{H}$$
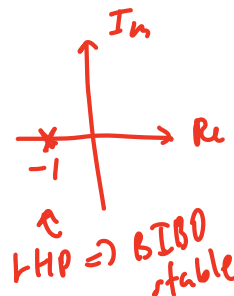
$$\hat{Z}_p = \frac{\frac{2}{s}(2s)}{\frac{2}{s} + 2s} = \frac{2s}{s^2+1}$$



• LTIC circuits in the s-domain - Example # 19-cont $t e^{pt} u(t) \leftrightarrow \frac{1}{(s-p)^2}$

$$\hat{H}(s) = \frac{2s}{(s+1)^2} = \frac{A_1}{s+1} + \frac{A_2}{(s+1)^2}$$

- Determine the characteristic poles and characteristic modes of the system.

$$\hat{y} = \hat{E} \cdot \hat{H} + \frac{\text{I.C.}}{\text{char. polyn.}}$$

characteristic poles: $-1, -1$

characteristic modes: $e^{-t}, t e^{-t}$

1 ind + 1 cap \Rightarrow 2nd order ODE

\Downarrow

ch. polyn. has
a degree of 2

\Downarrow

2 ch. poles

- LTIC circuits in the s-domain - Example # 19-cont

$$\widehat{Y}_{zs}(s) = \frac{2s\hat{F}}{(s+1)^2}$$

- Recall that $f(t) = e^{3t} \rightarrow \hat{F}(s) = \frac{1}{s-3}$


- Determine $y_{zs}(t)$

$$\hat{Y}_{zs} = \frac{2s}{(s+1)^2} \cdot \frac{1}{(s-3)} = \frac{A_0}{(s-3)} + \frac{A_1}{s+1} + \frac{A_2}{(s+1)^2} = \frac{\frac{6}{16}}{s-3} + \frac{-\frac{6}{16}}{s+1} + \frac{\frac{1}{2}}{(s+1)^2}$$

$$\downarrow \mathcal{L}^{-1}$$

$$y_{zs}(t) = \frac{3}{8} e^{3t} u(t) - \frac{3}{8} e^{-t} u(t) + \frac{1}{2} t e^{-t} u(t) \quad \checkmark$$

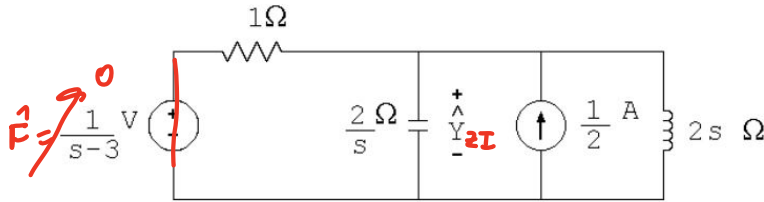- LTIC circuits in the s-domain - Example # 19-cont



- Determine $y_{zI}(t)$

$$\frac{1}{z_p} = \frac{1}{1} + \frac{1}{\frac{2}{s}} + \frac{1}{2s} \Rightarrow z_p = \frac{2s}{(s+1)^2}$$

$$\hat{y}_{zI} = z_p \cdot \frac{1}{2} = \frac{s}{(s+1)^2}$$

$$y_{zI}(t) = e^{-t} u(t) - t e^{-t} u(t) \quad V$$

• s-domain analysis of LTIC systems - Example # 19-cont

- Recall that

$$y_{zs}(t) = -\frac{3}{8}e^{-t}u(t) + \frac{1}{2}te^{-t}u(t) + \frac{3}{8}e^{3t}u(t)$$

$$y_{zi}(t) = (1-t)e^{-t}u(t)$$

- Determine $y(t) = y_{zs}(t) + y_{zi}(t) = \frac{5}{8}e^{-t}u(t) - \frac{1}{2}te^{-t}u(t) + \frac{3}{8}e^{3t}u(t) \checkmark$