
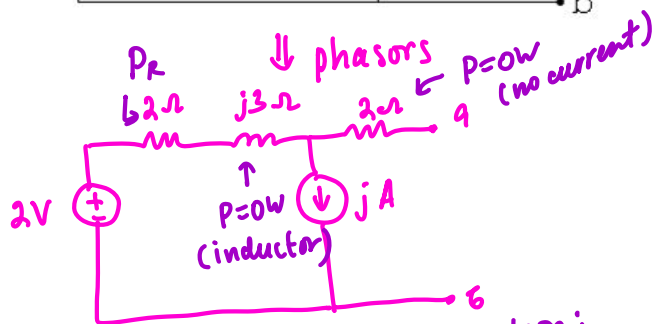

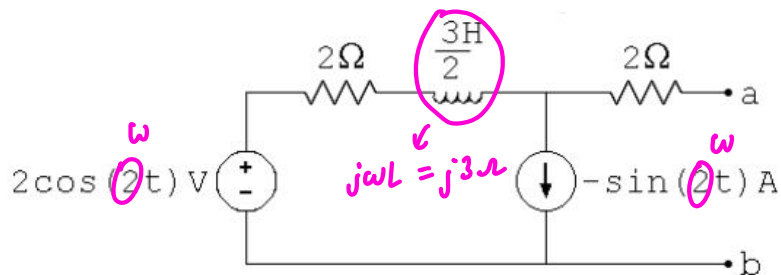
## • Example #9

- Determine the average absorbed power in each element:



By energy conservation:  
 $\sum P = 0$

$$P_{in} = -1W$$

$$p = \frac{1}{2} \operatorname{Re} \{ V I^* \}$$

$$P_R = \frac{1}{2} R |I|^2$$

$$I \cdot I^* = |I|^2$$

$$= \cos(2t - \frac{\pi}{2} + \pi)$$

$$\downarrow e^{j\pi/2} = jA$$


$$P_R = \frac{1}{2} R |I|^2 = \frac{1}{2} \cdot R |j|^2 = \frac{1}{2} \cdot R = 1W$$

$$P_{2V} = \frac{1}{2} \operatorname{Re} \{ V I^* \} = \frac{1}{2} \operatorname{Re} \{ 2 \cdot (-j)^* \} = \frac{1}{2} \operatorname{Re} \{ 2j \} = 0W$$

$$\text{get magnitude } 0 + j \rightarrow \sqrt{0^2 + 1^2} = 1$$

- Available power

For  $R_T > 0$

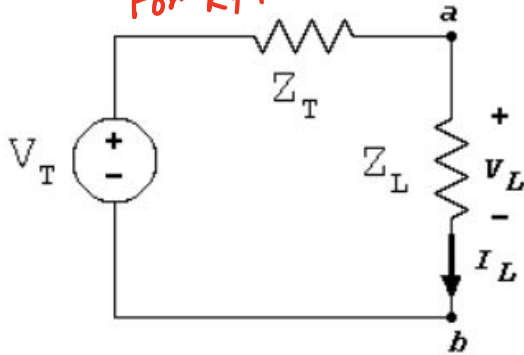

$$Z_T = R_T + jX_T$$

$$Z_L = R_L + jX_L$$

$$P_a = \frac{|V_T|^2}{8R_T} = \left( \frac{1}{2} \right) \frac{|V_T|^2}{4R_T}$$

↑ from phasors
↑ only real part of  $Z_T$

$$P_L = \frac{1}{2} \operatorname{Re} \{ V_L \cdot I_L^* \} = \frac{1}{2} \operatorname{Re} \left\{ \frac{V_T Z_L}{(Z_T + Z_L)} \cdot \frac{V_T^*}{(Z_T + Z_L)^*} \right\} \quad \text{①}$$

$$I_L = \frac{V_L}{Z_L} = \frac{V_T}{Z_T + Z_L} \quad \text{②} \quad \frac{1}{2} \operatorname{Re} \left\{ \frac{|V_T|^2 \cdot Z_L}{|Z_L + Z_T|^2} \right\} =$$

$$V_L = V_T \left( \frac{Z_L}{Z_T + Z_L} \right)$$

$$= \frac{1}{2} \frac{|V_T|^2 \cdot R_L}{|Z_L + Z_T|^2} =$$

$$= \frac{1}{2} \frac{|V_T|^2 \cdot R_L}{|(R_L + R_T) + j(X_L + X_T)|^2}$$


$$Z_L = R_T - jX_T = Z_T^*$$

matched load


$$\left\{ \begin{array}{l} X_L = -X_T \\ R_L = R_T \end{array} \right.$$
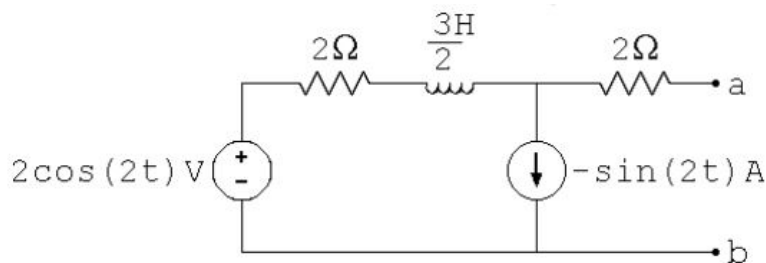
## • Example #9-cont

- Determine the available average absorbed power:



↓ phasors

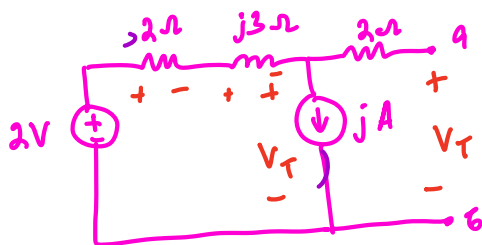

$$P_a = \frac{1}{2} \cdot \frac{|V_T|^2}{4R_T} = \frac{1}{8} \frac{(\sqrt{5^2 + (-2)^2})^2}{4} = \frac{29}{32} \text{ W only if}$$


$$Z_L = Z_T^* = 4 - j3\Omega$$

Get  $V_T$ :

$$\text{KVL: } -2 + 2j + j(j3) + V_T = 0$$


$$V_T = 5 - j2 \text{ V}$$

Get  $Z_T$ :

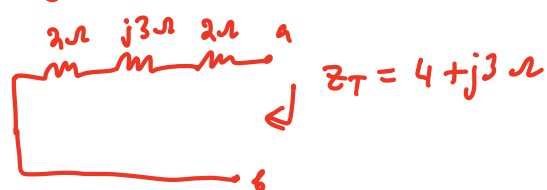
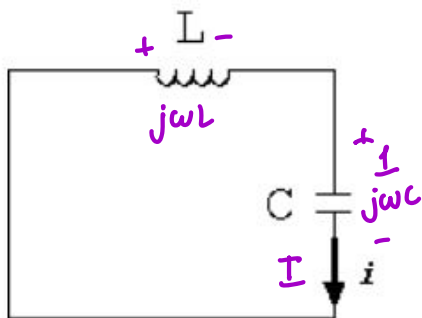
## • Resonance

- Recall the circuit below with  $v_C(0^-) = 1V$ ,  $i_L(0^-) = 0A$  and  $v_C(t) = A \cos(t + \theta)$



$$KVL: V_L + V_C = 0$$

$$j\omega L \cdot I + \frac{1}{j\omega C} \cdot I = 0$$

$$I \left( j\omega L - \frac{j}{\omega C} \right) = 0$$

↖ can be satisfied by any  $I$   
as long as

$$j\omega L - \frac{j}{\omega C} = 0$$

$$\omega L = \frac{1}{\omega C}$$


$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

resonant  
frequency

- Resonance:** possible existence of steady-state co-sinusoidal oscillations in a source-free circuit.

- Resonance-cont

- What if we add a source?

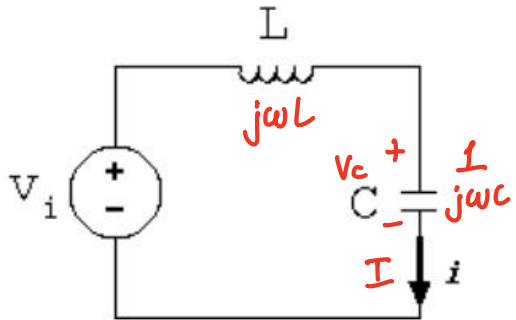


$$V_c = V_i \left( \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + j\omega L} \right) = \frac{V_i}{-\omega^2 LC + 1} \Rightarrow V_c \rightarrow \infty$$

if  $\omega = \frac{1}{\sqrt{LC}}$  (resonance frequency) where the denominator becomes zero.

## • Resonance-cont

- What if we add a resistor too?

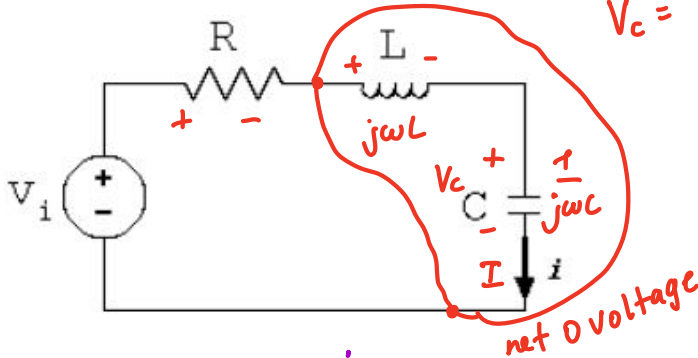

$$V_c = V_i \frac{\frac{1}{j\omega C}}{\left(\frac{1}{j\omega C} + j\omega L + R\right)} = \frac{V_i}{1 - \omega^2 LC + j\omega RC}$$

0 if  $\omega = \frac{1}{\sqrt{LC}}$

$$Z_s = R + j\omega L - \frac{j}{\omega C}$$

0 if  $\omega = \frac{1}{\sqrt{LC}}$

$L$  and  $C$  act like a short,  
but they still have voltage, just  
opposite in signs to each other  
 $\Rightarrow$  max current achieved!