
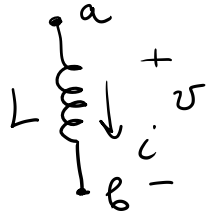


• Differentiators and integrators

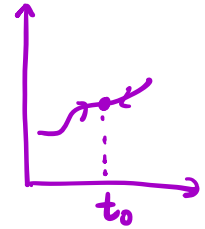

$v = L \frac{di}{dt}$ ← current in inductor is continuous! for all practical sources
 $i_L(0^-) = i_L(0^+) = i_L(0)$
 can jump If we want to know $i \Rightarrow$

$$\int_{-\infty}^t v(s) ds = Li(t) \Rightarrow i(t) = \frac{1}{L} \int_{-\infty}^t v(s) ds =$$




$$i_L(t_0^-) = i_L(t_0^+) = i_L(t_0)$$

$$= \frac{1}{L} \int_{-\infty}^0 v(s) ds + \frac{1}{L} \int_0^t v(s) ds = i(t)$$

i_0
 initial state

- Differentiators and integrators-cont

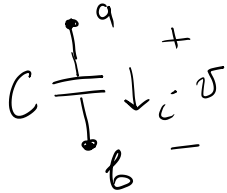

$\dot{v} = C \frac{dv}{dt}$ → voltage in a capacitor is continuous! for all practical sources


can jump $\int_{-\infty}^t i(s) ds = C v(t)$

$v(0^-) = v(0) = v(0^+)$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(s) ds =$$

$$= \underbrace{\frac{1}{C} \int_{-\infty}^0 i(s) ds}_{v_0 \text{ initial state}} + \frac{1}{C} \int_0^t i(s) ds = v(t)$$

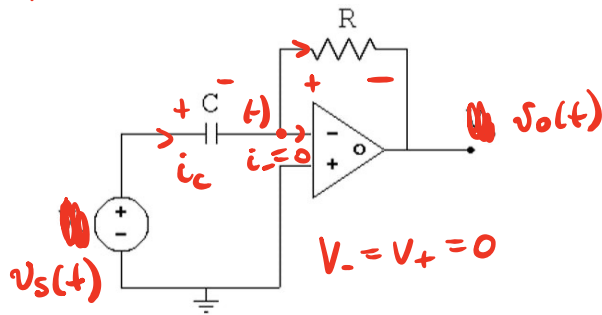- Example #8: Obtain V_o in the following circuit assuming the ideal op-amp approximation



KCL @ $(-)$:

$$i_c = \frac{V_- - V_o}{R}$$

$$i_c = C \frac{dv_c}{dt}$$


$$v_o(t) = -R i_c(t) = -R \left(C \frac{dv_c}{dt} \right) =$$

$$= -RC \frac{d}{dt} (v_s - \underbrace{V_-}_0)$$

$$v_o(t) = -RC \frac{dv_s}{dt}$$

Voltage differentiator

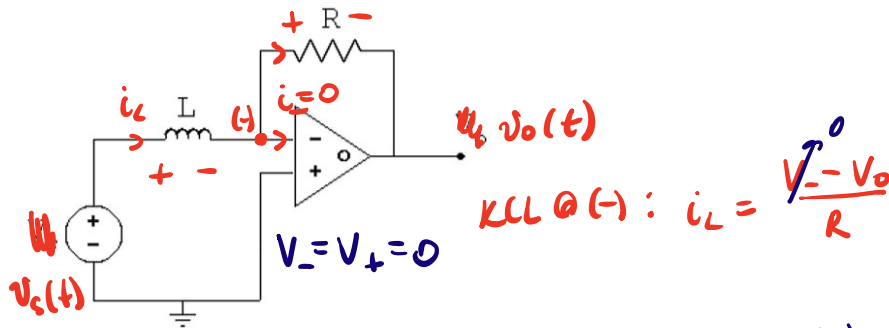- **Example #9:** Obtain V_o in the following circuit assuming the ideal op-amp approximation



$$v_L = L \frac{di_L}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(x) dx$$

$$\begin{aligned} v_o(t) &= -R i_L(t) = \\ &= -R \left(\frac{1}{L} \int_{-\infty}^t v_L(x) dx \right) = \\ &= -\frac{R}{L} \int_{-\infty}^t (v_s - \cancel{V_-}) dx \end{aligned}$$

$$v_o(t) = -\frac{R}{L} \int_{-\infty}^t v_s(x) dx$$

← integrator

- Linearity, time-invariance and **LTI** systems

- Recall from previous example: \downarrow linear and time-invariant

$$v_{out}(t) = -\frac{R}{L} \int_{-\infty}^t v_s(x) dx =$$



$v_s(t)$ - input

$v_{out}(t)$ - output

$$= -\frac{R}{L} \int_{-\infty}^0 v_s(x) dx - \frac{R}{L} \int_0^t v_s(x) dx =$$

$$= v_0 - \frac{R}{L} \int_0^t v_s(x) dx =$$

$$= v_{zi}(t) + v_{zs}(t)$$

zero-input
response

(when $v_s(t) = 0$)
no input

zero-state
response

(when $v_0 = 0$)
no initial
state

- Linearity, time-invariance and LTI systems-cont
 → no initial state

In a **zero-state** linear system, a weighted sum of inputs produces a similarly weighted sum of corresponding **zero-state** outputs, consistent with the superposition principle. So,

if

$$f_1(t) \rightarrow \boxed{\text{Zero-state linear}} \rightarrow y_{zs,1}(t)$$

$$f_2(t) \rightarrow \boxed{\text{Zero-state linear}} \rightarrow y_{zs,2}(t)$$

then

$$f_3(t) = k_1 f_1(t) + k_2 f_2(t) \rightarrow \boxed{\text{Zero-state linear}} \rightarrow y_{zs,3}(t) = k_1 y_{zs,1}(t) + k_2 y_{zs,2}(t)$$

- Linearity, time-invariance and LTI systems-cont

- Similarly, in a *zero-input* linear system, a weighted sum of initial states produces a similarly weighted sum of corresponding *zero-input* outputs, consistent with the superposition principle.
→ no input
- A system is *linear*, if it is both *zero-state* linear and *zero-input* linear and the output is the sum of the *zero-state* and the *zero-input* responses.

• Example #10: Linearity

- Consider a system with input $f(t)$, initial state $y(0) = y_0$ and input-output rule given by

$$y(t) = y_0 e^{-t} - \int_0^t f(x) dx$$

- Determine if the system is linear or not

zero-state linear \Rightarrow

$$y_0 = 0 \Rightarrow y_{zs}(t) = - \int_0^t f(x) dx$$

yes linear + zero-input \Rightarrow yes linear \Rightarrow linear $\ddot{\smile}$

$$f_1(t) \rightarrow \boxed{} \rightarrow y_1(t) = - \int_0^t f_1(x) dx$$

$$f_2(t) \rightarrow \boxed{} \rightarrow y_2(t) = - \int_0^t f_2(x) dx$$

$$f_3(t) \rightarrow \boxed{} \rightarrow y_3(t) \stackrel{?}{=} k_1 y_1 + k_2 y_2 \quad (*)$$

Same \Rightarrow z-s linear $\ddot{\smile}$

$$\begin{aligned} & \text{" } - \int_0^t f_3(x) dx = - \int_0^t (k_1 f_1 + k_2 f_2) dx = \\ & = k_1 \underbrace{\left(- \int_0^t f_1 dx \right)}_{y_1} + k_2 \underbrace{\left(- \int_0^t f_2 dx \right)}_{y_2} \quad (4) \end{aligned}$$

$$k_1 f_1 + k_2 f_2$$

• Example #10: Linearity-cont

- Consider a system with input $f(t)$, initial state $y(0) = y_0$ and input-output rule given by

$$y(t) = y_0 e^{-t} - \int_0^t f(x) dx$$

- Determine if the system is linear or not

zero-input $\Rightarrow f(t) = 0 \Rightarrow y_{ZI}(t) = y_0 e^{-t}$

$y_0 \rightarrow y_{ZI,0}(t) = y_0 e^{-t}$

$y_1 \rightarrow y_{ZI,1}(t) = y_1 e^{-t}$

z-I linear ~

$y_3 = k_1 y_0 + k_2 y_1 \rightarrow y_{ZI,3}(t) \stackrel{?}{=} k_1 y_{ZI,0} + k_2 y_{ZI,1} \quad (*)$

" $y_3 e^{-t} = (k_1 y_0 + k_2 y_1) e^{-t} = k_1 \underbrace{(y_0 e^{-t})}_{y_{ZI,0}} + k_2 \underbrace{(y_1 e^{-t})}_{y_{ZI,1}} \quad (x)$