
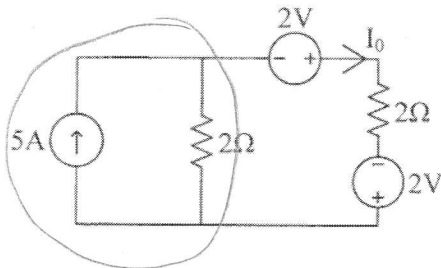


Problem 1 (12 points)

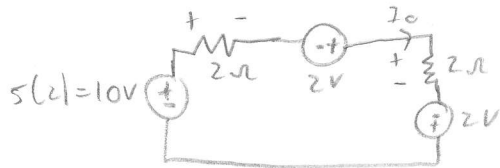(a) In the following circuit find the value of I_0 .



Source transformation




KVL

$$10 + 2 + 2 = 2I_0 + 2I_0$$

$$\Rightarrow I_0 = \frac{10 + 2 + 2}{2 + 2} = \frac{14}{4} = \frac{7}{2} \text{ A}$$

$$I_0 = \frac{7}{2} \text{ A}$$

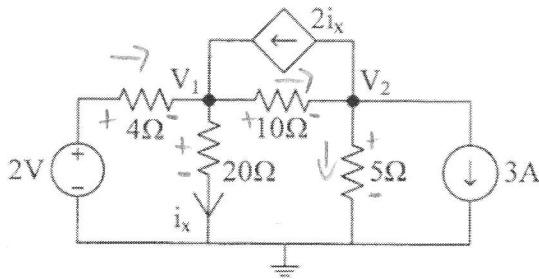(b) In the following circuit, what is the node voltage V_2 .



Node-voltage method

$$\textcircled{1} \quad \frac{2 - V_1}{4} + 2i_x = \frac{V_1 - 0}{20} + \frac{V_1 - V_2}{10}$$

$$\textcircled{2} \quad \frac{V_1 - V_2}{10} = 2i_x + \frac{V_2 - 0}{5} + 3$$

$$i_x = \frac{V_1 - 0}{20}$$

$$\frac{1}{2} = V_1 \left(\frac{1}{20} + \frac{1}{10} + \frac{1}{4} - \frac{2}{20} \right) + V_2 \left(-\frac{1}{10} \right) = V_1 \frac{14 + 5 - 2}{20} - \frac{1}{10} V_2 = \frac{3}{10} V_1 - \frac{1}{10} V_2$$

$$\Rightarrow V_1 = \left(\frac{1}{2} + \frac{1}{10} V_2 \right) \frac{10}{3} = \frac{5 + V_2}{3}$$


$$V_1 \left(\frac{1}{10} - \frac{2}{20} \right) + V_2 \left(-\frac{1}{10} - \frac{1}{5} \right) = 3 = \left(\frac{5 + V_2}{3} \right) \left(\frac{2 - 2}{20} \right) + V_2 \left(\frac{-1 - 2}{10} \right) = -\frac{3}{10} V_2$$

$$\Rightarrow V_2 = 3 \left(-\frac{10}{3} \right) = -10 \text{ V}$$

$$V_2 = -10 \text{ V}$$

Problem 2 (13 points)

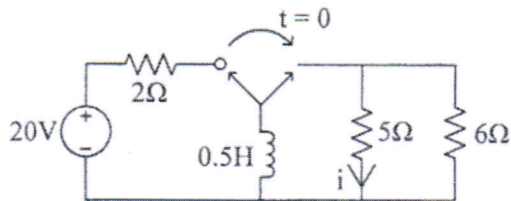(a) The following circuit is at the steady state at $t = 0^-$. Find $i(t)$, $t > 0$.




For $t < 0$ in steady state



$$i_L(0^-) = 0 \text{ A}$$

$$i_L(0^+) = \frac{20}{2} = 10 \text{ A}$$

For $t > 0$

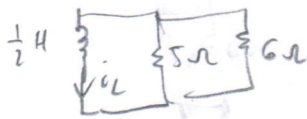

$$i_L(\infty) = 0 = B$$

$$i_L(t) = B + Ae^{-t/\tau} = 0 + Ae^{-t/11} = 10e^{-60t/11}$$

$$\tau = \frac{L}{R_{eq}} = \frac{0.5}{\frac{11}{30}} = \frac{11}{60}$$

$$R_{eq} = 5 \parallel 6 = \frac{5(6)}{5+6} = \frac{30}{11}$$

$$i_L(0^+) = i_L(0^-) = 10 = B + A$$


by continuity of i_L

By current division

$$i = -i_L \frac{6}{6+5} = -\frac{5}{11} i_L$$

$$i(t) = \frac{-60}{11} e^{-60t/11} \text{ A}$$

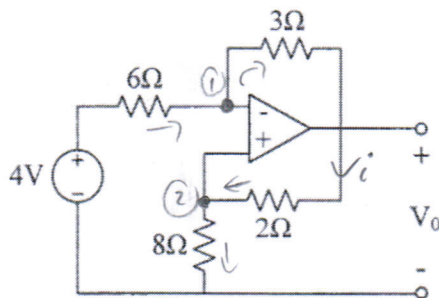(b) In the following ideal op-amp circuit, what is the power absorbed by 2Ω resistor?



$$v_- = v_+$$

KCL @ ①

$$\frac{4 - v_+}{6} = \frac{v_+ - v_o}{3} \Rightarrow v_o = \left[2 + v_+ \left(\frac{-1}{2} - 1 \right) \right] (-1) = -2 + \frac{3}{2} v_+$$

$$v_+ = 8i$$

$$v_o = -2 + \frac{3}{2} 8i = -2 + 12i$$

$$i = \frac{v_o}{8+2} = \frac{v_o}{10} = \frac{1}{10} (-2 + 12i)$$


$$= -\frac{1}{5} + \frac{6}{5} i \Rightarrow i = \frac{-\frac{1}{5}}{1 - \frac{6}{5}} = \frac{-\frac{1}{5}}{-\frac{1}{5}} = 1 \text{ A}$$

$$P_{2\Omega} = Ri^2 = 2(1)^2 = 2 \text{ W}$$

$$P_{2\Omega} = 2 \text{ W}$$

Problem 3 (12 points)

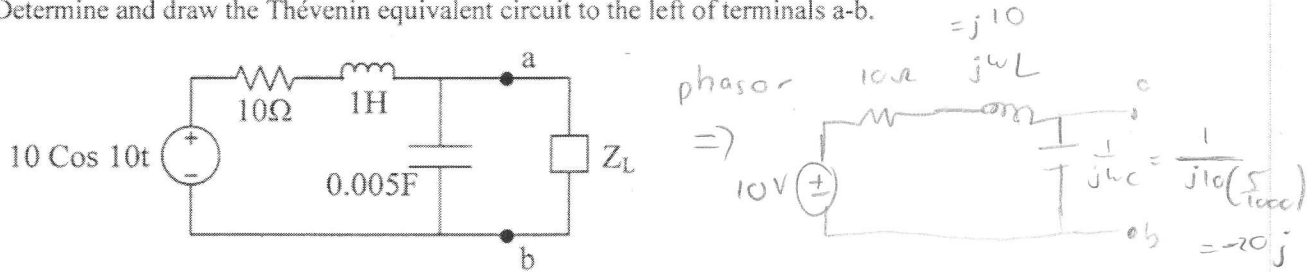(a) Determine and draw the Thévenin equivalent circuit to the left of terminals a-b.



$V_T = \text{open circuit voltage}$


By voltage division: $V_T = 10 \frac{(-20j)}{-20j + 10 + j10} = \frac{-200j}{10 - 10j} = \frac{-20j}{1-j} \text{ V} = V_T$

z_T is equivalent impedance after

$z_T = (10 + j10) \parallel (-20j) = \frac{(10 + j10)(-20j)}{10 + j10 - 20j} = \frac{-200j + 200}{10 - 10j} = \frac{20(1-j)}{10(1-j)} = 20 \Omega$

Handwritten note: "source suppression"

$z_T = 20 \Omega$

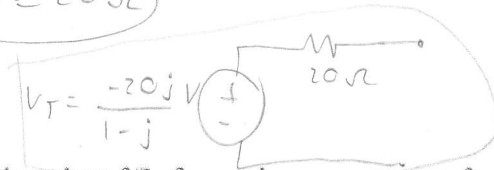

(b) Find the value of Z_L for maximum power transfer to Z_L . And then find the maximum power delivered to Z_L .

For max power $z_L = z_T^* = 20 \Omega$

$P_a = \frac{1}{2} \left| \frac{V_T}{2} \right|^2 \frac{1}{R_T} = \frac{1}{2} \frac{10^2}{1^2 + 1^2} \frac{1}{20} = \frac{100}{80} = \frac{10}{8} = \frac{5}{4} \text{ W}$

$z_L = 20 \Omega$



$P_{\max} = 5/4 \text{ W}$

Problem 4 (13 points)

The periodic input signal $f(t)$ is described by

$$f(t) = 3 + 2 \cos(\underbrace{2t}_{\omega_1}) + \cos(\underbrace{4t}_{\omega_2} - 70^\circ) + 6 \cos(\underbrace{6t}_{\omega_3} + 45^\circ)$$

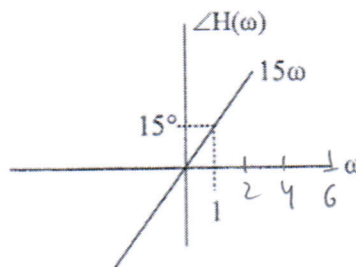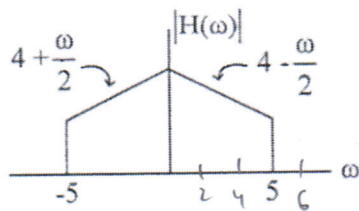Determine the output signal $y(t)$ for which the magnitude and phase of transfer function is given by



$$|H(0)| = 4$$

$$|H(2)| = 4 - \frac{2}{2} = 3$$

$$|H(4)| = 4 - \frac{4}{2} = 2$$

$$|H(6)| = 0$$

$$\angle H(0) = 0$$

$$\angle H(2) = 15(2) = 30$$

$$\angle H(4) = 15(4) = 60$$

$$\angle H(6) = 15(6) = 90$$

2f

$$f(t) = \sum_{n=0}^{\infty} A_n \cos(\omega_n t + \theta_n)$$

then

$$y(t) = \sum_{n=0}^{\infty} A_n |H(\omega_n)| \cos(\omega_n t + \theta_n + \angle H(\omega_n))$$

$$= 3 |H(0)| + 2 |H(2)| \cos(2t + 30^\circ) + |H(4)| \cos(4t - 70^\circ + 60^\circ) + 6 |H(6)| \cos(6t + 45^\circ + 90^\circ)$$

$$y(t) = 12 + 6 \cos(2t + 30^\circ) + 2 \cos(4t - 10^\circ)$$

Problem 5 (12 points)

An LTI system is given by $H(\omega) = \frac{1}{2 + j\omega}$. If the input is $f(t) = e^{2t} u(-t)$, determine the zero-state response $y(t)$ of this system.

$$F(\omega) = \frac{1}{2 - j\omega}$$


$$\Rightarrow Y(\omega) = F(\omega)H(\omega) = \frac{1}{2 - j\omega} \frac{1}{2 + j\omega} = \frac{1}{4 + \omega^2} = \frac{1}{4} \frac{2}{2^2 + \omega^2}$$

$$e^{-2|t|}$$


$$y_{zs}(t) = \frac{1}{4} e^{-2|t|}$$

Problem 6 (13 points)


Consider the following system

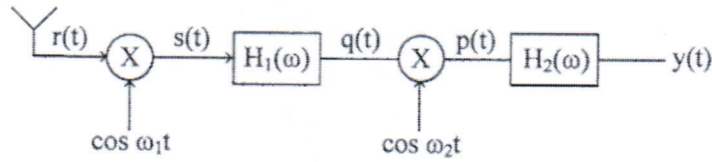

with $\omega_1 = 800$ rad/s

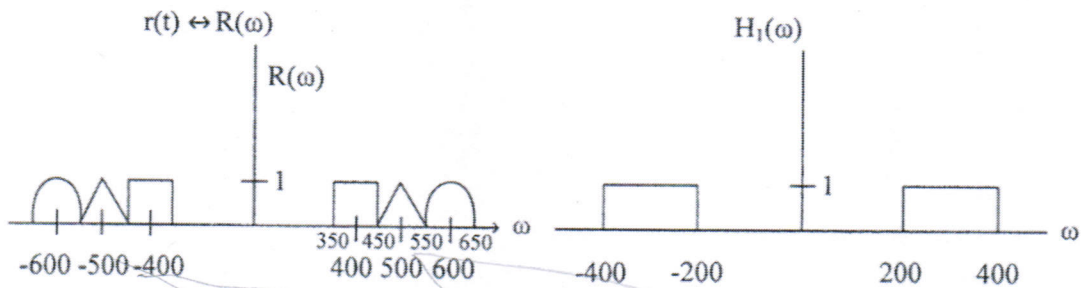


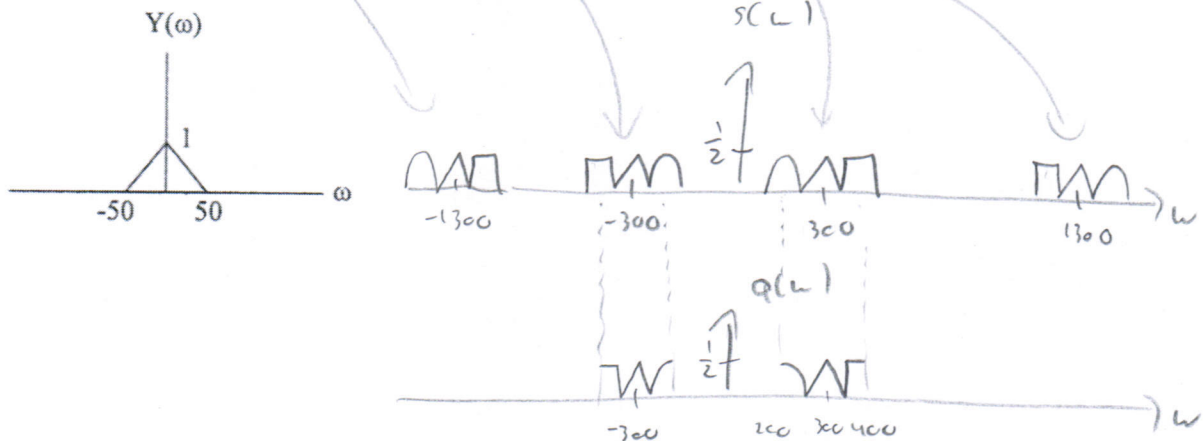Find ω_2 and $H_2(\omega)$ such that the output of the system is



need to move by 300

If $\omega_2 = 300$


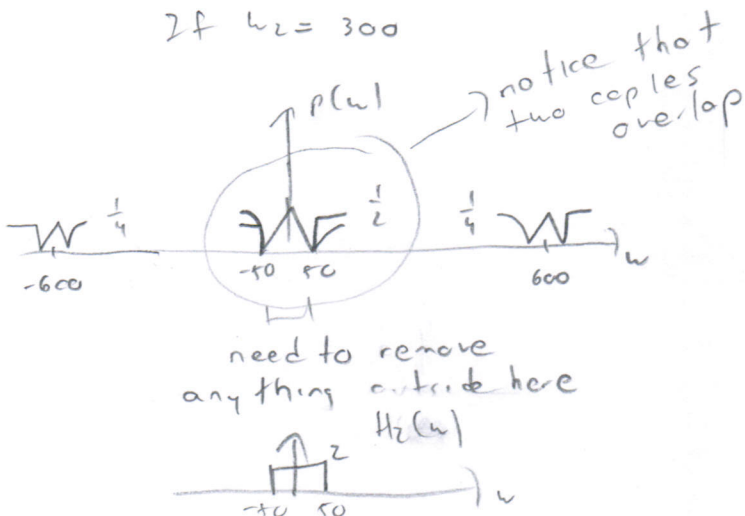


$$\omega_2 = \underline{300 \text{ rad/s}}$$


$$H_2(\omega) = \underline{2 \text{ rect}\left(\frac{\omega}{100}\right)}$$

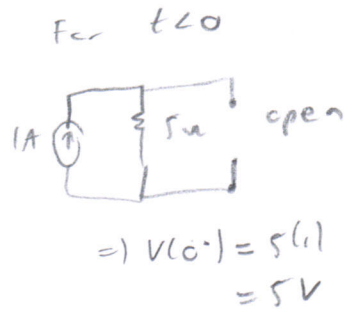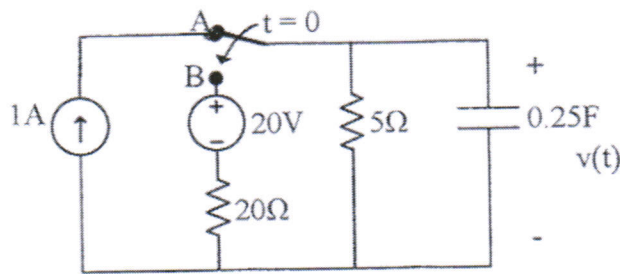Problem 7 (13 points)

In the following circuit, the switch has been in the A position for a long time and the circuit is at the steady state. The switch goes to the B position at time $t = 0$.



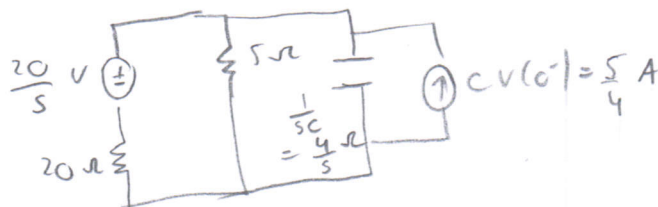(a) Draw the equivalent circuit in the s-domain, $t > 0$.



(b) Obtain $\hat{V}(s)$, $t > 0$.

Superposition


• $\frac{20}{s} V$ only : $5 \parallel \frac{4}{s} = \frac{5(\frac{4}{s})}{5 + \frac{4}{s}} = \frac{20}{5s + 4}$

$\hat{V}(s) = \frac{4 + 5s}{s(5s + 4)}$ ✓

By voltage division

$\hat{V} = \frac{20}{s} \cdot \frac{20}{5s + 4}$

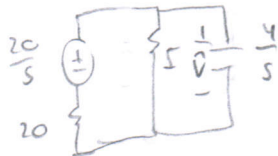$= \frac{(20)^2}{s(5s + 4)(20 + 20(5s + 4))}$
 $= \frac{20}{s(5 + 5s)} = \frac{4}{s(1 + s)}$



• $\frac{5}{4} A$ only : $5 \parallel 20 = \frac{5(20)}{5 + 20} = \frac{100}{25} = 4$

By current division

$\hat{I}_C = \frac{5}{4} \cdot \frac{4}{4 + \frac{4}{s}} = \frac{20s}{4(4s + 4)} = \frac{5s}{4(s + 1)}$



$\hat{V} = \frac{4}{s} \hat{I}_C = \frac{4}{s} \cdot \frac{5s}{4(s + 1)} = \frac{5}{s + 1}$

$\Rightarrow \hat{V} = \text{the terms} : \frac{4}{s(1 + s)} + \frac{5}{s + 1} = \frac{4 + 5s}{s(1 + s)}$

Problem 7 (continued)

(c) Obtain $v(t)$, for $t > 0s$.

By PFE


$$\hat{V} = \frac{4+s}{s(s+1)} = \frac{A_0}{s} + \frac{A_1}{s+1}$$
$$= \frac{4+s(0)}{(0+1)} + \frac{4+s(-1)}{-1} = \frac{4}{s} + \frac{1}{s+1}$$

$\mathcal{J}^{-1} \downarrow$

$$4u(t) + e^{-t}u(t)$$

$$v(t) = 4u(t) + e^{-t}u(t) \text{ V}$$

(d) Plot $v(t)$ for $t > -1s$.

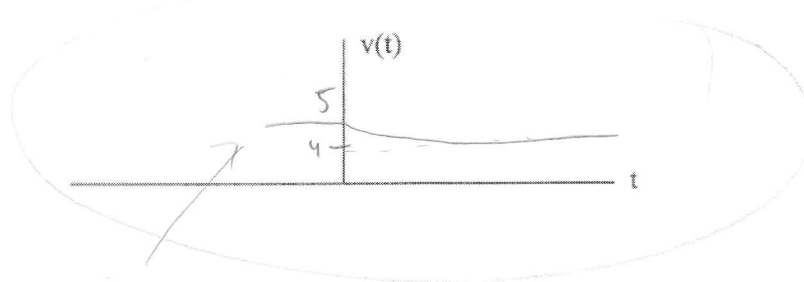

Notice that we had initial condition of 5V in steady state, which the inverse Laplace could not tell us (it only tells us what happens for $t > 0$)

Problem 8 (12 points)

(a) Consider the following differential equation describing an LTI system.

i) If $f(t) = u(t)$ and $y(0^-) = 1$, find $y_{zi}(t)$, $y_{zs}(t)$ and $y(t)$.

$$\frac{dy}{dt} + 3y(t) = f(t) \Rightarrow sY - y(0^-) + 3Y = F$$

$$\Rightarrow Y = \frac{F + y(0^-)}{s+3}$$

$$y_{zi} = \frac{y(0^-)}{s+3} = \frac{1}{s+3} \xrightarrow{\mathcal{I}^{-1}} e^{-3t} u(t)$$

$$y_{zs} = \frac{F}{s+3} = \frac{1}{s(s+3)} = \frac{A_0}{s} + \frac{A_1}{s+3}$$

$$= \frac{\frac{1}{0+3}}{s} + \frac{\frac{-1}{3}}{s+3} = \frac{1}{3s} - \frac{1}{3(s+3)}$$

$$\xrightarrow{\mathcal{I}^{-1}} \frac{1}{3} u(t) - \frac{1}{3} e^{-3t} u(t)$$

ii) Find the impulse response $h(t)$ of this system.

$$H(s) = \frac{y_{zs}(s)}{F(s)} = \frac{1}{s+3} \xrightarrow{\mathcal{I}^{-1}} e^{-3t} u(t)$$

$$y_{zi}(t) = \frac{e^{-3t} u(t)}{s+3}$$


$$y_{zs}(t) = \frac{\frac{1}{3} u(t) - \frac{1}{3} e^{-3t} u(t)}{s+3}$$

$$y(t) = \frac{\frac{1}{3} u(t) + \frac{2}{3} e^{-3t} u(t)}{s+3}$$

$$\xrightarrow{\mathcal{I}^{-1}} y_{zi} + y_{zs}$$

$$h(t) = \frac{e^{-3t} u(t)}{s+3}$$

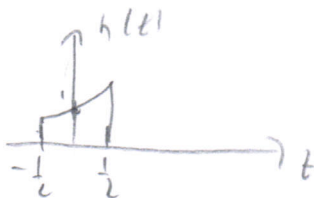(b) If impulse response $h(t)$ is given as $h(t) = e^{3t} \text{rect}(t)$ for a system, is this system BIBO stable or not? Causal or not? (You have to justify your answer, no justification will not get any credit)



BIBO Stable ☒ yes ☐ no

Causal ☐ yes ☒ no


$$\int_{-\infty}^{\infty} |h(t)| dt < \infty \checkmark \Rightarrow \text{BIBO}$$

$h(t) \neq 0$ for some $t < 0 \Rightarrow$ not causal

Problem 3 (12 points)


For $f(t) = 3 + 2\cos(t) + \sin(2t)$

and the following circuit

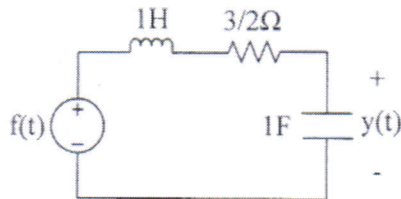

by voltage division
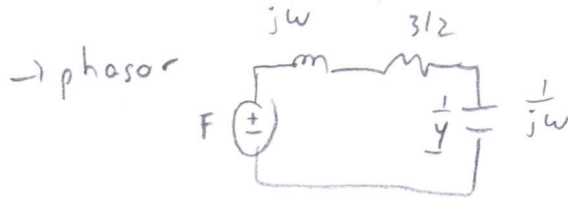
$$\Rightarrow Y = F \frac{\frac{1}{j\omega}}{\frac{1}{j\omega} + j\omega + \frac{3}{2}} = F \frac{2}{2(-\omega^2 + 1) + 3j\omega} = H(\omega)$$



(a) Is $f(t)$ periodic? If so, what is the period?

Yes $\left. \begin{matrix} \omega_1 = 0 \\ \omega_2 = 1 \\ \omega_3 = 2 \end{matrix} \right\} \text{ratios are rational numbers}$

$$\omega_0 = 1 \text{ rad/s} \\ \Rightarrow T = \frac{2\pi}{\omega_0} = 2\pi \text{ s}$$

Periodic: ☒ YES ☐ NO

$T = \underline{2\pi} \text{ sec}$

(b) What are the trigonometric fourier series coefficients of $f(t)$?

$$f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} (a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t))$$

$$\Rightarrow a_0 = 6$$

$$a_1 = 2$$

$$b_2 = 1$$

all others are zero

(c) Find $y(t)$, the output of the circuit above, for the given $f(t)$.

$$H(0) = 1$$

$$H(1) = \frac{2}{3j} = \frac{2}{3} e^{-j\pi/2}$$

$$H(2) = \frac{2}{-6 + 6j} = \frac{2}{6\sqrt{2}} e^{-j3\pi/4} = \frac{1}{3\sqrt{2}} e^{-j3\pi/4}$$

$$f(t) = 3 + 2\cos(t) + \sin(2t)$$


↓

$$y(t) = 3H(0) + 2|H(1)|\cos(t + \angle H(1)) + |H(2)|\sin(2t + \angle H(2)) \\ = 3 + \frac{2}{3}\cos(t - \pi/2) + \frac{1}{3\sqrt{2}}\sin(2t - 3\pi/4)$$

$$y(t) = 3 + \frac{2}{3}\cos(t - \frac{\pi}{2}) + \frac{1}{3\sqrt{2}}\sin(2t - \frac{3\pi}{4}) \quad \checkmark$$

Problem 1 (12 points)

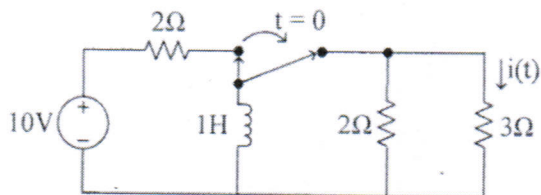(a) The following circuit is at the steady state at $t = 0^-$. Find $i(t)$, $t > 0$.



For $t < 0$ in steady state

$$10V \text{ source, } 2\Omega \text{ resistor, } V_{iL} = \frac{10}{2} = 5A = i_L(0^-)$$

For $t > 0$

$$i_L(t) = 9 + Ae^{-t/\tau}$$

$$\tau = \frac{L}{R_{eq}} = \frac{1}{6/5} = \frac{5}{6}$$

$$R_{eq} = 2 \parallel 3 = \frac{2(3)}{2+3} = \frac{6}{5}$$

$$i_L(\infty) = 9 = 0$$

$$i_L(0^+) = i_L(0^-) = 5 = 9 + A$$


$$\Rightarrow i_L(t) = 5e^{-6t/5}$$

By current division

$$i = -i_L \frac{2}{2+3} = -\frac{2}{5} e^{-6t/5}$$

$$i(t) = \frac{-2e^{-6t/5}}{5} A$$

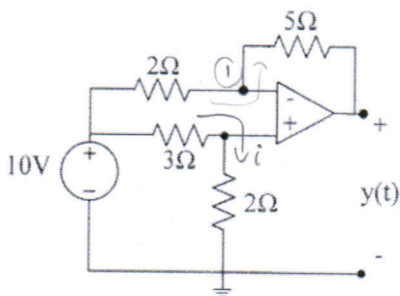(b) In the following circuit, find the output $y(t)$.



$$i = \frac{10}{3+2} = \frac{10}{5} = 2A$$

$$V_+ = 2i = 2(2) = 4V = V_+$$


KCL @ ①

$$\frac{10 - V_+}{2} = \frac{V_+ - y}{5}$$

$$\Rightarrow y = \left[\left(5 - \frac{V_+}{2} \right) 5 - V_+ \right] (-1) = \left[25 - V_+ \left(\frac{5}{2} + 1 \right) \right] (-1)$$

$$= \left(25 - \frac{7}{2} V_+ \right) (-1) = \left(25 - \frac{7}{2} (4) \right) (-1) = (25 - 14) (-1) = \frac{y(t)}{1} = -11V$$

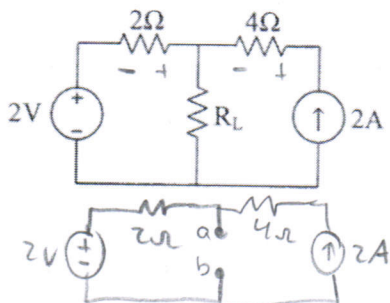(c) What is the maximum power absorbed by R_L .



V_T is open circuit voltage

$$V_T = 2 + 2(2) = 2 + 4 = 6V$$

R_T is R_{eq} after source suppression


$$R_T = 2\Omega$$

$$P_{max} = \left(\frac{V_T}{2} \right)^2 \frac{1}{R_T} = \left(\frac{6}{2} \right)^2 \frac{1}{2} = \frac{9}{2} W$$

$$P_{max} = \frac{9}{2} W$$

Problem 2 (12 points)

(a) Determine $v_{out}(t)$.

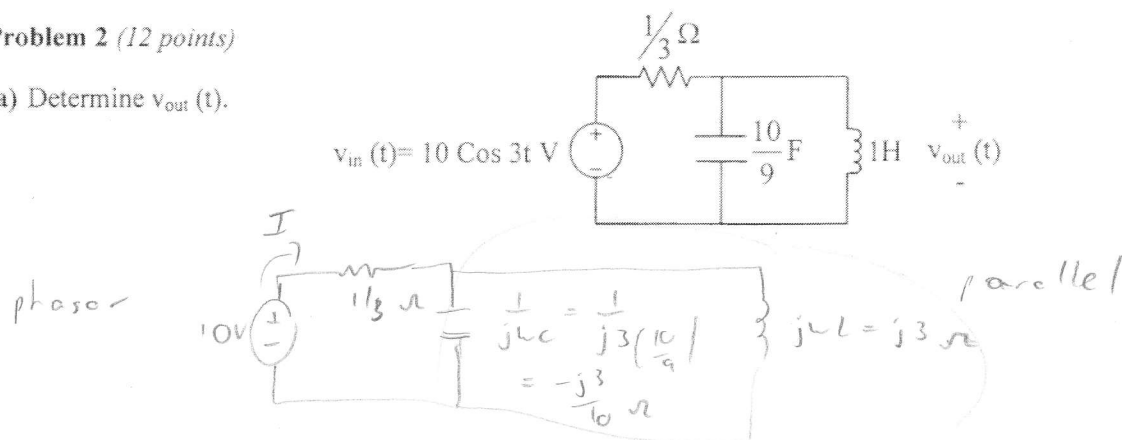

By voltage division

$$\begin{aligned} \hat{V} &= 10 \frac{\left(-\frac{j}{3}\right)}{\frac{-j}{3} + \frac{1}{3}} = \frac{-j10}{3-j+1} = \frac{-j10}{2-j} = \frac{-j10}{1-j} = \frac{10}{\sqrt{2}} e^{j(-\frac{\pi}{2} - (-\frac{\pi}{4}))} \\ &= \frac{10}{\sqrt{2}} e^{-j\frac{\pi}{4}} \end{aligned}$$

$$v_{out}(t) = \frac{10}{\sqrt{2}} \cos\left(3t - \frac{\pi}{4}\right) \text{ V}$$

(b) Determine the average power supplied by the input source $v_{in}(t)$.

In phasor, $I = \frac{10}{\frac{1}{3} - \frac{j}{3}} = \frac{30}{1-j} = \frac{30}{\sqrt{2}} e^{+j\pi/4}$

because of SAS convention \rightarrow

$$\begin{aligned} P &= \frac{1}{2} \operatorname{Re}\{V I^*\} = \frac{1}{2} \operatorname{Re}\left\{10 \left(-\frac{30}{\sqrt{2}} e^{j\pi/4}\right)^*\right\} = \frac{1}{2} (10) \left(-\frac{30}{\sqrt{2}}\right) \operatorname{Re}\{e^{-j\pi/4}\} \\ &= -\frac{150}{\sqrt{2}} \cos\left(-\frac{\pi}{4}\right) = -\frac{150}{\sqrt{2}} \frac{1}{\sqrt{2}} = -75 \text{ W} \end{aligned}$$


absorbed

Answer = +75 W supplied

Problem 3 (12 points)

For $f(t) = 3 + 2\cos(t) + \sin(2t)$

and the following circuit

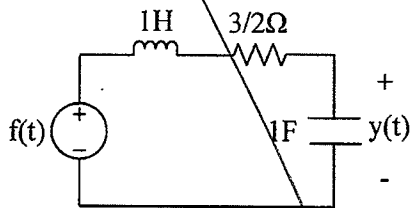

REPEATED
PROBLEM

(a) Is $f(t)$ periodic? If so, what is the period?

Periodic: ☐ YES ☐ NO

$T =$ _____ sec

(b) What are the trigonometric fourier series coefficients of $f(t)$?

(c) Find $y(t)$, the output of the circuit above, for the given $f(t)$.

$y(t) =$ _____

Problem 4 (12 points)

Let $f(t)$ be the periodic function with period $T=4$ given by

$$f(t) = \begin{cases} 2t & 0 \leq t \leq 2 \\ 0 & 2 < t < 4 \end{cases}$$


The following coefficients of its exponential Fourier series are known:

$$F_{-1} = \frac{j2\pi - 4}{\pi^2}$$

$$F_{-2} = \frac{-j}{\pi}$$

$$F_{-3} = \frac{j6\pi - 4}{9\pi^2}$$

$$F_{-4} = \frac{-j}{2\pi}$$

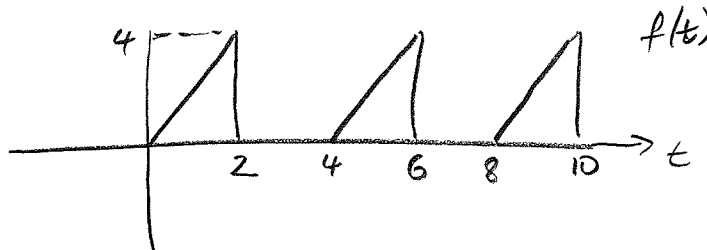

(a) Find the exponential coefficients $F_0, F_1, F_2, F_3,$ and F_4 .

$$F_0 = \text{DC value} = \frac{1}{4} \int_0^4 f(t) dt = \frac{\frac{1}{2}(2)(4)}{4} = 1$$

$$F_n = F_{-n}^* \text{ since } f(t) \text{ is real}$$

$$F_0 = 1$$

$$F_1 = \frac{-j2\pi - 4}{\pi^2}$$

$$F_2 = \frac{j}{\pi}$$

$$F_3 = \frac{-j6\pi - 4}{9\pi^2}$$

$$F_4 = \frac{j}{2\pi}$$

(b) Find the compact Fourier coefficients c_0, c_1, c_2, c_3, c_4 and $\theta_1, \theta_2, \theta_3, \theta_4$.

$$c_n = 2|F_n| \quad \theta_n = \angle F_n$$

Note that θ_1 and θ_3

are in 3rd quadrant,

so they are $-\pi + \tan^{-1}(\dots)$

$$c_0 = 2F_0 = 2$$

$$c_1 = \frac{2\sqrt{4\pi^2 + 16}}{\pi^2} \quad \theta_1 = -\pi + \tan^{-1}\left(\frac{2\pi}{4}\right)$$

$$c_2 = \frac{2}{\pi} \quad \theta_2 = \frac{\pi}{2}$$

$$c_3 = \frac{2\sqrt{36\pi^2 + 16}}{9\pi^2} \quad \theta_3 = -\pi + \tan^{-1}\left(\frac{6\pi}{4}\right)$$

$$c_4 = \frac{1}{\pi} \quad \theta_4 = \frac{\pi}{2}$$

(c) The signal $f(t)$ is the input to an LTI system with frequency response $H(\omega) = \text{sinc}(\omega)$. Obtain the compact Fourier series coefficients of the output $\hat{c}_0, \hat{c}_1, \hat{c}_2, \hat{c}_3, \hat{c}_4$ and $\hat{\theta}_1, \hat{\theta}_2, \hat{\theta}_3, \hat{\theta}_4$.

$$T = 4 \Rightarrow \omega_0 = \frac{2\pi}{T} = \frac{\pi}{2}$$

$$H(0) = \text{sinc}(0) = 1$$

$$H(\omega_0) = \text{sinc}\left(\frac{\pi}{2}\right) > 0$$

$$H(2\omega_0) = \text{sinc}(\pi) = 0$$

$$H(3\omega_0) = \text{sinc}\left(\frac{3\pi}{2}\right) < 0$$

$$H(4\omega_0) = \text{sinc}(2\pi) = 0$$

$$\hat{c}_0 = H(0)c_0 = 2$$

$$\hat{c}_1 = \frac{\text{sinc}(\pi/2)}{\pi^2} c_1 \quad \hat{\theta}_1 = -\pi + \tan^{-1}\left(\frac{2\pi}{4}\right)$$

$$\hat{c}_2 = 0 \quad \hat{\theta}_2 = \text{not applicable}$$


$$\hat{c}_3 = \frac{-\text{sinc}(3\pi/2)}{9\pi^2} c_3 \quad \hat{\theta}_3 = \tan^{-1}\left(\frac{6\pi}{4}\right)$$

$$\hat{c}_4 = 0 \quad \hat{\theta}_4 = \text{not applicable}$$

Note: $|H(3\omega_0)| = -\text{sinc}\left(\frac{3\pi}{2}\right) \quad \angle H(3\omega_0) = \pi$

Problem 5 (13 points)

(a) $f(t)$ is given as in the figure.

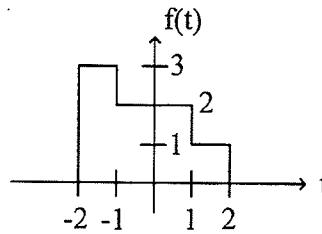

i) Find $F(\omega)$.

$$f(t) = 3 \operatorname{rect}(t+1.5) + 2 \operatorname{rect}(t/2) + \operatorname{rect}(t-1.5)$$

$$F(\omega) = 3 \operatorname{sinc}\left(\frac{\omega}{2}\right) e^{j\omega(1.5)} + 4 \operatorname{sinc}(\omega) + \operatorname{sinc}\left(\frac{\omega}{2}\right) e^{-j\omega(1.5)}$$

$$F(\omega) = \underline{\hspace{2cm}}$$

ii) Let $g(t) = \sqrt{f(t)}$. Find the energy of $g(t)$.

$$\begin{aligned} \mathcal{E} &= \int_{-\infty}^{\infty} |g(t)|^2 dt = \int_{-\infty}^{\infty} f(t) dt = \text{Area under } f(t) \\ &= 1 \times 3 + 2 \times 2 + 1 \times 1 \\ &= 8 \text{ J} \end{aligned}$$

$$\mathcal{E} = \underline{8 \text{ J}}$$

(b) Let $x(t) = 2e^{-t} \operatorname{rect}\left(\frac{t}{2}\right)$.

i) Find $X(\omega)$.

$$\begin{aligned} X(\omega) &= \int_{-\infty}^{\infty} 2e^{-t} \operatorname{rect}\left(\frac{t}{2}\right) e^{-j\omega t} dt = 2 \int_{-1}^1 e^{-(1+j\omega)t} dt = 2 \left. \frac{e^{-(1+j\omega)t}}{-(1+j\omega)} \right|_{-1}^1 \\ &= 2 \left(\frac{e^{-(1+j\omega)}}{-(1+j\omega)} - \frac{e^{(1+j\omega)}}{-(1+j\omega)} \right) = \frac{2}{1+j\omega} (e^{1+j\omega} - e^{-1-j\omega}) \end{aligned}$$

$$X(\omega) = \underline{\hspace{2cm}}$$




ii) Find the energy of $x(t)$.

$$\mathcal{E} = \int_{-\infty}^{\infty} |x(t)|^2 dt = \int_{-1}^1 4e^{-2t} dt = 4 \left. \frac{e^{-2t}}{-2} \right|_{-1}^1 = -2 (e^{-2} - e^2) = 2(e^2 - e^{-2}) \text{ J}$$

$$\mathcal{E} = \underline{2(e^2 - e^{-2}) \text{ J}}$$

Problem 6 (13 points)

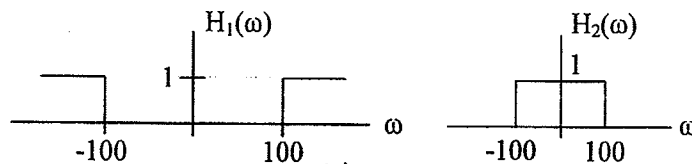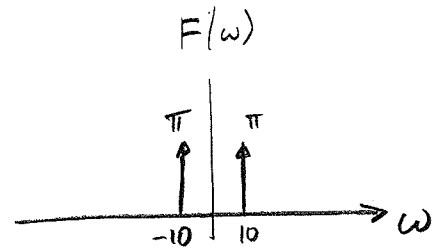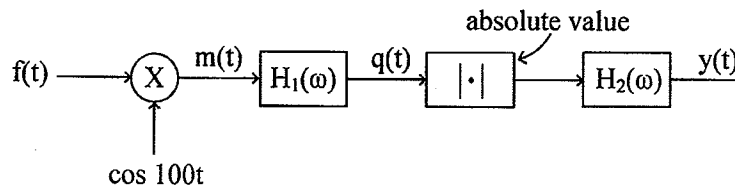(a) The signal $f(t) = \cos(10t)$ is input to the following system.



$m(t) = \cos(10t) \cos(100t)$
 $= \frac{1}{2} \cos(90t) + \frac{1}{2} \cos(110t)$

modulation

$q(t) = \frac{1}{2} \cos(110t)$

$M(\omega)$ has impulses at $\omega = -110$ and $\omega = -90$ with heights $\pi/2$ and $\pi/2$ respectively. It also has impulses at $\omega = 90$ and $\omega = 110$ with heights $\pi/2$ and $\pi/2$ respectively.
 $Q(\omega)$ has impulses at $\omega = -110$ and $\omega = 110$ with heights $\pi/2$ and $\pi/2$ respectively.

$$|q(t)| = \frac{1}{2} |\cos(110t)| = \frac{1}{2} \left(\frac{c_0}{2} + \sum_{n=1}^{\infty} c_n \cos(n 220t + \theta_n) \right)$$


where $c_0 = 2 \left(\text{DC value of } |\cos(110t)| \right)$

$$= 2 \frac{110}{\pi} \int_{-\pi/220}^{\pi/220} \cos(110t) dt$$

$$= 2 \frac{110}{\pi} \frac{\sin(110t)}{110} \Big|_{-\pi/220}^{\pi/220}$$

$$= \frac{2}{\pi} \left(\sin\left(\frac{\pi}{2}\right) - \sin\left(-\frac{\pi}{2}\right) \right) = \frac{4}{\pi}$$
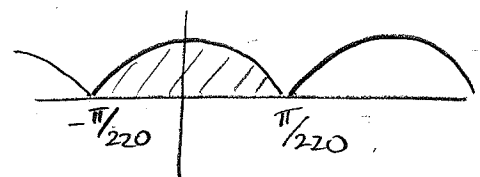
$$y(t) = \frac{1}{2} \frac{c_0}{2} = \frac{1}{\pi}$$



Find:


$$m(t) = \frac{1}{2} \cos(90t) + \frac{1}{2} \cos(110t)$$

$$q(t) = \frac{1}{2} \cos(110t)$$

$$y(t) = \frac{1}{\pi}$$

Problem 1

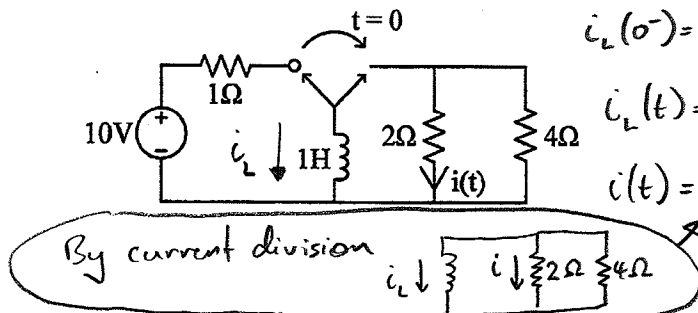(a) The following circuit is in the steady state at $t = 0^-$. Find $i(t)$, $t > 0$.




$$i_L(0^-) = 10 \text{ A} \quad i_L(\infty) = 0 \quad \tau = \frac{L}{R_{\text{th}}} = \frac{1}{8/6} = 0.75$$

$$i_L(t) = 10 e^{-t/0.75}$$

$$i(t) = -\frac{4}{6} i_L(t) = -\frac{20}{3} e^{-t/0.75}$$

$$i(t) = \underline{\hspace{2cm}}$$

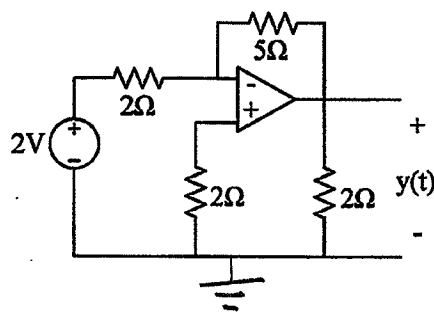(b) Find the output $y(t)$ in the following ideal op-amp circuit.




$$V_+ = 0 \text{ since current into } \oplus \text{ is } 0$$

$$\Rightarrow V_- = 0$$

$$\text{KCL @ } \ominus : \frac{2 - V_-}{2} = \frac{V_- - y(t)}{5} \Rightarrow y(t) = -5 \text{ V}$$

$$y(t) = \underline{-5 \text{ V}}$$

(c) Find I_0 in the following circuit.

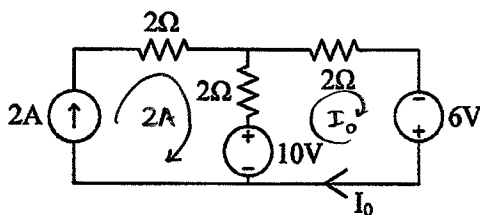

KVL around loop I_0


$$6 + 10 = 2(I_0 - 2) + 2I_0$$

$$16 = 4I_0 - 4$$

$$I_0 = 5 \text{ A}$$


$$I_0 = \underline{5 \text{ A}}$$

R_{TH} : Test signal method

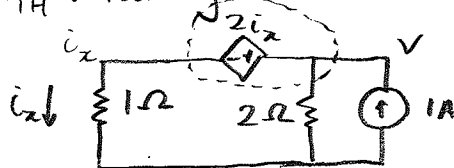

Problem 2

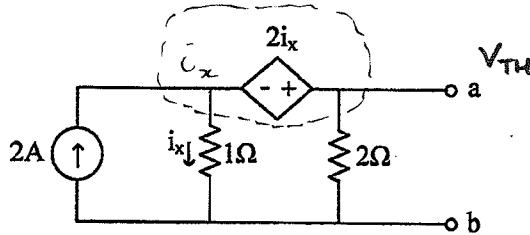- (a) For the network shown below, determine the Thevenin voltage, Thevenin resistance, and Norton current between nodes a and b.




$$V_{TH} = i_x(1) + 2i_x = 3i_x$$

KCL around supernode

$$2 = i_x + \frac{3i_x}{2} \Rightarrow i_x = \frac{4}{5} \Rightarrow V_{TH} = \frac{12}{5} \text{ V}$$

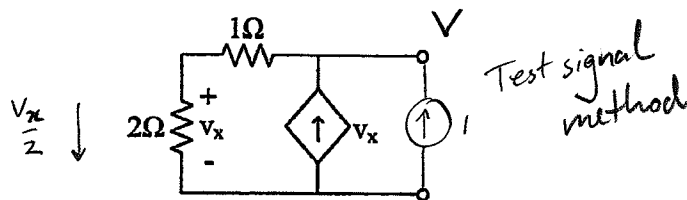- (b) Determine the Thevenin Resistance for the network shown below.




$$R_{TH} = -3 \Omega$$

$$\text{KCL @ } V: \frac{V_x}{2} = i_x + 1 \Rightarrow V_x = -2$$


$$V = \left(\frac{V_x}{2}\right)(1+2) = -3 \Rightarrow R_{TH} = -3 \Omega$$

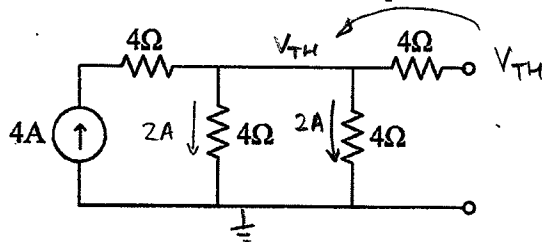- (c) Determine the maximum available power for the network shown below.



$$V_{TH} = 2 \times 4 = 8 \text{ V}$$

$$P_a = \frac{8^2}{3} \text{ W}$$

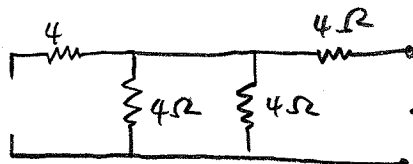


$$R_{TH} = 4 + (4 \parallel 4) = 6 \Omega$$

$$P_a = \frac{V_{TH}^2}{4R_{TH}} = \frac{64}{24} = \frac{8}{3} \text{ W}$$

Problem 3

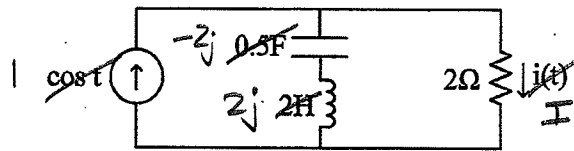(a) Use the phasor method to determine the steady-state current $i(t)$.



$$\omega = 1 \quad \frac{1}{j\omega C} = \frac{1}{j(0.5)} = -2j$$


$$j\omega L = 2j$$

Current division:

$$I = 1 \frac{-2j + 2j}{-2j + 2j + 2} = 0$$


$$i(t) = 0 \text{ A}$$

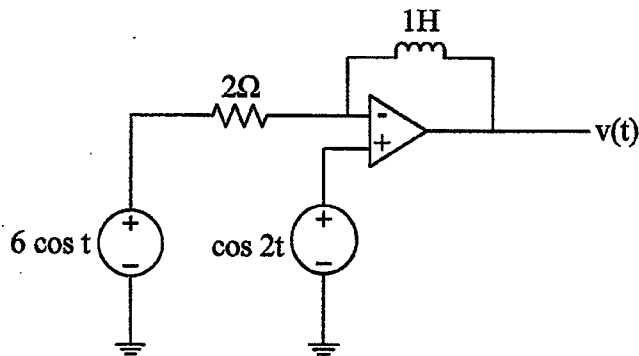(b) Use the phasor method to find the steady-state voltage $v(t)$. Assume an ideal op-amp.



By superposition


$\omega = 1$

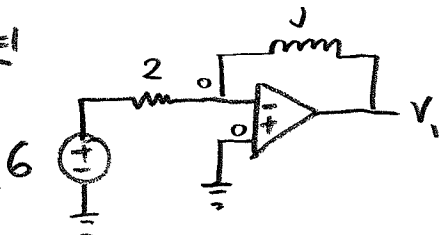

$$v(t) = 3 \cos(t - \pi/2) + \sqrt{2} \cos(2t + \pi/4)$$

$$\text{KCL @ } \ominus \quad \frac{V_1 - 0}{j} = \frac{0 - 6}{2} \Rightarrow V_1 = -3j \Rightarrow |V_1| = 3, \angle V_1 = -\pi/2 \Rightarrow v_1(t) = 3 \cos(t - \pi/2)$$

$\omega = 2$

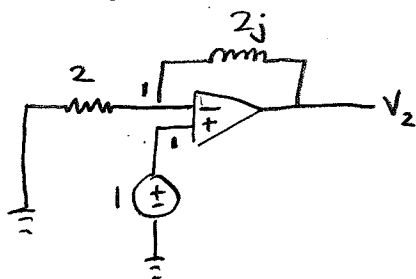

$$\text{KCL @ } \ominus \quad \frac{V_2 - 1}{2j} = \frac{1 - 0}{2} \Rightarrow V_2 = 1 + j$$


$$\Rightarrow |V_2| = \sqrt{2}, \angle V_2 = \pi/4$$

$$\Rightarrow v_2(t) = \sqrt{2} \cos(2t + \pi/4)$$

$$V(t) = v_1(t) + v_2(t) = 3 \cos(t - \pi/2) + \sqrt{2} \cos(2t + \pi/4)$$


Problem 4

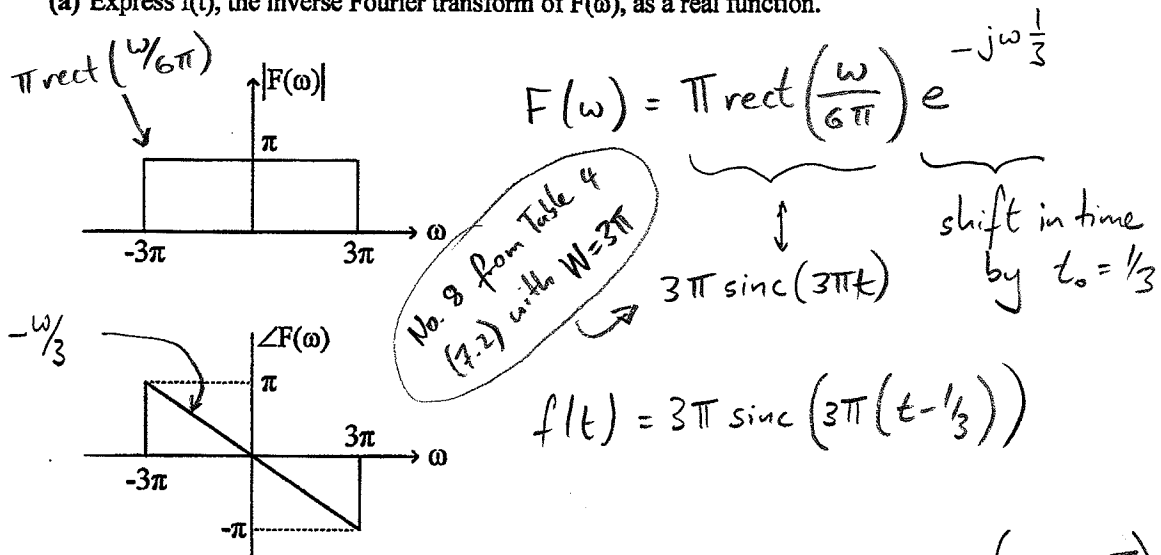(a) Express $f(t)$, the inverse Fourier transform of $F(\omega)$, as a real function.





$$f(t) = \underline{3\pi \operatorname{sinc}(3\pi t - \pi)}$$

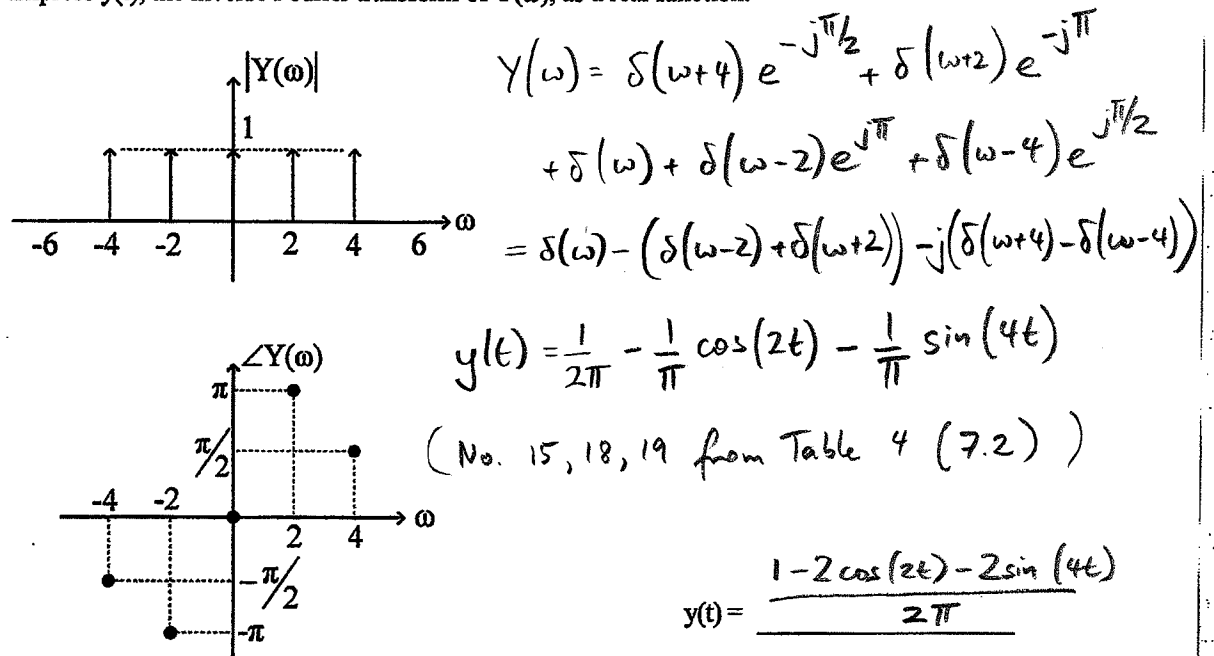(b) Express $y(t)$, the inverse Fourier transform of $Y(\omega)$, as a real function.



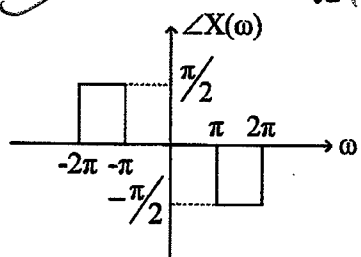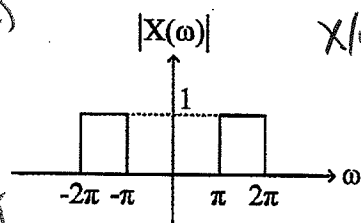(c) Express $x(t)$, the inverse Fourier transform of $X(\omega)$, as a real function.

No. 8 in Table 4 (7.2)
with $W = \pi/2$
and freq shift
property of FT



$$X(\omega) = \text{rect}\left(\frac{\omega + \frac{3}{2}\pi}{\pi}\right) e^{j\pi/2} + \text{rect}\left(\frac{\omega - \frac{3}{2}\pi}{\pi}\right) e^{-j\pi/2}$$


$$= j \left(\text{rect}\left(\frac{\omega + \frac{3}{2}\pi}{\pi}\right) - \text{rect}\left(\frac{\omega - \frac{3}{2}\pi}{\pi}\right) \right)$$

$$x(t) = j \left(\frac{1}{2} \text{sinc}\left(\frac{\pi}{2}t\right) e^{-j\frac{3}{2}\pi t} - \frac{1}{2} \text{sinc}\left(\frac{\pi}{2}t\right) e^{j\frac{3}{2}\pi t} \right)$$

$$= \text{sinc}\left(\frac{\pi}{2}t\right) \frac{1}{2j} \left(e^{j\frac{3}{2}\pi t} - e^{-j\frac{3}{2}\pi t} \right)$$

$$x(t) = \text{sinc}\left(\frac{\pi}{2}t\right) \sin\left(\frac{3}{2}\pi t\right)$$

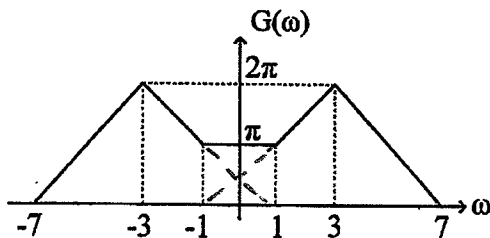(d) Express $g(t)$, the inverse Fourier transform of $G(\omega)$, as a real function.



$$g(t) = 8 \text{sinc}^2(2t) \cos(3t)$$

$$G(\omega) = 2\pi \Delta\left(\frac{\omega+3}{8}\right) + 2\pi \Delta\left(\frac{\omega-3}{8}\right)$$

$$= 2 \Delta\left(\frac{\omega}{8}\right) * \left(\pi \delta(\omega+3) + \pi \delta(\omega-3) \right)$$

$$\downarrow$$

$$\frac{4}{\pi} \text{sinc}^2(2t)$$

$$\updownarrow$$

$$\cos(3t)$$

Using freq. convolution property of F.T.

$$g(t) = 2\pi \left(\frac{4}{\pi} \text{sinc}^2(2t) \right) (\cos(3t)) = 8 \text{sinc}^2(2t) \cos(3t)$$

No. 10 in Table 4 (7.2)
with $W=4$

Problem 5

Let $f(t) = \frac{1}{1+t^2}$ and $y(t) = \frac{1}{1+(t-1)^2}$.

(a) Consider the LTI system $f(t) \rightarrow \boxed{h(t)} \rightarrow y(t)$. Obtain the Fourier transform $Y(\omega)$.

From #4 in Table 4 (7.2), $F(\omega) = \pi e^{-|\omega|}$

Since $y(t) = f(t-1)$, $Y(\omega) = F(\omega) e^{-j\omega 1}$ (time shift property)

$$Y(\omega) = \pi e^{-|\omega|} e^{-j\omega}$$

(b) Let $h(t)$ be the impulse response from part (a) and consider the LTI system

$h(t+1) \rightarrow \boxed{\frac{1}{1+(t+1)^2}} \rightarrow \hat{y}(t)$. Obtain $\hat{y}(t)$.

Since $y(t) = f(t-1) = f(t) * \delta(t-1)$, $h(t) = \delta(t-1)$.


So, $h(t+1) = \delta(t)$

Therefore $\hat{y}(t) = \delta(t) * \frac{1}{1+(t+1)^2} = \frac{1}{1+(t+1)^2}$

$$\hat{y}(t) = \frac{1}{1+(t+1)^2}$$

(c) Can $f(t)$ be sampled without aliasing? If so, which is the minimum required sampling rate ω_0 (rad/s). If not, why?

$$F(\omega) = \pi e^{-|\omega|}$$

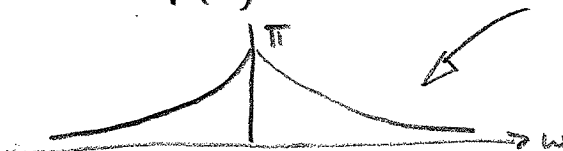

$F(\omega)$ is not bandlimited, so it cannot be sampled without aliasing.

(d) Suppose that before sampling at 10 rad/s, $f(t)$ goes through an ideal low-pass filter LPF. For which range of values of the filter's bandwidth (BW) will the sampling not produce aliasing?

We require sampling rate $\omega_s > 2(BW)$

So, $BW < \frac{\omega_s}{2} = \frac{10 \text{ rad/s}}{2} = 5 \text{ rad/s}$

$$\boxed{BW < 5 \text{ rad/s}}$$

Problem 6

(a) An LTI system with input $f(t)$ and output $y(t)$ is described by the ODE

$$\frac{d^2 y}{dt^2} + 2y(t) = f(t)$$

Determine the frequency response $H(\omega) = \frac{Y(\omega)}{F(\omega)}$.

$$\rightarrow (j\omega)^2 Y(\omega) + 2Y(\omega) = F(\omega)$$

$$H(\omega) = \frac{Y(\omega)}{F(\omega)} = \frac{1}{2 - \omega^2}$$

$$H(\omega) = \frac{1}{2 - \omega^2}$$

(b) A bandpass filter has frequency response $H(\omega) = \frac{j\omega}{1 - \omega^2 + j\omega}$. $H(1) = \frac{j}{1 - 1^2 + j} = 1 = 1e^{j0}$

Determine the filter's output, $y(t)$, for input $f(t) = 3\cos t$.

$$y(t) = 3 |H(1)| \cos(t + \angle H(1))$$

$$= 3 \times 1 \times \cos(t + 0)$$

$$= 3 \cos t$$

$$y(t) = \underline{3 \cos(t)}$$


Determine the steady-state response to a DC input $f(t) = 10$.

$$y_{ss}(t) = H(0) f(t) \text{ since DC is at } \omega = 0$$

$$= \frac{0}{1 - 0^2 + j0} f(t)$$

$$= 0$$

$$y_{ss}(t) = \underline{0}$$

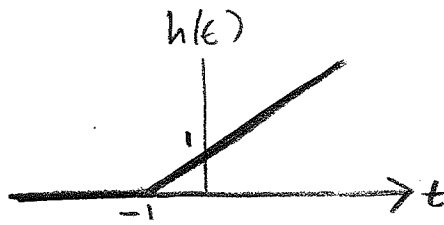

Problem 7 Let $h(t) = (t+1)u(t+1)$ be the impulse response of an LTI system.

(a) Obtain the Laplace transform $\hat{H}(s)$, as well as its poles, zeros, and region of convergence,

ROC.

$$\begin{aligned}\hat{H}(s) &= \int_{0^-}^{\infty} (t+1)u(t+1)e^{-st} dt = \int_{0^-}^{\infty} (t+1)u(t)e^{-st} dt \quad \text{because integral starts at } 0^- \\ &= \mathcal{L}\{t u(t) + u(t)\} = \frac{1}{s^2} + \frac{1}{s} = \frac{s+1}{s^2}\end{aligned}$$

See also Example 11.9 (p. 375) in textbook

$$\hat{H}(s) = \frac{(s+1)}{s^2}$$

poles = 0 (double pole)

zeros = -1, $\pm \infty$

ROC = $\{Re(s) > 0\}$

(b) Is the system causal and/or BIBO stable? Why or why not? (no points if no valid reason)

Noncausal because $h(-1/2) = 1/2 \neq 0$

Not BIBO stable because $\int_{-\infty}^{\infty} |h(t)| dt \rightarrow \infty$

Causal:

Yes

No

☒

Also not BIBO stable because poles (at 0) are not in LHP

BIBO Stable:

Yes

No

☒

(c) Obtain the Laplace transform of $g(t) = \frac{d^2}{dt^2} h(t)$.

$$\hat{G}(s) = s^2 \hat{H}(s) - s h(0^-) - h'(0^-)$$

From the graph of $h(t)$ above,

$$h(0^-) = 1$$

$$h'(0^-) = 1$$

$$\hat{G}(s) = \underline{0}$$

$$\text{So } \hat{G}(s) = s^2 \frac{s+1}{s^2} - s - 1 = 0$$

Alternative: $\frac{d}{dt} h(t) = u(t+1)$, so $g(t) = \frac{d^2}{dt^2} h(t) = \delta(t+1)$
 $\hat{G}(s) = 0$ since $g(t) = 0$ for all $t > 0$

(see graph)