


Analog Signal Processing
Thursday, September 26, 8:45-10pm
Exam I

Last Name:	Solutions
First Name:	
UIN:	
netID	
Course: (circle one)	<div style="display: flex; justify-content: space-around;"> ECE210 ECE211 </div>
Section to return exam: (circle one)	<div style="display: flex; justify-content: space-around;"> 11AM 12PM 2PM 3PM </div>

<p>Clearly PRINT your name in CAPITAL LETTERS.</p> <p>This is a closed book and closed notes exam.</p> <p>Calculators are not allowed.</p> <p>To get full credit, please SHOW all your work and simplify your answers.</p> <p>Write your final answers in the spaces provided.</p> <p>All answers should INCLUDE UNITS whenever appropriate.</p> <p>The exam is printed double-sided.</p>	<p style="text-align: center;">DO NOT write in these spaces.</p> <p>Problem 1 (30 points): _____</p> <p>Problem 2 (25 points): _____</p> <p>Problem 3 (25 points): _____</p> <p>Problem 4 (20 points): _____</p> <p>Total: (100 points): _____</p>
--	---

1. (30 pts) The two parts of this problem are unrelated.

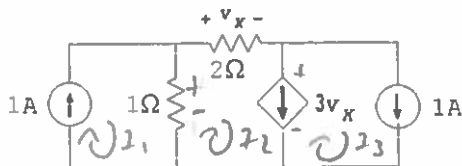- (a) [15 pts] Consider the circuit below. Determine the voltage V_X and the absorbed power at the dependent source, P_{3V_X} .



$$V_X = \underline{-2/5 \text{ V}}$$

$$P_{3V_X} = \underline{-48/25 \text{ W}}$$

$$I_1 = 1$$

$$I_3 = 1$$


$$3V_X = I_2 - I_3 = I_2 - 1 = 3(2I_2) = 6I_2 \Rightarrow 5I_2 = -1 \Rightarrow I_2 = -\frac{1}{5}$$

$$V_X = 2I_2$$

$$= 2\left(-\frac{1}{5}\right) = -\frac{2}{5}$$

$$P_{3V_X} = 3V_X [1(I_1 - I_2) - 2I_2] = 3\left(-\frac{2}{5}\right) \left[1 - \left(-\frac{1}{5}\right) - 2\left(-\frac{1}{5}\right)\right] = -\frac{6}{5} \left[\frac{5+1+2}{5}\right] = -\frac{48}{25}$$

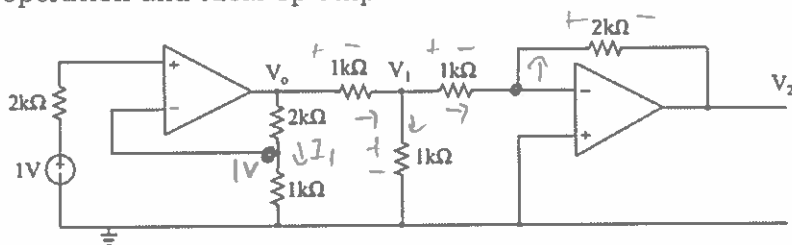- (b) [15 pts] Determine the voltages V_0 , V_1 and V_2 in the following circuit, assuming linear operation and ideal op-amp conditions.



$$V_0 = \underline{3 \text{ V}}$$

$$V_1 = \underline{1 \text{ V}}$$


$$V_2 = \underline{-2 \text{ V}}$$

$$I_1 = \frac{1}{1k} \Rightarrow V_0 = (2k + 1k)I_1 = \frac{3k}{1k} = 3$$

$$\text{KCL @ } V_1: \frac{V_0 - V_1}{1k} = \frac{V_1 - 0}{1k} + \frac{V_1 - 0}{1k} \Rightarrow 3V_1 = V_0 \Rightarrow V_1 = 1 \text{ V}$$

$$\text{KCL @ } \ominus: \frac{V_1 - 0}{1k} = \frac{0 - V_2}{2k} \Rightarrow V_2 = -2V_1 = -2$$

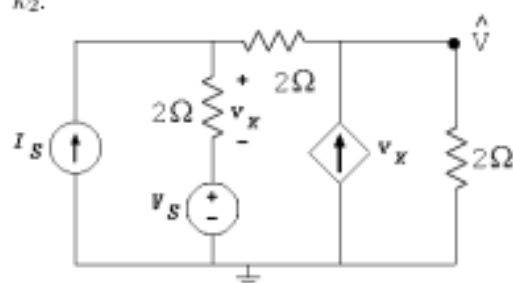2. (25 pts) Consider the resistive circuit shown in the diagram below. Node voltage \hat{V} can be expressed as $\hat{V} = k_1 V_S + k_2 I_S$. Use superposition to obtain the value of k_1 and the value of k_2 .



Suppress " I_S ";

$$\text{KCL: } \frac{V - V_S}{4} + \frac{V}{2} = v_x \quad \dots (1)$$

$$\text{and } v_x = \frac{V - V_S}{2} \quad \dots (2)$$

solve (1) and (2) for V .

$$V = -V_S$$

$$k_1 = -1$$

Suppress " V_S "

$$\text{KCL: } I_S + \frac{V - v_x}{2} = \frac{v_x}{2} \quad \dots (1)$$

$$v_x = \frac{V}{2} + \frac{V - v_x}{2} \quad \dots (2)$$

solve (1) and (2) for V .


$$V = 6 I_S$$

$$k_2 = 6.$$

$$k_1 = -1 \quad \underline{\hspace{2cm}}$$

$$k_2 = 6 \quad \underline{\hspace{2cm}}$$

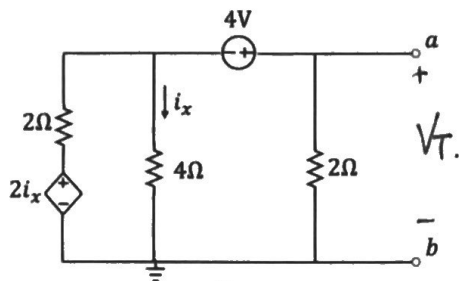3. (25 pts) Consider the circuit below. Determine Thevenin's voltage, V_T , and Norton's current, I_N , between nodes a and b . Also draw the corresponding Thevenin equivalent circuit and Norton equivalent circuit.



$$V_T = 2 \text{ V}$$

$$I_N = 2 \text{ A}$$

Supernode KCL @ Top.

$$\frac{(V_T - 4) - 2i_x}{2} + \frac{(V_T - 4) - 0}{4} + \frac{V_T}{2} = 0$$


$$\frac{(V_T - 4) - 0}{4} = i_x$$

$$\frac{V_T - 4}{2} - \frac{V_T - 4}{2} + \frac{V_T - 4}{4} + \frac{V_T}{2} = 0$$

$$\frac{V_T - 4}{2} + \frac{V_T}{2} = 0$$

$$\Rightarrow V_T = 2 \text{ V}$$

$$i_x = -\frac{1}{2} \text{ A}$$

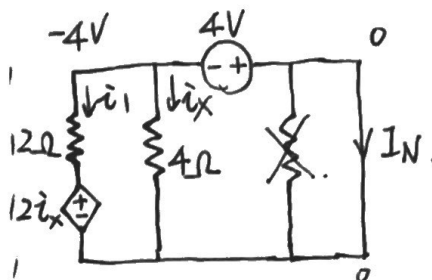

$$i_x = \frac{-4 - 0}{4} = -1 \text{ A}$$

$$\text{Voltage of } 2i_x = -2 \text{ V}$$

$$i_1 = \frac{-4 - (-2)}{2} = -1 \text{ A}$$


Supernode KCL @ Top

$$I_N + i_1 + i_x = 0$$


$$I_N = -(i_1 + i_x) = 2 \text{ A}$$

$$R_T = \frac{V_T}{I_N} = 1 \Omega$$


Thevenin equivalent circuit

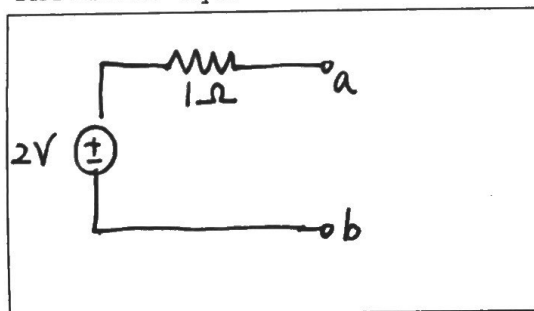

Norton equivalent circuit

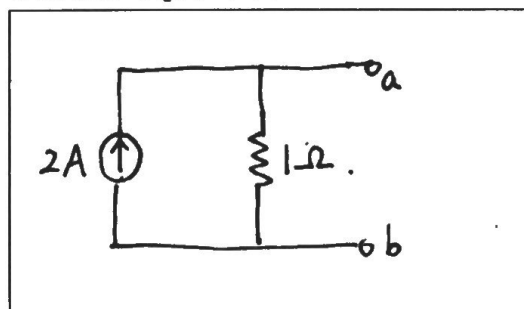

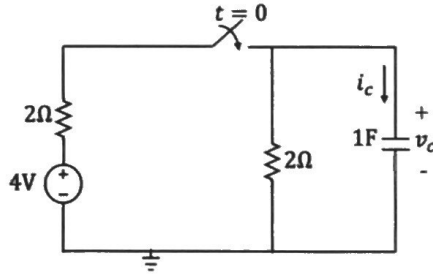4. (20 pts) Consider the circuit below, assuming that $v(0^-) = 2V$.



$$v_c(0^-) = 1V.$$

- (a) [3 pts] Determine $i_C(0^+)$ and $v_C(0^+)$. Explain.

$v_C(0^+) = v_C(0^-) = 1V$. because voltage across capacitor doesn't jump (is continuous).
 at $t=0^+$. KCL @ Top node. $v_C(0^+) = 2V$ at top node

$$\frac{1-4}{2} + \frac{1-0}{2} + i_C(0^+) = 0$$

$$i_C(0^+) = 1A$$

$$i_C(0^+) = \underline{1A}$$

$$v_C(0^+) = \underline{1V}$$

- (b) [2 pts] For $t > 0$, determine time constant. Show your work.

$$V_T = \frac{2}{2+2} \cdot 4 = 2V.$$

$$R_T = 2 \parallel 2 = 1\Omega.$$

Equivalent ckt after $t > 0$.

$$\tau = RC = 1s.$$

$$\tau = \underline{1s}.$$

- (c) [3 pts] Determine the steady state values of i_C and v_C . Explain.

at steady state, capacitor behave like a open circuit

Use voltage divider rule


$$V_C = 4 \cdot \frac{2}{2+2} = 2V.$$

$$i_C(\infty) = 0 \text{ since open ckt } i_C(\infty) = \underline{0A}$$

$$v_C(\infty) = \underline{2V}$$

1. [8 pts] Express $v_C(t)$ for $t > 0$.

Equivalent ckt from problem 4.(b).

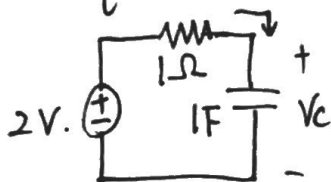

use KVL.

$$2 = R \cdot C \frac{dv_C}{dt} + v_C.$$

$$\frac{dv_C}{dt} + \frac{1}{RC} v_C = \frac{1}{RC} V_T. \quad (\text{or directly write ODE})$$

$$\frac{dv_C}{dt} + v_C = 2.$$

$$v_C(t) = A e^{-t} + 2. \quad \text{with initial condition } v_C(0^+) = 1 \text{ V.}$$

$$v_C(0^+) = A + 2 = 1 \Rightarrow A = -1.$$

$$\therefore v_C(t) = -1 e^{-t} + 2 \quad \text{for } t > 0$$

$$v_C(t) = -1 e^{-t} + 2 \quad \text{for } t > 0.$$

- (a) [4 pts] Below sketch $v_C(t)$ for $t > 0$. Label numerical values on the axes.

