

• Example #13: Time-invariance

- Consider a system with input $f(t)$, initial state $y(0) = y_0$ and input-output rule given by

$$y(t) = \underset{0}{y_0} + f(t^2)$$

- Determine if the system is time-invariant or not

zero-state $\Rightarrow y_0 = 0 \Rightarrow y_{zs}(t) = f(t^2)$

$$f_1(t) \rightarrow \boxed{} \rightarrow y_1(t) = f_1(t^2)$$

$$f_2(t) \rightarrow \boxed{} \rightarrow y_2(t) \stackrel{?}{=} y_1(t - t_d)$$


$$f_1(t - t_d) \stackrel{?}{=} f_1((t - t_d)^2)$$

$$f_2(t^2) = f_1(t^2 - 3^{td}) \quad \checkmark \quad \text{not T.I.} \ddot{\sim}$$

$$y_1(t - 3) = f_1((t - 3)^2) \quad \checkmark$$

$t_d = 3s$ -
used for
simplifying only,
has to work
for any t_d

- First-order RC and RL circuits

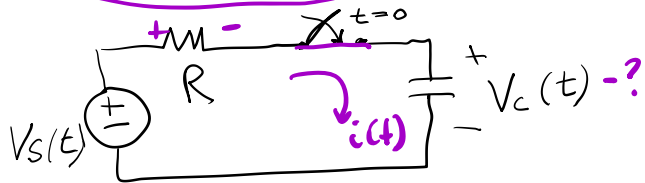

$$v_c(0^-) = v_c(0) = v_c(0^+) - \text{I.C.}$$

$t > 0$

$$\text{KVL: } -v_s(t) + i(t) \cdot R + v_c(t) = 0$$

$$i(t) = C \frac{dv_c}{dt}$$

$$RC \frac{dv_c}{dt} + v_c(t) = v_s(t) \quad | : RC$$

$$\boxed{\frac{dy}{dt} + \frac{1}{RC} y = \frac{v_s(t)}{RC} f(t)}$$

In general:

$$f(t) = \frac{dy}{dt} + ay(t)$$

First-order linear ordinary differential equation (ODE)

with constant coefficients,
which governs RC circuit for $t > 0$

- First-order ODE with constant coefficients

$$f(t) = \frac{dy}{dt} + ay(t)$$

- How to solve?

- Start with a simple case: constant input

$$f(t) = K \Rightarrow K = \frac{dy}{dt} + ay(t)$$

$y(t) = B - \text{constant}$ 

$$K = 0 + a \cdot B \Rightarrow B = \frac{K}{a}$$

$$y_p(t) = \frac{K}{a}$$

↑
particular
solution

- First-order ODE with constant coefficients-cont

$$\ominus \frac{k}{a} + \overset{?}{A} e^{-at}$$

1 when $t=0$

To get A:

$$y(0^-) = y(0^+) = \frac{k}{a} + A$$

if continuous

↓

$$A = y(0^+) - \frac{k}{a}$$

$$y(t) = \frac{k}{a} + \left(y(0^+) - \frac{k}{a} \right) e^{-at}$$

$$K = \frac{dy}{dt} + ay(t)$$

$$y(t) = \underbrace{\frac{K}{a}}_{y_0(t)} + \underbrace{y_h(t)}_{\text{homogeneous solution}} \ominus$$

$$k = \frac{d}{dt} \left(\frac{k}{a} + y_h \right) + a \left(\frac{k}{a} + y_h \right)$$

$$K = \frac{dy_h}{dt} + K + ay_h$$

$$\frac{dy_h}{dt} + ay_h = 0$$

$$y_h = A e^{-at}$$

$$-a \cdot A e^{-at} + a \cdot A e^{-at} = 0$$

- First-order ODE with constant coefficients-cont

$$K = \frac{dy}{dt} + ay(t)$$

$$y(t) = \frac{K}{a} + y_h(t)$$

- First-order ODE with constant coefficients-cont

$$K = \frac{dy}{dt} + ay(t)$$

- For $t > 0$

$$y(t) = \underbrace{y_p(t)} + \underbrace{y_h(t)} = \underbrace{B} + \underbrace{Ae^{-at}} = \underbrace{\frac{K}{a}}_{y_p} + \underbrace{\left(y(0^+) - \frac{K}{a}\right) e^{-at}}_{y_h}$$

- Solution to RC circuit with constant source

- Recall

$$K = \frac{dy}{dt} + ay(t)$$

for $t \geq 0$ $y(t) = \underbrace{\frac{K}{a}}_{y_p} + \underbrace{(y(0^+) - \frac{K}{a})}_{y_h} e^{-at}$

$$y_p = \frac{K}{a} = \frac{V_s}{RC} \cdot RC = V_s$$

← constant source

$$y_h = (y(0^+) - \frac{K}{a}) e^{-at} = (v_c(0^-) - V_s) e^{-\frac{t}{RC}}$$

$$v_c(t) = (v_c(0^-) - V_s) e^{-\frac{t}{RC}} + V_s \quad \text{for } t \geq 0$$


$$\frac{V_s}{RC} = \frac{dV_c}{dt} + \frac{1}{RC} V_c(t)$$

For a capacitor:

$$y(0^+) = y(0^-) = v_c(0^-)$$

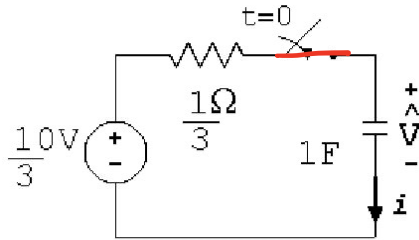• Example #14:

- Consider the following circuit with $V_c(0^-) = 1V$.
- Determine $V_c(t)$ and $i_c(t)$.



for $t > 0$:

$$\textcircled{1} \frac{dv_c}{dt} + \frac{1}{RC} v_c(t) = \frac{V_s}{RC} = 10$$

$$\textcircled{2} \frac{dv_c}{dt} + 3v_c(t) = 10$$

$$\textcircled{3} y(t) = y_p + y_h = \textcircled{B} + A e^{-at}$$

$$0 + 3B = 10 \Rightarrow B = \frac{10}{3}$$

$$\textcircled{4} v_c(t) = \frac{10}{3} + A e^{-3t}$$

if $t=0$


⑤ Find A:

$$v_c(0^-) = v_c(0^+) = 1 = \frac{10}{3} + A \Rightarrow A = 1 - \frac{10}{3} = -\frac{7}{3}$$

$$\textcircled{6} v_c(t) = \frac{10}{3} - \frac{7}{3} e^{-3t}$$

↗ 0 when $t \rightarrow \infty$


↑ units, please

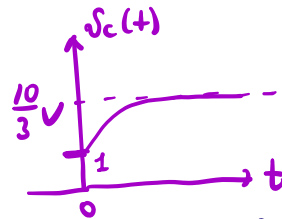

$$v_c(0^+) = \frac{10}{3} - \frac{7}{3} = 1 = v_c(0^-)$$


$i_c(t) - ?$
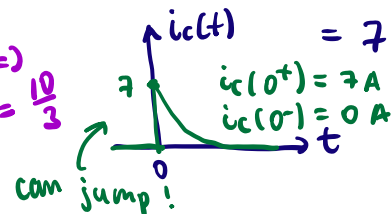
$$i_c(t) = C \frac{dv_c}{dt} = 7 e^{-3t} A$$



• Time-constant

• Recall

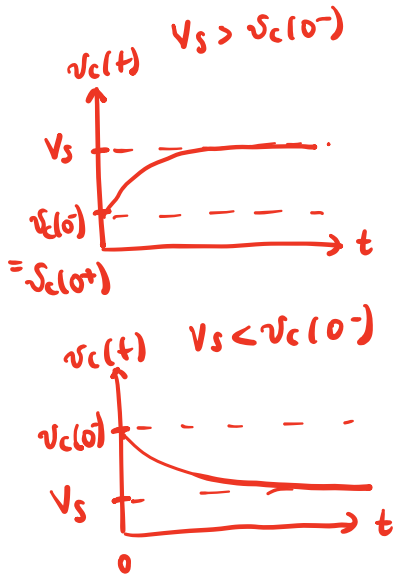

Rate of decay is controlled
by a time constant

$$\tau = RC$$

$$y(t) = \frac{K}{a} + \left(y(0^+) - \frac{K}{a}\right) e^{-at}$$

$$v_c(t) = \underbrace{(v_c(0^-) - V_s)}_{\text{transient response}} e^{-\frac{t}{RC}} + \underbrace{V_s}_{\text{steady-state response}}$$

(part which goes to 0 when $t \rightarrow \infty$) (which is left after transient response has vanished)