

11) a)  $\alpha = ?$  (varies by student)

b) i)  $f_1(t) = -10 \sin(2t - \frac{\pi}{2}) = -10 \cos(2t - \frac{\pi}{2} - \frac{\pi}{2})$

$$\Rightarrow F_1 = -10 e^{j(-\frac{\pi}{2} - \frac{\pi}{2})} = 10 e^{j(-\frac{\pi}{2} - \frac{\pi}{2} + \pi)}$$

$$= 10 e^{j\pi \left( \frac{-2 - \alpha + 2\alpha}{2\alpha} \right)} = 10 e^{j\pi \left( \frac{\alpha - 2}{2\alpha} \right)}$$

plug in  $\alpha$

ii)  $f_2(t) = -\alpha \cos(3t) + \alpha \sin(3t) \rightarrow$  same frequency

$\downarrow$  phasor

$\downarrow$   
 $-j$

$$\Rightarrow F_2 = -\alpha(1) + \alpha(-j) = -\alpha(1+j) = \alpha \sqrt{1^2+1^2} e^{j(\pi+\frac{\pi}{4})}$$

$$= \sqrt{2} \alpha e^{-j\frac{3\pi}{4}} \quad = \frac{5\pi}{4} \rightarrow \pi$$

$\downarrow$  plug in  $\alpha$

c)  $\frac{d^2}{dt^2} y + \frac{d}{dt} y + \alpha y = f(t) = \sin(\alpha t)$

$\downarrow \omega = \alpha$

$\downarrow$  phasors

$$(j\omega)^2 Y + j\omega Y + \alpha Y = -j \Rightarrow Y = \frac{-j}{-\alpha^2 + j\alpha + \alpha} = \frac{-j}{\alpha(1-\alpha+j)}$$

$$= \frac{e^{-j\pi/2}}{\alpha \sqrt{(1-\alpha)^2 + 1^2}} e^{j(\pi + \tan^{-1}(\frac{1}{1-\alpha}))}$$

$$= \frac{e^{+j(\frac{\pi}{2} + \pi + \tan^{-1}(\frac{1}{1-\alpha}))}}{\alpha \sqrt{1+(1-\alpha)^2}}$$

$$\Rightarrow y(t) = \frac{1}{\alpha \sqrt{1+(1-\alpha)^2}} \cos\left(\alpha t + \frac{\pi}{2} - \tan^{-1}\left(\frac{1}{1-\alpha}\right)\right) \leftarrow \text{plug in } \alpha$$

Notice that no matter what the value of  $\alpha$  is, the calculation is simple.

Problem 2 solutions:

Note: replace every instance of the symbol  $\beta$  with your own numerical value obtained from your UIN.

a)  $\beta$

b) Method 1:  $P_{Z2} = \frac{1}{2} \text{Re}\{V_{Z2} I_{Z2}^*\} = \frac{1}{2} \text{Re}\{Z_{Z2} I_{Z2} I_{Z2}^*\} = \frac{1}{2} \text{Re}\{Z_2 |I_2|^2\}$ , where  $|I_2|^2$  is real and  $Z_2$  is imaginary, so  $P_{Z2} = 0$ .

Method 2:  $Z_2 = j2 \Omega$ , so  $Z_2$  corresponds to in an inductor (if  $\omega > 0$ ) or a capacitor (if  $\omega < 0$ ). Either way,  $P_{Z2} = 0$ .

(Note 1: no numerical computation is required to reach this solution)

(Note 2: This part of the problem is essentially the same as problems 3c and 3d of HW #6)

c) Rectangular form:  $Z_1 = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC} = \frac{\beta}{1 + j} = \frac{\beta(1-j)}{2} = \frac{\beta}{2} - j\frac{\beta}{2}$ .

(Note: The computational complexity should not be affected by your  $\beta$  value as  $\beta$  is an odd number regardless of you UIN)

d)  $Z_3 = Z_1 - Z_2 \implies Z_1 = Z_2 + Z_3$

According to current division, the current through  $Z_1$  is  $I_1 = I_S/2$


$P_{Z1} = \frac{1}{2} \text{Re}\{V_1 I_1^*\} = \frac{1}{2} \text{Re}\{Z_1 I_1 I_1^*\} = \frac{1}{2} \text{Re}\{Z_1 |I_1|^2\} = \frac{1}{2} |I_1|^2 \text{Re}\{Z_1\} = \frac{1}{8} |I_S|^2 \text{Re}\{Z_1\} = \frac{1}{8} 4\beta^2 2\beta = \beta^3$

(Note: Leaving your solution to be something like  $47^3$  is acceptable. )

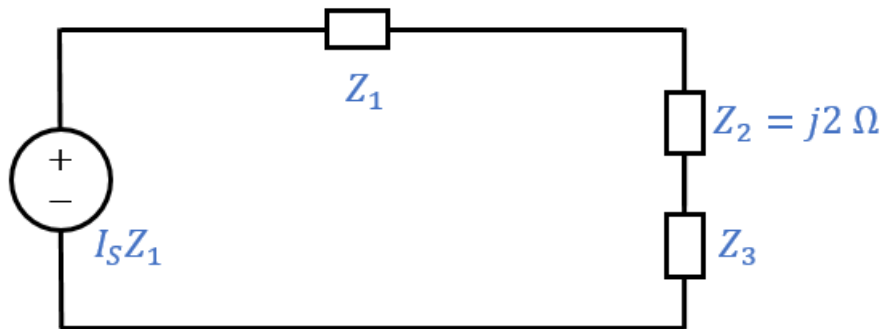e)  $P_{Z2} = 0$ , so the problem is converted to finding  $Z_3$  that maximizes  $P_3$ .

According to the concept of matched load,  $P_3$  is maximized when  $Z_3 = Z_T^*$

To find  $Z_T$ , we convert the original circuit into the following via source transformation:



$$Z_T = Z_1 + Z_2 = \beta + j \cdot 3.14 + j2 = \beta + j5.14$$

$$Z_3 = Z_T^* = \beta - j5.14$$

(Note: this part does not involve any numerical computations on  $\beta$ )

3) a)  $\alpha = \underline{\hspace{2cm}}$



b) LC circuit

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \omega_0 = \frac{1}{\sqrt{\alpha \alpha}} = \frac{1}{\sqrt{\alpha^2}}$$

$$L = \alpha H$$

$$C = \alpha F$$

$$\boxed{\omega_0 = \frac{1}{\alpha}}$$

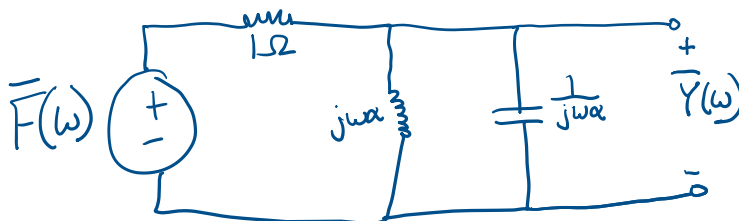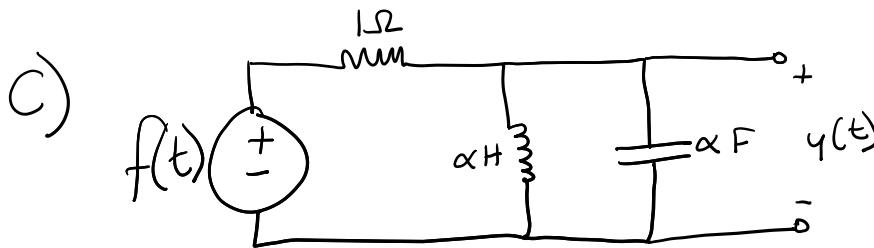

\* There are Many ways to find  $H(w) = \frac{\bar{Y}(w)}{\bar{F}(w)}$ .  
Below are a few methods.

Method 1: Source Transformation



$$V(w) = I_r$$


$$V(w) = \frac{w\alpha}{j((w\alpha)^2 - 1) + w\alpha} \bar{F}(w)$$

$$\boxed{H(w) = \frac{V(w)}{\bar{F}(w)} = \frac{w\alpha}{j((w\alpha)^2 - 1) + w\alpha}}$$

$$\bar{I}_r = \frac{\left(\frac{1}{jw\alpha} + jw\alpha\right)^{-1}}{1 + \left(\frac{1}{jw\alpha} + jw\alpha\right)^{-1}} \bar{F}(w) \Rightarrow \frac{\left(\frac{-j + j(w\alpha)^2}{w\alpha}\right)^{-1}}{1 + \left(\frac{-j + j(w\alpha)^2}{w\alpha}\right)^{-1}} \bar{F}(w)$$

$$= \frac{w\alpha}{j((w\alpha)^2 - 1) + w\alpha} \bar{F}(w) \Rightarrow \frac{w\alpha}{j((w\alpha)^2 - 1) + w\alpha} \bar{F}(w)$$

## Method 2: Node Voltage

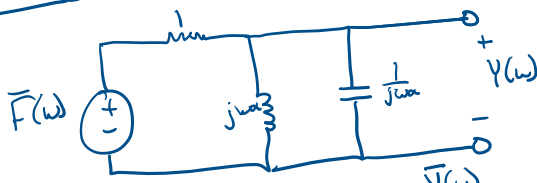

$$\frac{F(w) - \bar{Y}(w)}{1} = \frac{\bar{Y}(w)}{jw\alpha} + jw\alpha \bar{Y}(w) \Rightarrow \bar{F}(w) = \bar{Y}(w) + \frac{1}{jw\alpha} \bar{Y}(w) + jw\alpha \bar{Y}(w)$$

$$\bar{Y}(w) = \frac{1}{1 + jw\alpha + \frac{1}{jw\alpha}} \bar{F}(w)$$

$$H(w) = \frac{\bar{Y}(w)}{\bar{F}(w)} = \frac{1}{1 + jw\alpha + \frac{1}{jw\alpha}}$$

$$H(w) = \frac{1}{\frac{w\alpha + j((w\alpha)^2 - 1)}{w\alpha}} \Rightarrow \frac{w\alpha}{w\alpha + j((w\alpha)^2 - 1)}$$

## Method 3: Voltage Division



$$\bar{Y}(w) = \frac{\left(\frac{1}{jw\alpha} + jw\alpha\right)^{-1}}{1 + \left(\frac{1}{jw\alpha} + jw\alpha\right)^{-1}} \bar{F}(w) \Rightarrow$$

$$\frac{\left(\frac{-j + j(w\alpha)^2}{w\alpha}\right)^{-1}}{1 + \left(\frac{-j + j(w\alpha)^2}{w\alpha}\right)^{-1}} \bar{F}(w)$$

$$= \frac{\frac{w\alpha}{j((w\alpha)^2 - 1)}}{1 + \frac{w\alpha}{j((w\alpha)^2 - 1)}} \bar{F}(w) \Rightarrow$$

$$\bar{Y}(w) = \frac{w\alpha}{w\alpha + j((w\alpha)^2 - 1)} \bar{F}(w)$$

$$H(w) = \frac{\bar{Y}(w)}{\bar{F}(w)} = \frac{w\alpha}{w\alpha + j((w\alpha)^2 - 1)}$$

$$d) \quad f(t) = 2 + 2 \cos(2t)$$

$$Y(\omega) = \sum H(\omega) \bar{F}(\omega)$$

$$y(t) = 2|H(\omega=0)| + 2|H(\omega=2)| \cos(2t + \angle H(\omega=2))$$

$$H(\omega) = \frac{\omega \alpha}{\omega \alpha + j((\omega \alpha)^2 - 1)} = \frac{\omega \alpha (\omega \alpha - j((\omega \alpha)^2 - 1))}{(\omega \alpha)^2 + ((\omega \alpha)^2 - 1)^2}$$

$$= \frac{(\omega \alpha)^2 - j \omega \alpha ((\omega \alpha)^2 - 1)}{(\omega \alpha)^2 + ((\omega \alpha)^2 - 1)^2}$$

$$|H(\omega)| = \sqrt{\frac{(\omega \alpha)^4 + (\omega \alpha)^2 ((\omega \alpha)^2 - 1)^2}{((\omega \alpha)^2 + ((\omega \alpha)^2 - 1)^2)^2}} \Rightarrow \sqrt{\frac{(\omega \alpha)^2 ((\omega \alpha)^2 + ((\omega \alpha)^2 - 1)^2)}{((\omega \alpha)^2 + ((\omega \alpha)^2 - 1)^2)^2}}$$

$$|H(\omega)| = \sqrt{\frac{(\omega \alpha)^2}{(\omega \alpha)^2 + ((\omega \alpha)^2 - 1)^2}}$$

$$|H(\omega=0)| = 0$$

$$|H(\omega=2)| = \sqrt{\frac{4\alpha^2}{4\alpha^2 + (4\alpha^2 - 1)^2}}$$

$$\angle H(\omega) = \tan^{-1} \left( \frac{-\omega \alpha ((\omega \alpha)^2 - 1)}{(\omega \alpha)^2} \right) = \tan^{-1} \left( \frac{-((\omega \alpha)^2 - 1)}{\omega \alpha} \right)$$

$$\angle H(\omega=2) = \tan^{-1} \left( \frac{1-4\alpha^2}{2\alpha} \right)$$

$$y(t) = 2(0) + 2 \sqrt{\frac{4\alpha^2}{4\alpha^2 + (4\alpha^2 - 1)^2}} \cos(2t + \tan^{-1} \left( \frac{1-4\alpha^2}{2\alpha} \right))$$

≠ 4

a)  $d = ?$  (varies by student)

b) Notice  $h(t) = f(-(t+d))$

Recall that if  $g(t) = f(-t)$

$$\Rightarrow G_\eta = F_{-\eta}$$

And if  $h(t) = g(t+d)$


$$\Rightarrow H_\eta = G_\eta e^{j\eta\omega d} = F_{-\eta} e^{j\eta\omega d}$$

$$= F_{-\eta} e^{j\eta \frac{\pi}{5} d}$$

$$T=10 \Rightarrow \omega_0 = \frac{2\pi}{10} = \frac{\pi}{5}$$

$$= \begin{cases} 0 & \eta = 0 \\ \frac{(-1)^{-\eta} e^{j\eta \frac{\pi}{5} d}}{j\eta \pi d} & \eta \neq 0 \end{cases}$$

↑ plug in  $d$

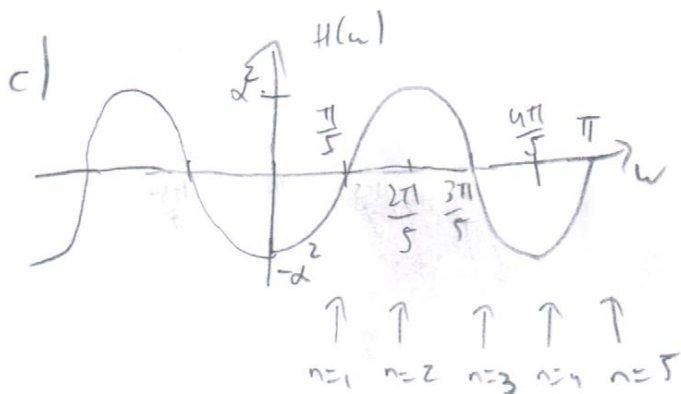

$$\sin\left(\frac{5\omega}{2} - \frac{\pi}{2}\right) = -\cos\left(\frac{5\omega}{2}\right)$$

only  $n = \pm 2, \pm 4$   
go through

$$y(t) = \sum_{n=-\infty}^{\infty} F_n H(n\omega_0) e^{jn\omega_0 t}$$

$$= \frac{-1}{j2\pi d} e^{j\frac{2\pi}{5}t} + \frac{+1}{j2\pi d} e^{-j\frac{2\pi}{5}t} + \frac{-1(-d)}{j4\pi d} e^{j\frac{4\pi}{5}t} + \frac{+1(-d)}{j4\pi d} e^{-j\frac{4\pi}{5}t}$$

$$= -\frac{d}{\pi} \sin\left(\frac{2\pi}{5}t\right) + \frac{d}{2\pi} \sin\left(\frac{4\pi}{5}t\right)$$

↑  
Notice

$$\omega_{orig} = \frac{2\pi}{5} \text{ rad/s}$$