

Analog Signal Processing**Thursday, October 21, 8:45-10pm****Exam II**

Last Name (capitalized):	
---	--


First Name:	
------------------------	--

UIN:	
-------------	--

netID:	
---------------	--

<p>Clearly PRINT your name in CAPITAL LETTERS.</p> <p>This is a closed book and closed notes exam.</p> <p>Calculators are not allowed.</p> <p>To get credit, please SHOW all your work and simplify your answers.</p> <p>Write your final answers in the spaces provided.</p> <p>All answers should INCLUDE UNITS whenever appropriate.</p> <p>The exam is printed double-sided.</p>	<p>DO NOT write in these spaces.</p> <p>Problem 1 (25 points):_____</p> <p>Problem 2 (25 points):_____</p> <p>Problem 3 (25 points):_____</p> <p>Problem 4 (25 points):_____</p> <p>Total: (100 points):_____</p>
---	--

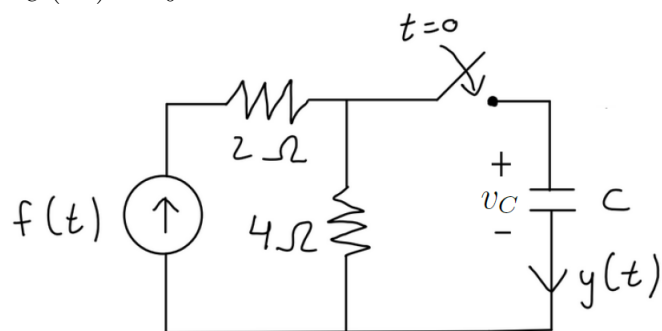1. (25 pts) Consider the LTI circuit below with current $f(t) = \cos(\omega t) + 3 \sin(\omega t)$ A and voltage $v_C(0^-) = v_0$ V.



It is known that the current $y(t) = 2 \cos(2t) + \sin(2t) + Be^{-2t}$ A for $t > 0$.

- (a) [5 pts] Write the ODE that governs this LTI system for $t > 0$ in terms of $f(t)$, C , $v_c(t)$ and ω .

ODE = _____

- (b) [3 pts] Determine the value of C = _____

- (c) [3 pts] Determine the value of ω = _____


(d) [4 pts] If $v_0 = 0\text{V}$, determine the value of $B =$ _____

(e) [4 pts] Determine steady-state current phasor $Y =$ _____

(f) [5 pts] If instead of $f(t) = \cos(\omega t) + 3\sin(\omega t)$ A, the input current source in this LTI system is given by $f_1(t) = 2\cos(\omega t - 1) + 6\sin(\omega t - 1)$ A, determine the steady-state response, $y_1(t)$.

$y_1(t) =$ _____

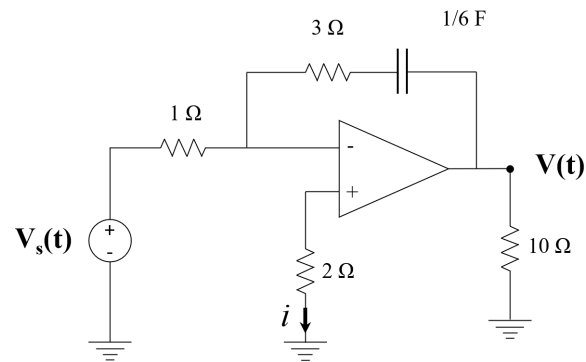2. (25 pts) The output voltage in the circuit below is given by $V(t) = 4\cos(2t)$. Using the phasor method and ideal op-amp approximations determine:



- (a) [18 pts] The input voltage $V_s(t)$ and express it in terms of real-valued functions only.

$$V_s(t) = \underline{\hspace{10cm}}$$


- (b) [3 pts] The current in the 2Ω resistor and express it in terms of real-valued functions only .

$$i_{2\Omega}(t) = \underline{\hspace{10cm}} .$$

- (c) [2 pts] The average absorbed power in the 1Ω resistor, $P_{1\Omega} = \underline{\hspace{5cm}}$

- (d) [2 pts] The average absorbed power in the capacitor, $P_C = \underline{\hspace{5cm}}$

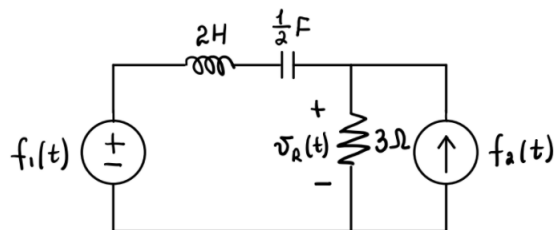3. (25 points) Consider the circuit below, where the output $y(t) = v_R(t)$.




- (a) [6 pts] Determine the frequency response $H_1(\omega)$, considering only the input voltage source, $f_1(t)$.

$$H_1(\omega) = \underline{\hspace{10cm}}$$

- (b) [5 pts] Determine the steady-state output voltage $v_{R_1}(t)$ given $f_1(t) = 3\cos(2t) + 2\sin\left(\frac{t}{2}\right)$ V.

$$v_{R_1}(t) = \underline{\hspace{10cm}}$$

Recall

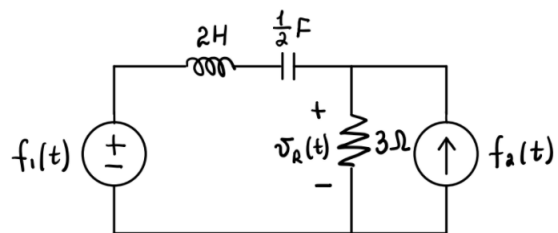

- (c) [6 pts] Determine the frequency response $H_2(\omega)$, considering only the input current source, $f_2(t)$.

$$H_2(\omega) = \underline{\hspace{10cm}}$$

- (d) [5 pts] Determine the steady-state output voltage $v_{R_2}(t)$ given $f_2(t) = 3 \cos(2t) + 2 \sin\left(\frac{t}{2}\right)$ A.

$$v_{R_2}(t) = \underline{\hspace{10cm}}$$

- (e) [3 pts] Determine the steady-state output voltage $v_R(t)$.

$$v_R(t) = \underline{\hspace{10cm}}$$

4. (25 points) The two parts of this problem are unrelated.

(a) Let the periodic signal $x(t)$ be defined over a period as

$$x(t) = \begin{cases} 2t + 4 & -2 < t \leq -1 \\ 2 & -1 < t \leq 1 \\ -2t + 4 & 1 < t \leq 2 \\ 0 & 2 < t \leq 4 \end{cases}$$

i. [2 pts] The period of $x(t)$ is $T =$ _____

ii. [3 pts] The average value of $x(t)$ is $x_{av} =$ _____

iii. [2 pts] Now let us define a different periodic signal $y(t) = dx(t)/dt$. Express $y(t)$ as a piecewise function like it is done for $x(t)$ above.

$y(t) =$ _____

- iv. [4 pts] Determine the Fourier coefficients Y_n for all n . You do not need to simplify.

$$Y_n = \underline{\hspace{4cm}}$$

- v. [4 pts] Use the derivative property to determine the Fourier coefficients X_n for all n .

$$X_n = \underline{\hspace{4cm}}$$

- (b) Consider the function $q(t) = 2\sin(2t) + 3\cos(4t)$,

- i. [2 pts] Its fundamental frequency is $\omega_0 = \underline{\hspace{4cm}}$

- ii. [5 pts] Express the function in exponential Fourier series form.

$$q(t) = \underline{\hspace{4cm}}$$

- iii. [3 pts] Its average power is $P_q = \underline{\hspace{4cm}}$

You may use this sheet for additional calculations but **do not** separate this sheet from the rest of the exam.

You may use this sheet for additional calculations but **do not** separate this sheet from the rest of the exam.

$f(t)$, period $T = \frac{2\pi}{\omega_o}$	Form	Coefficients
$\sum_{n=-\infty}^{\infty} F_n e^{jn\omega_o t}$	Exponential	$F_n = \frac{1}{T} \int_T f(t) e^{-jn\omega_o t} dt$
$\frac{a_o}{2} + \sum_{n=1}^{\infty} a_n \cos(n\omega_o t) + b_n \sin(n\omega_o t)$	Trigonometric	$a_n = F_n + F_{-n}$ $b_n = j(F_n - F_{-n})$
$\frac{c_o}{2} + \sum_{n=1}^{\infty} c_n \cos(n\omega_o t + \theta_n)$	Compact for real $f(t)$	$c_n = 2 F_n $ $\theta_n = \angle F_n$

Table 1: Fourier series forms.

	Name:	Condition:	Property:
1	Scaling	Constant K	$K f(t) \leftrightarrow K F_n$
2	Addition	$f(t) \leftrightarrow F_n, g(t) \leftrightarrow G_n, \dots$	$f(t) + g(t) + \dots \leftrightarrow F_n + G_n + \dots$
3	Time shift	Delay t_o	$f(t - t_o) \leftrightarrow F_n e^{-jn\omega_o t_o}$
4	Derivative	Continuous $f(t)$	$\frac{df}{dt} \leftrightarrow jn\omega_o F_n$
5	Hermitian	Real $f(t)$	$F_{-n} = F_n^*$
6	Even function	$f(-t) = f(t)$	$f(t) = \frac{a_o}{2} + \sum_{n=1}^{\infty} a_n \cos(n\omega_o t)$
7	Odd function	$f(-t) = -f(t)$	$f(t) = \sum_{n=1}^{\infty} b_n \sin(n\omega_o t)$
8	Average power		$P \equiv \frac{1}{T} \int_T f(t) ^2 dt = \sum_{n=-\infty}^{\infty} F_n ^2$

Table 2: Fourier series properties