

## Analog Signal Processing

Thursday, February 20, 8:45-10pm

## Exam I

<b>Full Name</b> <b>(First Last):</b> (all capital letters)	Solutions
---	-----------


<b>UIN:</b>		<b>netID:</b>	
-------------	--	---------------	--

<b>Course: (circle one)</b>  <b>Section to return exam: (circle one)</b>	ECE210  10AM	ECE211  11AM	ECE211  1PM	ECE211  2PM
--	--------------------	--------------------	-------------------	-------------------


<p>Clearly PRINT your name in CAPITAL LETTERS.</p> <p>This is a closed book and closed notes exam.</p> <p>Calculators are not allowed.</p> <p>To get full credit, please SHOW all your work and simplify your answers.</p> <p>Write your final answers in the spaces provided.</p> <p>All answers should INCLUDE UNITS whenever appropriate.</p> <p>The exam is printed <b>double-sided</b>.</p>	<p><b>DO NOT</b> write in these spaces.</p> <p>Problem 1 (25 points): _____</p> <p>Problem 2 (20 points): _____</p> <p>Problem 3 (30 points): _____</p> <p>Problem 4 (25 points): _____</p> <p>Total: (100 points): _____</p>
--	---

1. (25 pts) The two parts of this problem are unrelated.

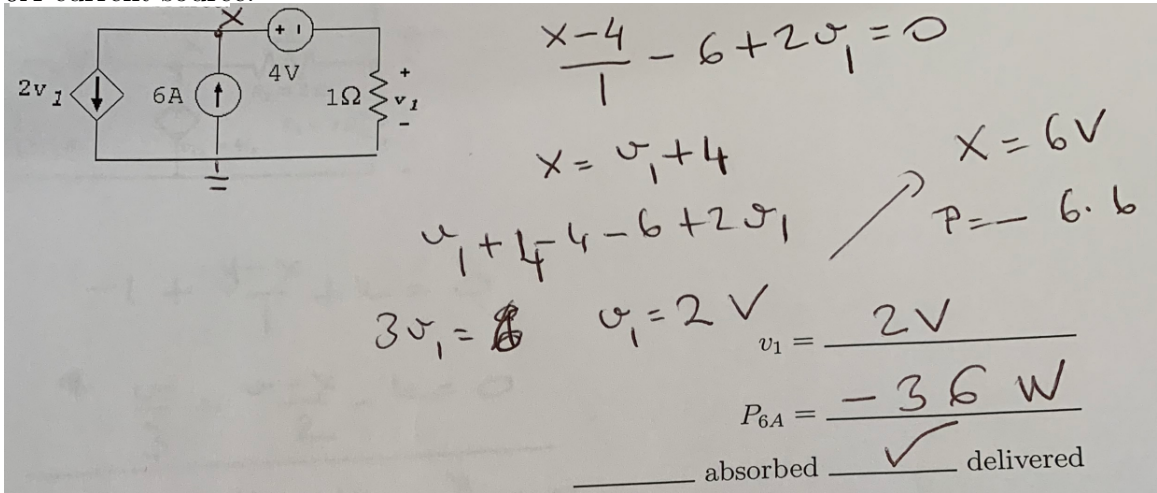- (a) [10 pts] For the circuit below, determine  $v_1$  and the power absorbed or delivered by the 6A current source.



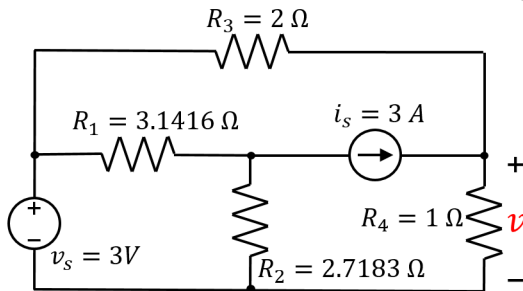- (b) [15 pts] Consider the circuit below. Use the superposition method to determine the constants  $k_1$  and  $k_2$  such that  $v = k_1 v_s + k_2 i_s$ .



Solution: Start from  $v = k_1 v_s + k_2 i_s$



- 1) Let  $v_s = 1V, i_s = 0A$ . The original circuit becomes sub-circuit a, where  $v = k_1$ .

According to voltage division,  $v = v_s \frac{R_4}{R_4 + R_3} = 1 \times \frac{1}{1+2} = \frac{1}{3} \Rightarrow k_1 = \frac{1}{3}$ .


- 2) Let  $v_s = 0V, i_s = 1A$ . The original circuit becomes sub-circuit b, where  $v = k_2$ .

According to current division (because  $R_3 || R_4$ ),  $i_4 = i_s \frac{R_3}{R_4 + R_3} = 1 \times \frac{2}{1+2} = \frac{2}{3}A$ .

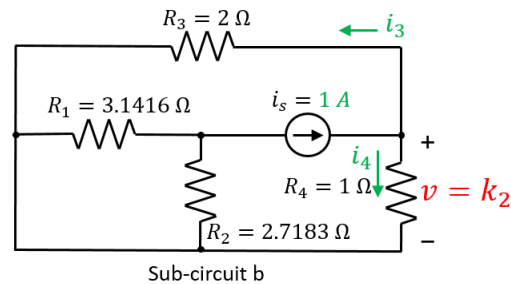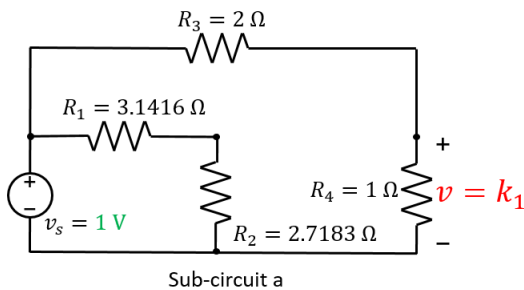$v = i_4 R_4 = \frac{2}{3}V \Rightarrow k_2 = \frac{2}{3}\Omega$



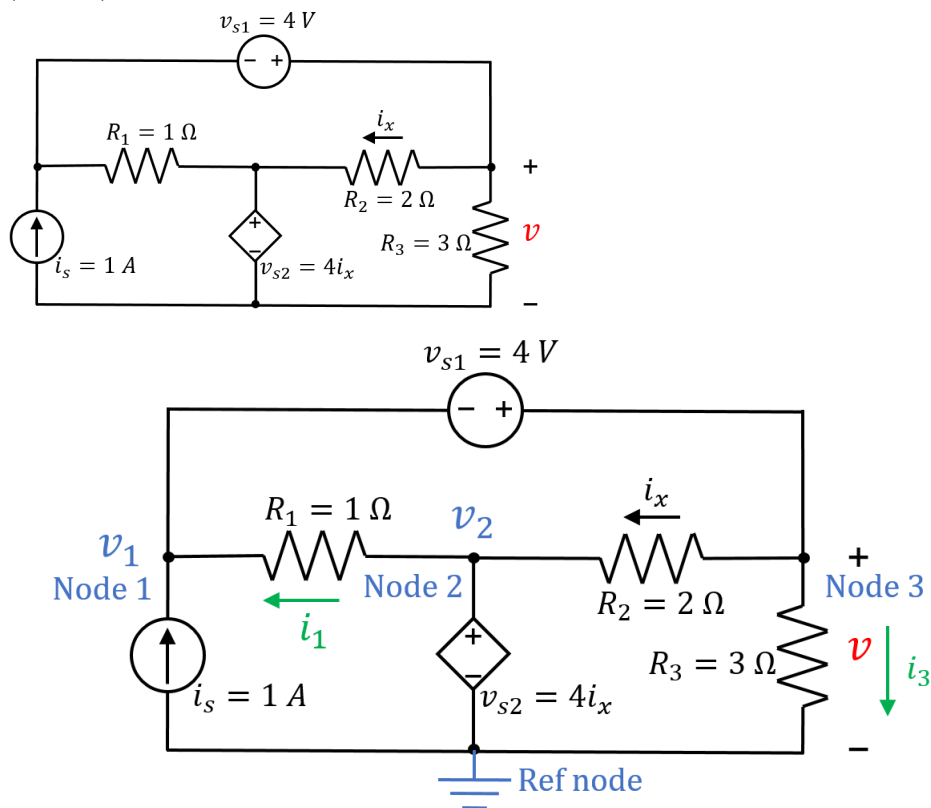2. (20 pts) Consider the circuit below. Use the node-voltage method to determine  $v$ .



Solution: 1) Choose the reference node, declare node voltage variables, and assign current directions to the resistors.

2) According to  $v_{s1} = 4\text{ V}$ , we obtain  $v_1 = v - 4$ .

3) According to  $v_{s2} = 4i_x$ , we obtain  $v_2 = 4i_x \Rightarrow v_2 = 4 \times \frac{v - v_2}{2} \Rightarrow v_2 = \frac{2}{3}v$

4) Nodes 1 and 3 form a super node. Applying KCL at this super node yields


$$i_s + i_1 = i_x + i_3 \Rightarrow 1 + \frac{v_2 - v_1}{1} = \frac{v_2}{4} + \frac{v}{3}$$

$$\Rightarrow 1 + \frac{2}{3}v - v + 4 = \frac{v}{6} + \frac{v}{3} \Rightarrow \boxed{v = 6\text{ V}}$$

$v =$  \_\_\_\_\_

3. (30 pts) The two parts of this problem are unrelated.

(a) [20] Consider the circuit below.

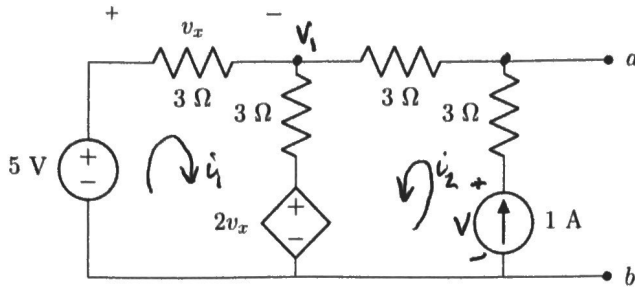

i. [10 pts] Determine the Thevenin equivalent voltage,  $V_T$ , between nodes  $a$  and  $b$ .

$$\begin{aligned} i_2 &= 1 \text{ A} \\ V_x &= 3i_1 \Rightarrow i_1 = \frac{V_x}{3} \\ 5 &= V_x + 3(i_1 + i_2) + 2V_x \\ 5 &= 3V_x + 3i_1 + 3i_2 \\ 5 &= 4V_x + 3(1) \\ 2 &= 4V_x \\ V_x &= \frac{1}{2} \text{ V} \\ i_1 &= \frac{1}{6} \text{ A} \end{aligned}$$


$$\begin{aligned} V_1 &= 5 - V_x \\ V_1 &= 4.5 \text{ V} \\ 1 &= \frac{V_T - V_1}{3} \\ 3 &= V_T - 4.5 \\ \boxed{V_T &= 7.5 \text{ V}} \end{aligned}$$

OR

$$\begin{aligned} V &= 3i_1 + 3i_2 + 3(i_1 + i_2) + 2V_x \\ V &= 3(1) + 3(1) + 3\left(\frac{1}{6} + 1\right) + 2\left(\frac{1}{2}\right) \\ V &= 7 + \frac{7}{2} = \frac{21}{2} \\ V_T &= V - 3i_2 \\ V_T &= \frac{21}{2} - 3 \\ \boxed{V_T &= \frac{15}{2} \text{ V}} \end{aligned}$$

$$V_T = \underline{7.5 \text{ V}}$$

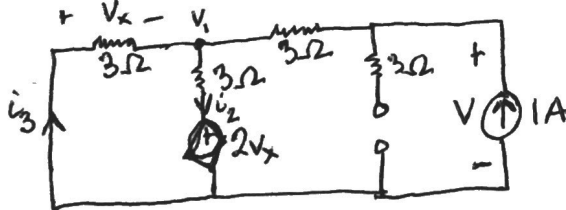ii. [10 pts] Determine the Thevenin equivalent resistance,  $R_T$ , between nodes  $a$  and  $b$ .




$$\begin{aligned} \frac{V - V_1}{3} &= 1 \text{ A} \\ \frac{V_1 - 2V_x}{3} &= i_2 \\ \frac{V_x}{3} &= i_3 \\ 1 + \frac{V_x}{3} &= \frac{V_1 - 2V_x}{3} \\ 3 + V_x &= V_1 - 2V_x \\ 3 + 3V_x &= V_1 \\ 3 + 3V_x &= -V_x \\ 3 &= -4V_x \\ V_x &= -\frac{3}{4} \text{ V} \end{aligned}$$

$$\begin{aligned} V_1 &= 0 - V_x \\ V_1 &= -V_x \\ V_1 &= \frac{3}{4} \text{ V} \end{aligned}$$

$$\begin{aligned} \frac{V - \frac{3}{4}}{3} &= 1 \\ V - \frac{3}{4} &= 3 \\ V &= \frac{15}{4} \text{ V} \\ R_T &= \frac{15/4}{1} \Rightarrow \boxed{R_T = \frac{15}{4} \Omega} \end{aligned}$$

$$R_T = \underline{\underline{\frac{15}{4} \Omega}}$$

(b) [10 pts] Consider the circuit below.

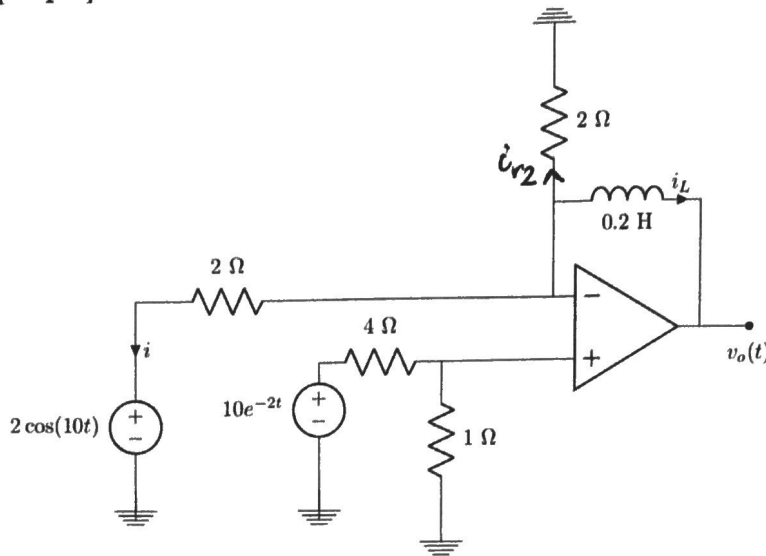

i. [07 pts] Determine the current through the inductor,  $i_L$ .

$$V_+ = \left(\frac{1}{4+1}\right) 10e^{-2t} \Rightarrow V_+ = \left(\frac{1}{5}\right) 10e^{-2t} \Rightarrow V_+ = 2e^{-2t} = V_-$$

$$\dot{v} = \frac{2e^{-2t} - 2\cos(10t)}{2} \Rightarrow \dot{v} = e^{-2t} - \cos(10t)$$

$$\dot{i}_{r2} = \frac{2e^{-2t} - 0}{2} \Rightarrow \dot{i}_{r2} = e^{-2t}$$

$$\dot{i}_L + \dot{i}_{r2} + \dot{v} = 0$$

$$\dot{i}_L = -\dot{v} - \dot{i}_{r2} \Rightarrow \dot{i}_L = \cos(10t) - e^{-2t} - e^{-2t}$$

$$\dot{i}_L = \cos(10t) - 2e^{-2t}$$

$$i_L = \cos(10t) - 2e^{-2t}$$

ii. [03 pts] Determine the output voltage,  $v_o$ .

$$V_L = V_- - V_o$$

$$V_L = L \frac{di_L}{dt}$$

$$V_o = V_- - V_L$$



$$V_o = 2e^{-2t} - 0.2(-10\sin(10t) + 4e^{-2t})$$

$$V_o = 2e^{-2t} + 2\sin(10t) - 0.8e^{-2t}$$

$$V_o = 2\sin(10t) + 1.2e^{-2t}$$

$$v_o = 2\sin(10t) + 1.2e^{-2t}$$

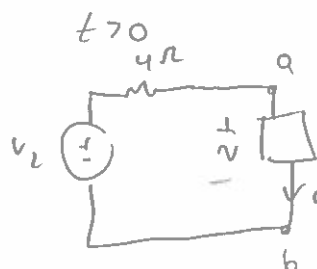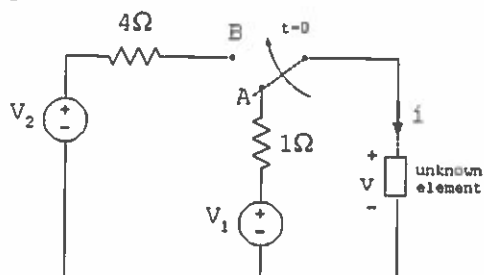4. (25 pts) Consider the circuit below. The switch is originally in position A it switches over to position B at time  $t = 0$ .



$$\Rightarrow R_T = 4\Omega$$

- (a) [03 pts] If it is known that that  $v(0^-) = 5V$ ,  $i(0^-) = 5A$ ,  $v(0^+) = 4V$  and  $i(0^+) = 4A$ , is the unknown element a resistor, an inductor or a capacitor? Explain why.

☒ resistor ☐ inductor ☐ capacitor

Explain:   
 In capacitor  $v_c(0^-) = v_c(0^+)$   
 In inductor  $i_L(0^-) = i_L(0^+)$   
 In resistor, no such restrictions

- (b) [06 pts] If the unknown element is an inductor, and it is known that  $v(1) = -20e^{-2}V$ , determine the value of the inductance,  $L$ .

$$i_L(t) = B + Ae^{-t/\tau}$$

$$v_L(t) = L \frac{di_L}{dt} = LA \left(-\frac{1}{\tau}\right) e^{-t/\tau}$$

$$v_L(1) = -\frac{LA}{\tau} e^{-1/\tau} = -20e^{-2}$$

$$\Rightarrow \frac{1}{\tau} = 2 \Rightarrow \frac{1}{\tau} = \tau = \frac{L}{R_T} = \frac{L}{4}$$

$$\Rightarrow L = 2$$

$$L = 2H$$

- (c) [16 pts] Assume the unknown element is a 0.01F capacitor and that the switch was in position A for a long time. Determine the constants  $a$ ,  $K_1$ ,  $K_2$  and  $K_3$ , such that  $v(t) = K_1 + K_2e^{-at} + K_3t$ , for  $t > 0$ . You may leave your answers in terms of  $V_1$  and  $V_2$ .

$$v_c(t) = B + Ae^{-t/\tau} \Rightarrow K_3 = 0$$

$$v_c(\infty) = B = V_2 \text{ (see } t_{cp})$$

$$= K_1$$

$$v_c(0^-) = v_c(0^+) = B + A = V_2 + A = V_1 \text{ (see } t_{cp})$$

$$\Rightarrow A = V_1 - V_2 = K_2$$

$$\tau = R_T C = 4(0.01) = \frac{4}{100} = \frac{1}{25}$$

$$a = \frac{1}{\tau} \Rightarrow a = 25$$

$$K_1 = V_2$$

$$K_2 = V_1 - V_2$$

$$K_3 = 0$$

$$a = 25$$