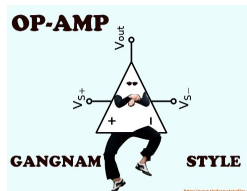


ECE 210 (AL2) - ECE 211 (E)

## Chapter 3

### Circuits for Signal Processing



Olga Mironenko  
University of Illinois  
Spring 2022


# Chapter objectives

- Apply ideal op-amp approximation to do signal processing
- Understand zero-input and zero-state responses
- Understand what is linearity and how to test if a system is linear
- Understand what is time-invariance and how to test if system is TI
- Analyze first order RC and RL circuits with constant inputs:
  - How to obtain particular and homogeneous solutions
  - How to obtain zero-state and zero-input solutions
  - How to obtain transient and steady-state solutions
  - Understand the effect of the time-constant in the solution
- Analyze first order RC, RL circuits with time-varying inputs
  - How to obtain particular and homogeneous solutions
  - How to obtain zero-state and zero-input solutions
  - How to obtain transient and steady-state solutions
- Be familiar with  $n$ -th order LTI systems


- Circuits for signal processing

- Addition
- Subtraction
- Amplification
- Differentiation
- Integration
- Etc.

- Operational amplifier (op-amp)

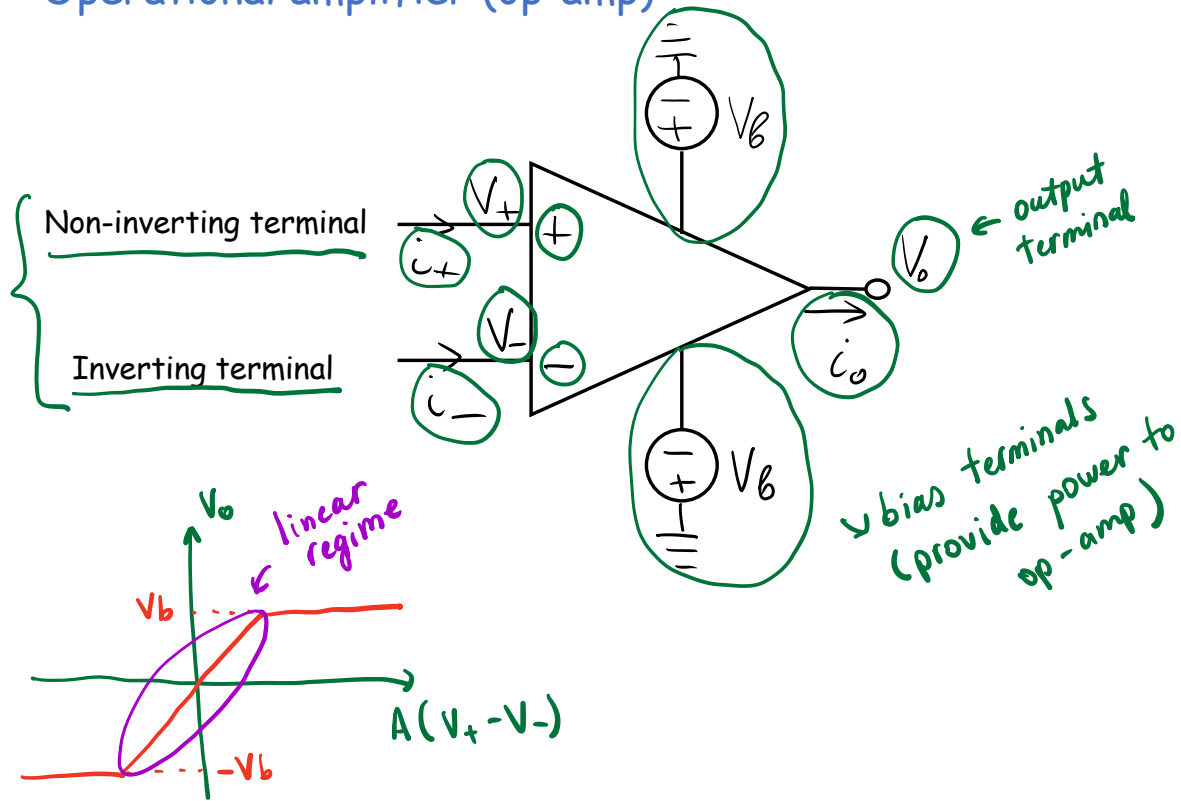

- Op-amp in the linear regime

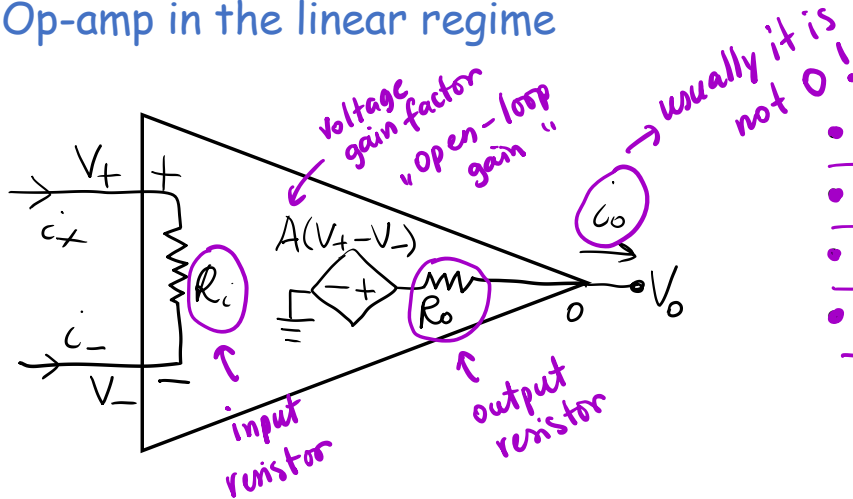


- $|V_+ - V_-| \ll (< 10\mu V)$
- $R_i \gg (> 10^6 \Omega)$
- $R_o \ll (< 10 \Omega)$
- $A \gg (> 10^6)$

ideal op-amp approximation:

$i_+ = i_- = 0$	$\rightarrow$ within pA $10^{-12}$
$V_+ = V_-$	$\rightarrow$ within $\mu V$

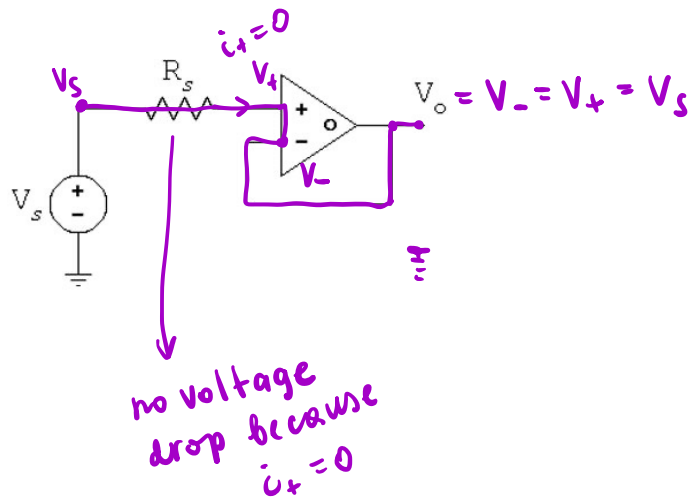- Example #1: voltage follower

- Obtain  $V_o$  in the following circuit assuming the ideal op-amp approximation




$$V_+ = V_-$$

$$i_+ = i_- = 0$$

## • Example #1-cont: voltage follower

- If  $V_o = V_s$ , why use the op-amp?


Consider attaching a load:

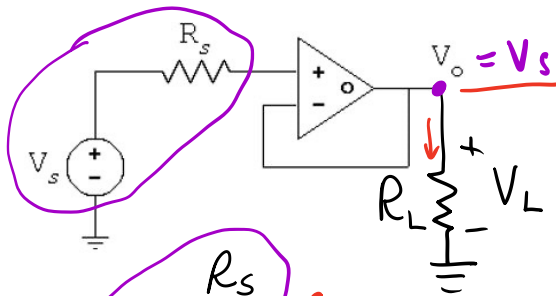

$$P_L = \frac{V_L^2}{R_L} = \frac{V_s^2}{R_L}$$

← full voltage from the source across the load

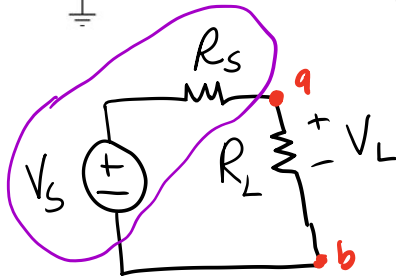↓ op-amp acts as a buffer between a source and a load




↑ less power :-

$$P_L = \frac{V_L^2}{R_L} = \frac{1}{R_L} \cdot \left( V_s \frac{R_L}{R_L + R_s} \right)^2 = \frac{V_s^2}{R_L} \underbrace{\left( \frac{R_L^2}{(R_L + R_s)^2} \right)}_{< 1}$$

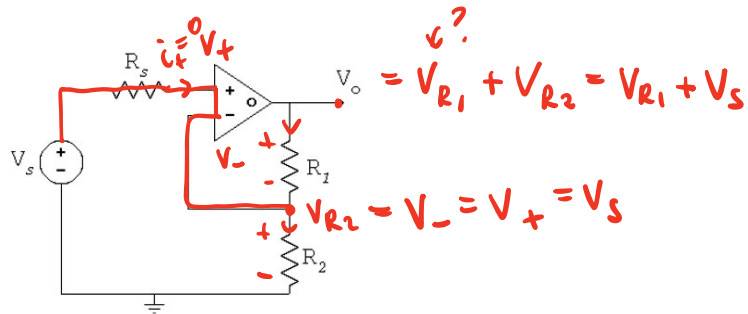• Example #2: non-inverting amplifier

- Obtain  $V_o$  in the following circuit assuming the ideal op-amp approximation



$$\begin{aligned} V_+ &= V_- \\ i_+ &= i_- = 0 \end{aligned}$$