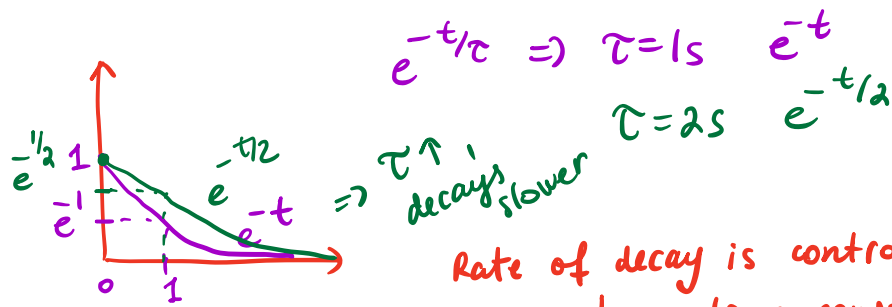


• Time-constant


• Recall

$$y(t) = \frac{K}{a} + \left(y(0^+) - \frac{K}{a}\right) e^{-at}$$



Rate of decay is controlled by a time constant

$$\tau = RC \text{ [s]}$$

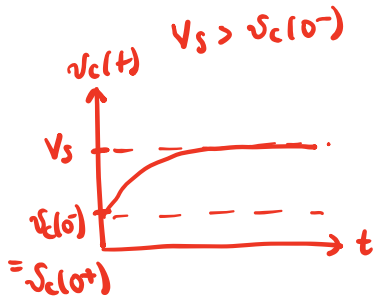


$$v_c(t) = \underbrace{(v_c(0^-) - V_s)}_{\text{transient response}} e^{-\frac{t}{RC}} + \underbrace{V_s}_{\text{steady-state response}}$$

transient response

steady-state response

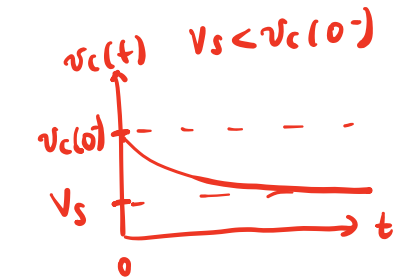(part which goes to 0 when $t \rightarrow \infty$) (which is left after transient response has vanished)



- Simple solution method (short cut) *only works for 1st order ODE with constant coefficients and constant inputs*

• Recall

$$i_c = C \frac{dv_c}{dt}$$

↓

at the steady state ($t \rightarrow \infty$)

cap. acts

as open-circuit

($i_c = 0$)

$$y(t) = B + Ae^{-\frac{t}{\tau}}$$

$$v_c(t) = B + Ae^{-t/\tau}$$

$$a = \frac{1}{RC} = \frac{1}{\tau}$$


Need to evaluate:

$$\bullet v_c(\infty) = B + Ae^{+\infty/\tau} = B = V_s$$

$$\bullet v_c(0^+) = v_c(0^-) = B + Ae^{-0/\tau} = B + A$$

if $t=0$

$$A = v_c(0^-) - B = v_c(0^-) - V_s$$

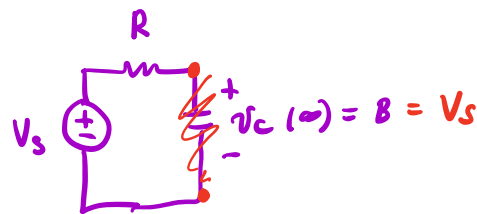


$$v_c(t) = V_s + (v_c(0^-) - V_s)e^{-t/\tau}$$

← same equation :-

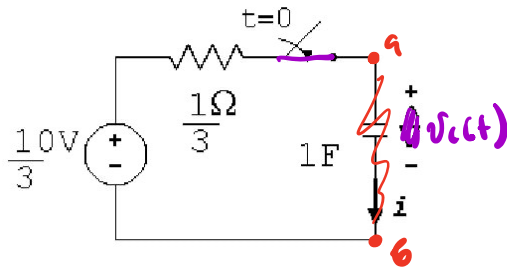• Example #14:

- Consider the following circuit with $V_c(0^-) = 1V$.
- Determine $V_c(t)$ for $t > 0$



- I.C.

$t > 0$? ? $-t/\tau$?

$$v_c(t) = B + A e^{-t/\tau}$$

$$v_c(\infty) = B = \frac{10}{3} V$$

$$v_c(0^-) = B + A \Rightarrow$$


$$1 = \frac{10}{3} + A \Rightarrow A = \left(1 - \frac{10}{3}\right) = -\frac{7}{3}$$

$$\tau = RC = \frac{1}{3} s$$

$$v_c(t) = \frac{10}{3} - \frac{7}{3} e^{-3t} V$$

- General RC circuits

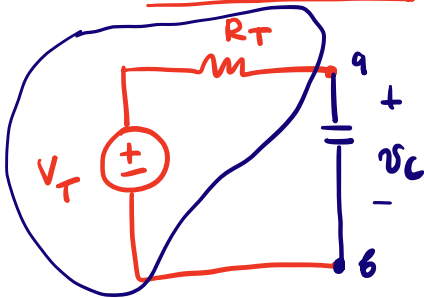- If a resistive circuit with a single capacitor:



↑
Thevenin's eq.
circuit as seen
by the capacitor

$$v_C(t) = V_T + (v_C(0^-) - V_T) e^{-t/\tau}$$

$$\tau = R_T C$$

$$v_C(\infty) = B = V_T$$

$$v_C(0^-) = B + A$$

- Zero-input (ZI), zero-state (ZS)

$$y(t) = y_{zs}(t) + y_{zi}(t)$$

- Recall

$$\frac{dy}{dt} + ay = k$$

↑
input

$$y(t) = \underbrace{\frac{K}{a}}_{y_p} + \underbrace{\left(y(0^+) - \frac{K}{a}\right)}_{y_h} e^{-at} =$$

$$= \frac{k}{a} + \cancel{y(0^+) e^{-at}} - \frac{k}{a} e^{-at}$$

z-s response



$$y_{zs}(t) = \frac{k}{a} - \frac{k}{a} e^{-at}$$

$$y_{zi}(t) = y(0^+) e^{-at}$$

• Example #15:

- Consider the circuit below.
- Assume the switch has been in position A for a long time and it switches to position B at time $t = 0$

- Determine $V_{ZS}(t)$ and $V_{ZI}(t)$

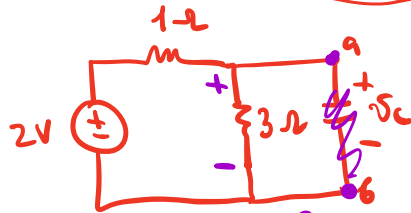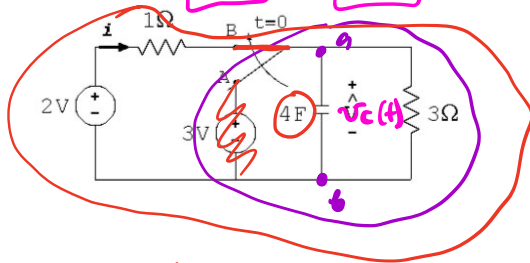

$$v_c(\infty) = B = 2 \left(\frac{3}{3+1} \right) = \frac{3}{2}$$

$$v_c(0^+) = v_c(0^-) = B + A \Rightarrow$$

$$A = (v_c(0^-) - \frac{3}{2})$$

" we are in DC steady-state


$t < 0$

$$v_c(0^-) = 3V$$

$t > 0$? ? $-t/\tau$?



$$v_c(t) = B + A e^{-t/\tau}$$

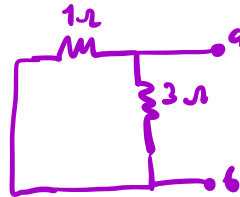Find τ : $\tau = R_{\text{eq}} C = \frac{3}{4} \cdot 4 = 3s$



$$R_{\text{eq}} = R_{\tau} = \frac{1 \cdot 3}{1+3} = \frac{3}{4} \Omega$$

• Example #15-cont:

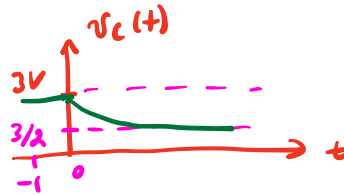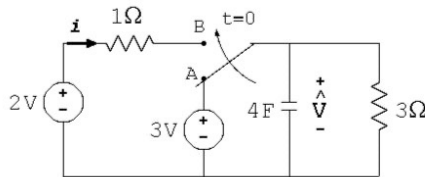

$$v_c(t) = B + A e^{-t/\tau} = \frac{3}{2} + (v_c(0^-) - \frac{3}{2}) e^{-t/3} = \frac{3}{2} + v_c(0^-) e^{-t/3} - \frac{3}{2} e^{-t/3}$$

$$\begin{aligned} v_{zs}(t) &= \frac{3}{2} - \frac{3}{2} e^{-t/3} \text{ V} \\ + v_{zs}(t) &= v_c(0^-) e^{-t/3} = 3 e^{-t/3} \text{ V} \Rightarrow v_c(t) = \frac{3}{2} - \frac{3}{2} e^{-t/3} + 3 e^{-t/3} \\ &= \frac{3}{2} + \underbrace{\frac{3}{2} e^{-t/3}}_{\text{"0" when } t \rightarrow \infty} \text{ V} \end{aligned}$$