
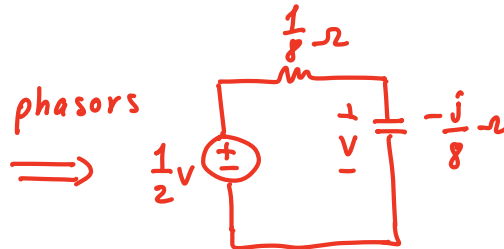


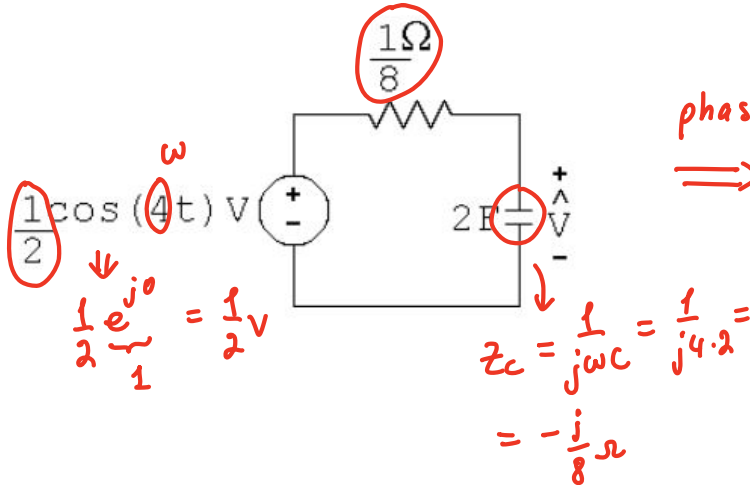- Example #4-cont.

- Determine $\widehat{v_{ss}}(t)$ using phasors:



Voltage division:


$$\begin{aligned}
 \hat{V} &= \frac{1}{2} \left(\frac{-j/8}{-j/8 + 1/8} \right) = \\
 &= \frac{1}{2} \left(\frac{-j}{1-j} \right) = \frac{1}{2} \frac{e^{-j\pi/2}}{\sqrt{1^2 + (-1)^2} e^{-j\pi/4}} = \\
 &= \frac{1}{2\sqrt{2}} e^{-j\pi/4} \text{ V}
 \end{aligned}$$

$$\widehat{v_{ss}}(t) = \frac{1}{2\sqrt{2}} \cos(4t - \pi/4) \text{ V}$$

same as before ~

• Example #6

- Determine $i_{ss}(t)$ using phasors:

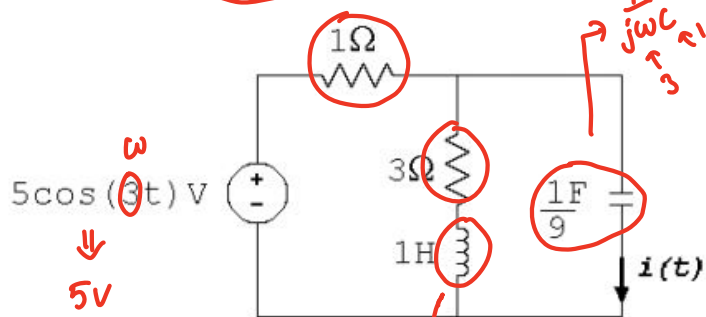


$$j\omega L = j \cdot 3 \cdot 1 = j3\Omega$$

$$Z_p = \frac{3(1+j)}{3+j4}$$

$$\frac{1}{j\omega C} = \frac{3}{j} = -j3\Omega$$

phasors

\Rightarrow

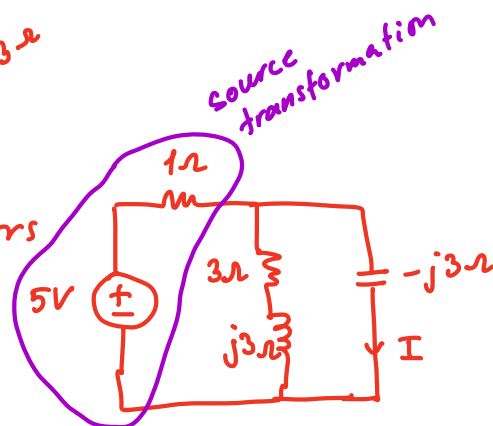

\Downarrow


current division:

$$I = 5 \left(\frac{Z_p}{-j3} \right) = \sqrt{2} e^{j\left(\frac{3\pi}{4} - \tan^{-1}\left(\frac{4}{3}\right)\right)} \text{ A}$$

$$i_{ss}(t) = \sqrt{2} \cos\left(3t + \frac{3\pi}{4} - \tan^{-1}\left(\frac{4}{3}\right)\right) \text{ A}$$

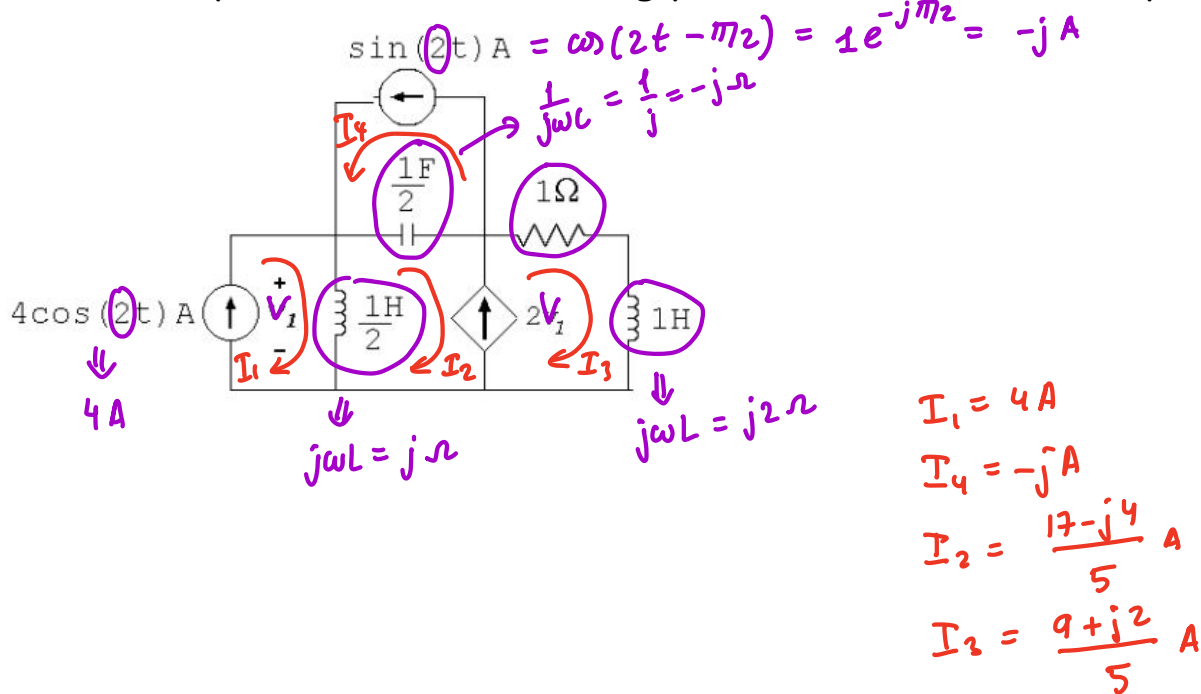
• Example #7

- Use the loop-current method using phasors to obtain the loop currents:



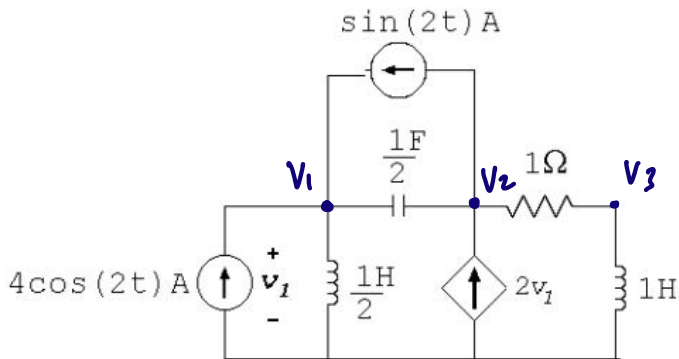• Example #7-cont

- Use the node-voltage method using phasors to obtain the node voltages:



$$V_1 = \frac{3+j4}{1-5j} \text{ V}$$


$$V_2 = 1+j4 \text{ V}$$

$$V_3 = -\frac{4+j8}{5} \text{ V}$$

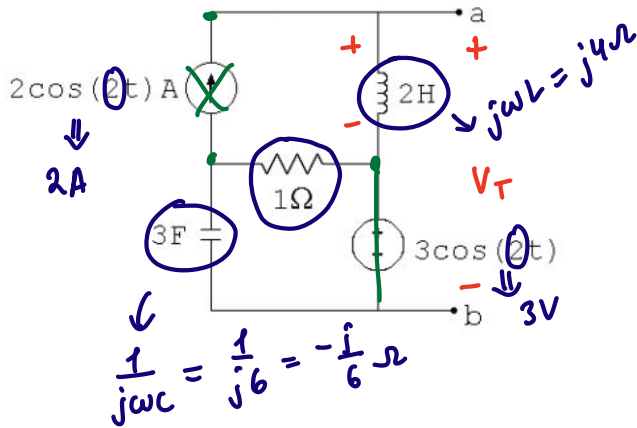Example #8

- Determine V_T , I_N and Z_T in phasors:

→ Thevenin's impedance $Z_T = R_T + jX_T$



Get V_T :

$$\begin{aligned} V_T &= V_{j4} + 3 = \\ &= 2(j4) + 3 = \\ &= 3 + j8 V \end{aligned}$$

Get Z_T :

$$Z_T = j4\Omega$$


Get I_N :

$$I_N = \frac{V_T}{Z_T} = \frac{3 + j8}{j4} A$$

- Average power

- Recall that absorbed power is

$$P = VI$$

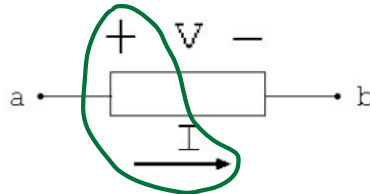

- If v and i are time-varying, then the instantaneous power is

$$p(t) = v(t)i(t)$$

- For periodic signals with period T , the average absorbed power is

$$P = \underbrace{\left(\frac{1}{T} \int_T p(t) dt \right)}_{\text{average}} = \underbrace{\frac{1}{T} \int_T v(t)i(t) dt}_{\text{average}}$$

- Average power for phasors

$$\operatorname{Re}\{z\} = \frac{z+z^*}{2}$$

$$P = \frac{1}{T} \int_T p(t) dt = \frac{1}{T} \int_T v(t)i(t) dt$$

$$\text{Recall: } v(t) = \operatorname{Re}\{V e^{j\omega t}\} = \frac{V e^{j\omega t} + (V e^{j\omega t})^*}{2} = \frac{V e^{j\omega t} + V^* e^{-j\omega t}}{2}$$

$$i(t) = \operatorname{Re}\{I e^{j\omega t}\} = \frac{I e^{j\omega t} + (I e^{j\omega t})^*}{2} = \frac{I e^{j\omega t} + I^* e^{-j\omega t}}{2}$$

$$v(t)i(t) = \left(\frac{V e^{j\omega t} + V^* e^{-j\omega t}}{2} \right) \left(\frac{I e^{j\omega t} + I^* e^{-j\omega t}}{2} \right) =$$

$$= \frac{1}{4} \left(V I e^{j2\omega t} + V I^* + V^* I + V^* I^* e^{-j2\omega t} \right) =$$

$$= \frac{1}{2} \left(\frac{V I e^{j2\omega t} + (V I e^{j2\omega t})^*}{2} + \frac{V I^* + (V I^*)^*}{2} \right) =$$

$$= \frac{1}{2} \left(\operatorname{Re}\{V I e^{j2\omega t}\} + \operatorname{Re}\{V I^*\} \right)$$

- Average power for phasors-cont

$$\begin{aligned}
 P &= \frac{1}{T} \int_T p(t) dt = \frac{1}{T} \int_T v(t) i(t) dt \\
 P &= \frac{1}{T} \int_T \left(\frac{1}{2} (\operatorname{Re} \{ V I e^{j2\omega t} \} + \operatorname{Re} \{ V I^* \}) \right) dt = \frac{1}{2T} \operatorname{Re} \{ V I^* \} \int_T dt = \frac{1}{2} \operatorname{Re} \{ V I^* \} \\
 &= \frac{1}{2} \cdot \frac{1}{T} \int_T \operatorname{Re} \{ \underbrace{V I e^{j2\omega t}}_{\text{phasor}} \} dt + \frac{1}{2} \cdot \frac{1}{T} \int_T \operatorname{Re} \{ V I^* \} dt = \\
 &= \frac{1}{2} \cdot \frac{1}{T} \int_T |V I| \cos(2\omega t + \angle V I) dt + \frac{1}{2} \operatorname{Re} \{ V I^* \}
 \end{aligned}$$


underbrace average of a cosine over 2 cycles is 0

$$P = \frac{1}{2} \operatorname{Re} \{ V I^* \}$$

← average power is purely real! (no j!)

- Average absorbed power

- Resistor

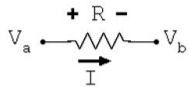

$$p = \frac{1}{2} \operatorname{Re} \{ \overset{R \cdot I}{V I^*} \} = \frac{1}{2} \operatorname{Re} \{ R \cdot \underbrace{I \cdot I^*}_{|I|^2} \} =$$

$$= \frac{R}{2} \operatorname{Re} \{ |I|^2 \} =$$

$$p = \left(\frac{1}{2} R |I|^2 \right) = \frac{1}{2} \frac{|V|^2}{R}$$

for DC:


$$p = R \cdot I^2$$

$$I_{\text{rms}} = \frac{|I|}{\sqrt{2}}$$

$$V_{\text{rms}} = \frac{|V|}{\sqrt{2}}$$

$$p = I_{\text{rms}}^2 \cdot R = \frac{V_{\text{rms}}^2}{R}$$

- Inductor

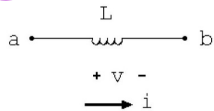

$$p = \frac{1}{2} \operatorname{Re} \{ \overset{j\omega L \cdot I}{V I^*} \} = \frac{1}{2} \operatorname{Re} \{ j\omega L \cdot \underbrace{I \cdot I^*}_{|I|^2} \} =$$

$$= \frac{1}{2} \omega L |I|^2 \operatorname{Re} \{ j \} = \underline{0W} !$$

- Capacitor

$$\underline{p = 0W} !$$

$$z \cdot z^* = |z|^2$$