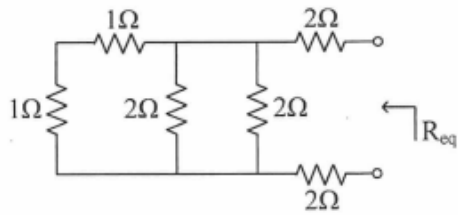



### Problem 1

(a) Find the  $R_{eq}$  in the following circuit.



$$R_{eq} = \underline{\hspace{2cm}}$$

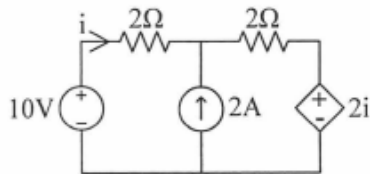(b) In the following circuit, find  $i$  and the power absorbed or delivered by  $2i$  dependent source.



$$i = \underline{\hspace{2cm}}$$

$$P = \underline{\hspace{2cm}}$$

Absorbed        Delivered       


### Problem 1 (25 points)

(a) (4 pts) A complex number  $Z$  is given as

(i)  $Z = (1 + j)^3$  find  $|Z| = \underline{\hspace{2cm}}$   $\angle Z = \underline{\hspace{2cm}}$


(ii)  $Z = (1 - j)e^{-j\pi/4}$  find  $|Z| = \underline{\hspace{2cm}}$   $\angle Z = \underline{\hspace{2cm}}$

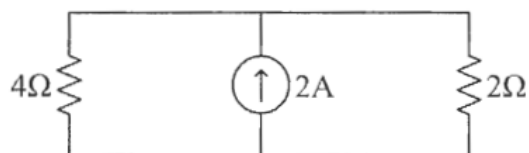(d) (5 pts) In the following circuit, how much power is supplied by 2A source.



P = \_\_\_\_\_

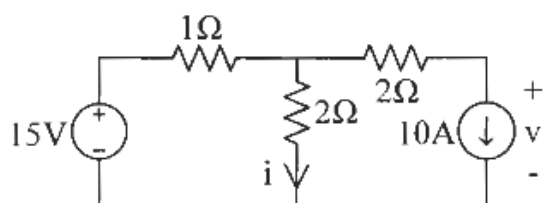
(a) In the following circuit, find  $v$  and  $i$ .



$v =$  \_\_\_\_\_


$i =$  \_\_\_\_\_

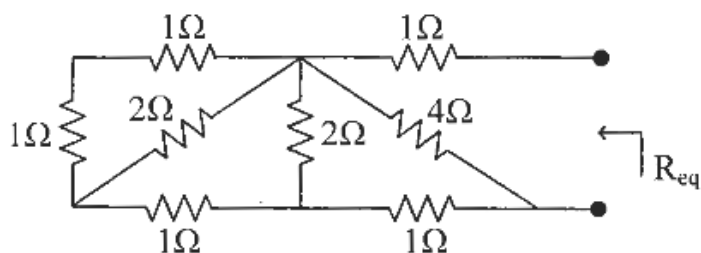(b) Find  $R_{eq}$  in the following circuit.



$R_{eq} =$  \_\_\_\_\_

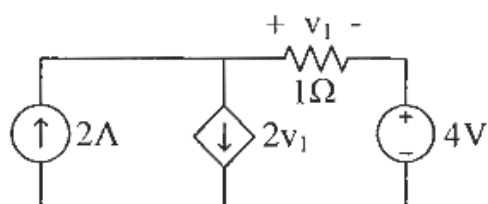(c) For the circuit below, find  $v_1$  and the power, absorbed or delivered by 4V source.




$v_1 =$  \_\_\_\_\_

P = \_\_\_\_\_

absorbed \_\_\_\_\_ delivered \_\_\_\_\_

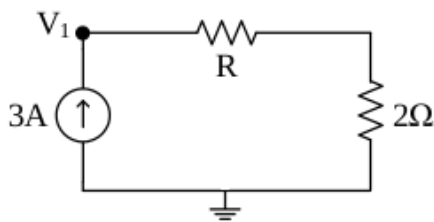
- (a) Consider the circuit below. Determine the value of the resistance  $R$  and of the node voltage  $V_1$  if the absorbed power by that resistor  $R$  is  $3W$ .



$$R = \underline{\hspace{2cm}}$$

$$V_1 = \underline{\hspace{2cm}}$$

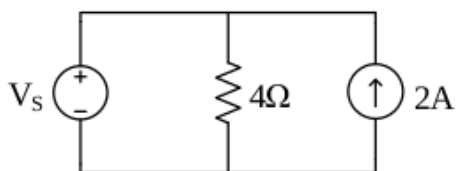- (b) Consider the circuit below. Determine the value of  $V_s$  and the absorbed power at the voltage source if the absorbed power at the current source is  $6W$ . (indicate if this power is absorbed or injected)



$$V_s = \underline{\hspace{2cm}}$$

$$P_s = \underline{\hspace{2cm}}$$

☐ absorbed    ☐ injected

- (c) Determine the magnitude and phase of the complex number  $Z = 2 + j6 + (1 + j)^6$ .

$$|Z| = \underline{\hspace{2cm}}$$

$$\angle Z = \underline{\hspace{2cm}}$$