

## Lecture 23, Monday, February 28, 2022

- *Resonance*: possible existence of steady-state co-sinusoidal oscillations without sources..

– RLC in parallel

\* Has resonant frequency  $\omega_0 = \frac{1}{\sqrt{LC}}$

\* At  $\omega_0$ ,


$$\cdot Z_L = -Z_C \rightarrow Z_L \parallel Z_C = \infty$$

parallel combination of L and C is like an open circuit

$$\rightarrow I_C + I_L = 0 \rightarrow I_C = -I_L \neq 0$$

$$\rightarrow I_R = I_s$$

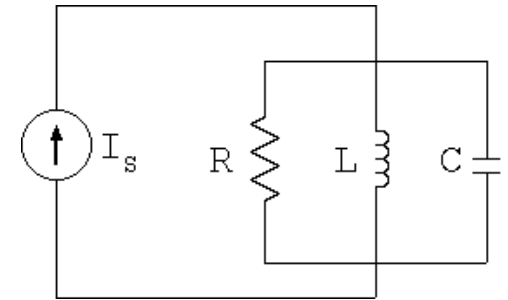• Get maximum voltage in circuit:  $V = RI_s$



- Frequency response of LTI systems:  $H(\omega)$

$$f(t) = |F| \cos(\omega t + \angle F) \rightarrow \boxed{H(\omega)} \rightarrow y(t) = \underbrace{|F||H(\omega)|}_{=|Y|} \cos\left(\omega t + \underbrace{\angle F + \angle H(\omega)}_{=\angle Y}\right)$$

•  $|H(\omega)|$  is called the magnitude (or amplitude) response of the LTI system:

$$|Y| = |F||H(\omega)|$$

the amplitude of the input gets multiplied by the amplitude response at the corresponding frequency.

- $\angle H(\omega)$  is called the phase response of the LTI system:

$$\angle Y = \angle F + \angle H(\omega)$$

the phase of the input gets shifted by the phase response at the corresponding frequency.

- It works the same way for sine functions:

$$f(t) = |F| \sin(\omega t + \angle F) \rightarrow \boxed{H(\omega)} \rightarrow y(t) = \underbrace{|F||H(\omega)|}_{=|Y|} \sin \left( \omega t + \underbrace{\angle F + \angle H(\omega)}_{=\angle Y} \right)$$