

## Lecture 22, Friday, February 25, 2022

- Available power

- In an RLC circuit with Thevenin voltage  $V_T$  and Thevenin impedance  $Z_T$ , the available power is

$$P_a = \frac{|V_T|^2}{8R_T}$$

*Important:* take the magnitude before squaring, and  $R_T = \text{Re}\{Z_T\}$  only.

- This maximum power is achievable only if the load impedance is the matched load:

$$Z_L = Z_T^* = R_T - jX_T$$

- *Resonance:* possible existence of steady-state co-sinusoidal oscillations without sources..

- RLC in series

- \* Has resonant frequency  $\omega_0 = \frac{1}{\sqrt{LC}}$

- \* At  $\omega_0$ ,

- $Z_L = -Z_c \rightarrow Z_L + Z_c = 0$

series combination of L and C is like a short circuit

$$\rightarrow V_c + V_L = 0 \rightarrow V_c = -V_L \neq 0$$

$$\rightarrow V_R = V_i$$

- Get maximum current in circuit:  $I = \frac{V_i}{R}$

