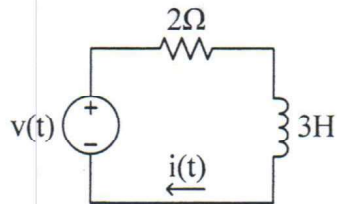



Problem 3

- (a) The circuit below has frequency response $H(\omega) = \frac{I}{V}$.



- i) Determine $H(\omega)$: _____
- ii) Determine the maximum value for $|H(\omega)|$: _____

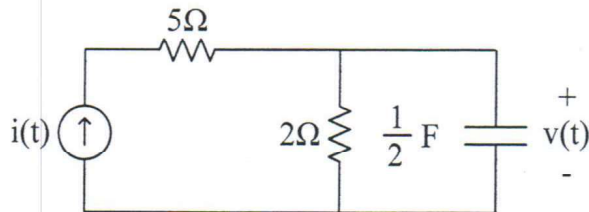- (b) The circuit below has frequency response $H(\omega) = \frac{V}{I}$.



- i) Determine $H(\omega)$: _____
- ii) Determine $|H(\omega)|$ as $\omega \rightarrow \infty$: _____
- iii) Determine $\angle H(\omega)$ as $\omega \rightarrow \infty$: _____

(c) An LTI system with input $f(t)$ and output $y(t)$ is described by the ODE

$$\frac{d^2y}{dt^2} + 2\frac{dy}{dt} + 3y(t) = f(t)$$

The frequency response for the system $H(\omega) = \frac{Y}{F}$.

i) Determine $H(\omega)$: _____


ii) Determine the value of ω ($\omega > 0$) such that $\angle H(\omega) = -\frac{\pi}{4}$: _____

10 Fall Exam 2

1. Problem 1 (25 points)

These problems are intended to be quick and easy:

(a) For the following circuit.

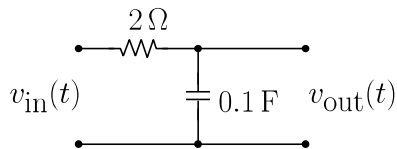

(3 pt)

i. Find the frequency response $H(\omega)$.

(1 pt)


ii. Is $H(\omega)$ the frequency response of a high pass, low pass or a band pass filter?

(3 pt)

iii. If $v_{in}(t) = 2 + \cos(5t + \frac{\pi}{4})$, then $v_{out}(t) = ?$

(2 pt)

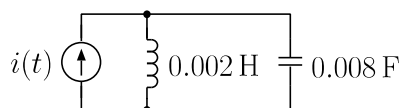
(b) What is the resonance frequency of the following circuit.



Problem 3 (25 points)

All parts of this problem are independent.

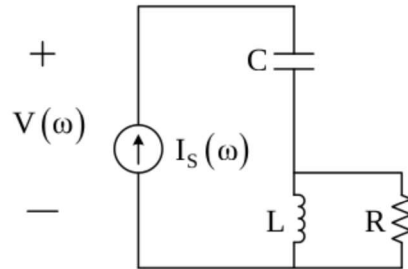- a) (5 points) In the circuit below, $H(\omega) = V(\omega)/I_S(\omega)$. Find $H(\omega)$. Your answer may include the variables, R, C, L and ω .



$$H(\omega) = \underline{\hspace{2cm}}$$

- b) A particular circuit is characterized by $H(\omega) = \frac{15j\omega}{25j\omega + (1 - \omega^2 64)}$

- i) (4points) What is the frequency ω_p , at which $|H(\omega)|$ is maximum?

$$\omega_p = \underline{\hspace{2cm}}$$

- ii) (4 points) What is $|H(\omega_p)|$?

$$|H(\omega_p)| = \underline{\hspace{2cm}}$$

Problem 3 (continued)

c) A circuit has input $f(t)$, output $y(t)$, and frequency response $H(\omega)$ given by

$$H(\omega) = \frac{a + j\omega b}{c + j\omega d}$$

You may answer each of the following sub-parts in terms of the variables a , b , c , and d if you wish. You may assume that a , b , c , and d are all positive real constants.

i) (4 points) If $f(t) = 6 \cos(35t)$, then $y(t) = A \cos(35t + \theta)$ for what value of A ?

$A =$ _____

ii) (4 points) If $f(t) = 6 \cos(35t)$, then $y(t) = A \cos(35t + \theta)$ for what value of θ ?


$\theta =$ _____

iii) (4 points) If $f(t) = 10$, what is $y(t)$?

$y(t) =$ _____

Problem 3

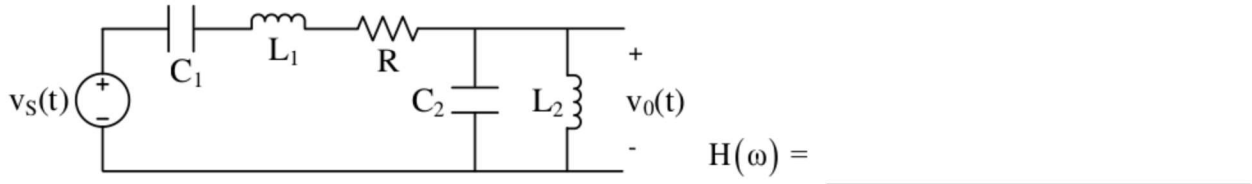- (a) Determine the frequency response $H(\omega) = \frac{V_o(\omega)}{V_s(\omega)}$ of the following circuit. Give the answer in terms of ω , C_1 , C_2 , L_1 , L_2 and R . Do not simplify your answer.



- (b) A linear system with the input $f(t)$ and output $y(t)$ is described by ODE

$$3 \frac{d^2 y}{dt^2} + 2 \frac{dy}{dt} + y(t) = 2 \frac{df}{dt} + f(t)$$

Determine the frequency response $H(\omega) = \frac{Y(\omega)}{F(\omega)}$ of the system.

$$H(\omega) =$$

- (c) Given an input $f(t) = 2 \cos \omega_1 t + \sin(\omega_2 t + \theta_2)$ and $H(\omega) = \frac{1 + j\omega}{2 + j\omega}$ determine the steady-state response $y_{ss}(t)$ of the system $H(\omega)$.

$$y_{ss}(t) =$$
