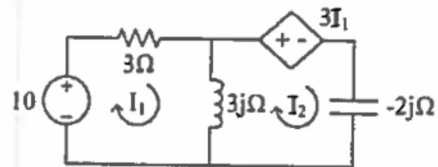


Sp 2013

**Problem 2**


(a) In the following circuit, write two loop equations in terms of  $I_1$  and  $I_2$ .



$$(\quad) I_1 + (\quad) I_2 = (\quad)$$

$$(\quad) I_1 + (\quad) I_2 = (\quad)$$

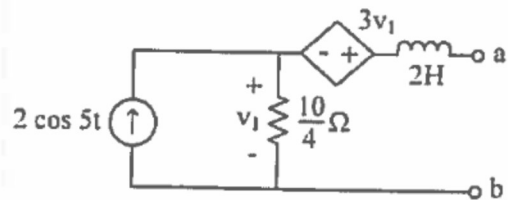(b) For the following circuit, find  $I_N$ ,  $Z_T$  and maximum available average power of the circuit between a and b. (Give  $I_N$  and  $Z_T$  in rectangular form i.e.  $\alpha + j\beta$ )




$$I_N = \underline{\hspace{2cm}}$$

$$Z_T = \underline{\hspace{2cm}}$$

Sp 17

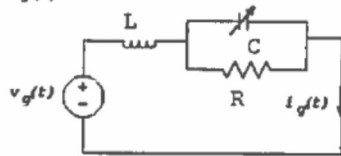2. (25 pts) The circuit shown below is operating in the sinusoidal steady state. The capacitance  $C$  is variable and is adjusted until the current  $i_g(t)$  is in phase with the sinusoidal voltage  $v_g(t)$ .




- (a) What is the value of capacitance  $C$  when  $L = 1\text{H}$ ,  $R = 2\Omega$  and  $v_g(t) = 4\cos(t)\text{V}$ ?

$C =$  \_\_\_\_\_

- (b) For the value of  $C$  identified in part (a), give the expression for  $i_g(t)$ , expressed in A.

## Problem 2

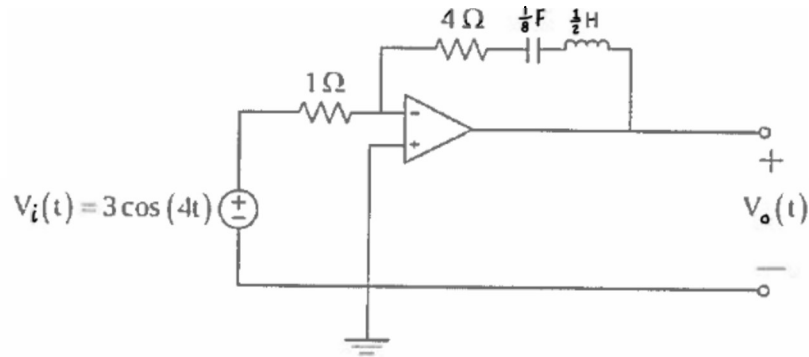

Assume the op-amp in this circuit is an ideal op-amp.


a) (15 points) Use the phasor method to calculate the output voltage  $V_o(t)$ .

b) (5 points) If a  $1000\ \Omega$  resistor is connected across the output terminals, what is the average power dissipated by the resistor?

**Problem 2 (continued)**

- c) (5 points) The op-amp is biased at  $\pm 15\text{V}$ . How would the output voltage change as the input signal frequency is increased or decreased from 4 rad/s? Explain your reasoning.

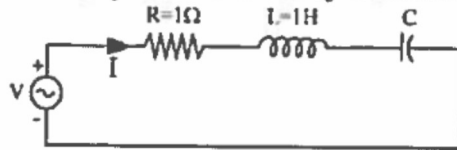2. (25 pts) An RLC series circuit consisting of a  $1\Omega$  resistor  $R$ , an inductance of value  $L = 1\text{ H}$  and a capacitor  $C$  is fed by a cosinusoidal voltage source.



- (a) If the cosinusoidal voltage source has angular frequency  $\omega = 1\text{ rad/s}$  and the current leads (is ahead of) the voltage at the source by  $45^\circ$ , what is the value of the capacitor  $C$ ?

$C =$  \_\_\_\_\_