

Lecture 7, Friday, January 28, 2022

- Superposition principle: Let $\mathbf{V}_{s_1}, \mathbf{V}_{s_2}, \dots, \mathbf{V}_{s_n}, \mathbf{I}_{s_1}, \mathbf{I}_{s_2}, \dots, \mathbf{I}_{s_m}$ be the complete set of *independent* sources in a resistive circuit. Then, any electrical response \mathbf{y} in the circuit (voltage or current) can be expressed as

$$\mathbf{y} = \mathbf{k}_1 \mathbf{V}_{s_1} + \mathbf{k}_2 \mathbf{V}_{s_2} + \dots + \mathbf{k}_n \mathbf{V}_{s_n} + \hat{\mathbf{k}}_1 \mathbf{I}_{s_1} + \hat{\mathbf{k}}_2 \mathbf{I}_{s_2} + \dots + \hat{\mathbf{k}}_m \mathbf{I}_{s_m},$$

where the constants $\mathbf{k}_1, \dots, \mathbf{k}_n, \hat{\mathbf{k}}_1, \dots, \hat{\mathbf{k}}_m$ are unique to each response \mathbf{y} .

- Basically, can look at the effect of each source separately, and then add their contributions.
 - * Remove independent voltage sources by short-circuiting them.
 - * Remove independent current sources by open-circuiting them.
 - * Always keep all the *dependent* sources.