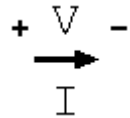


## Lecture 6, Wednesday, January 26, 2022


- Loop-current method

1. Assign loop currents  $\mathbf{I}_1, \mathbf{I}_2, \dots, \mathbf{I}_n$ .


2. Assign current directions and polarities to all elements (use SRS for simplicity).



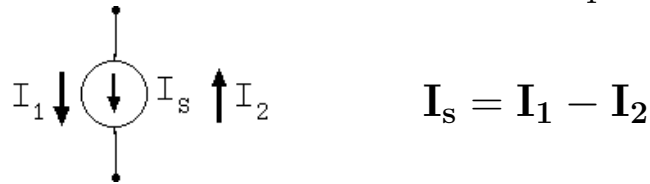3. Use Current sources to obtain equations between their loop currents.



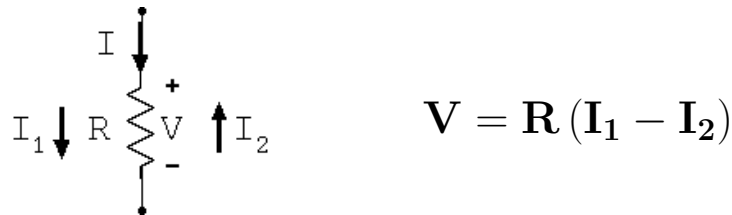4. Use KVL on remaining loops to get a total of  $\mathbf{n}$  equations in terms of the loop currents.




5. Solve equations.

\* Superloop: combine loops involved in a current source into a single *superloop*, bypassing the current source. This avoids introducing an additional variable for the voltage at the current source.

**continued on next page....**
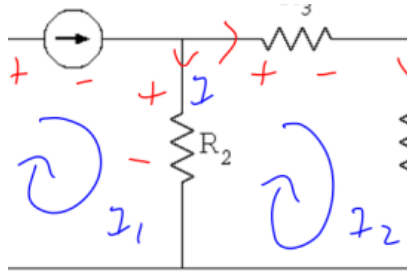
## Lecture 6, continued from previous page...

- There is a difference between *branch* currents, and *loop* currents:
  - branch currents are currents through elements and branches (elements in series),
  - loop currents go through loops across multiple elements and branches.
  - In the figure below, the branch current is the net current  $I$  through the resistor in the direction of the arrow (down)



- \* It is composed of two loop currents:  $I_1$  and  $I_2$
- \* loop current  $I_1$  is going in the same direction as  $I$
- \* loop current  $I_2$  is going in the opposite direction.
- \* So, the branch current  $I = I_1 - I_2$