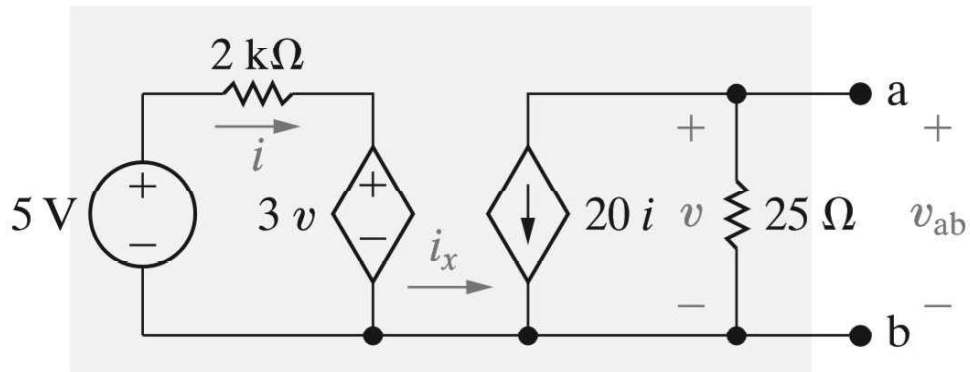



Problem 1

Find the Thévenin equivalent for the circuit containing dependent sources shown below:




Problem 3

The op amp shown is ideal. Calculate v_o if $v_a = 1V$ and $v_b = 0V$. Repeat for $v_a = 1V$ and $v_b = 2V$. If $v_a = 1.5V$, specify the range of v_b that avoids amplifier saturation.

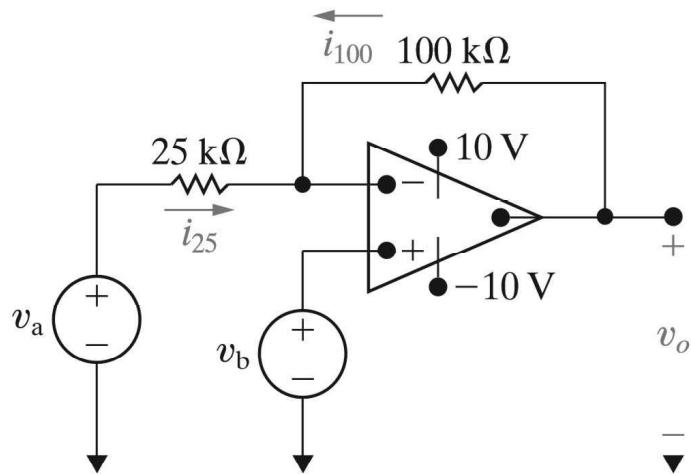

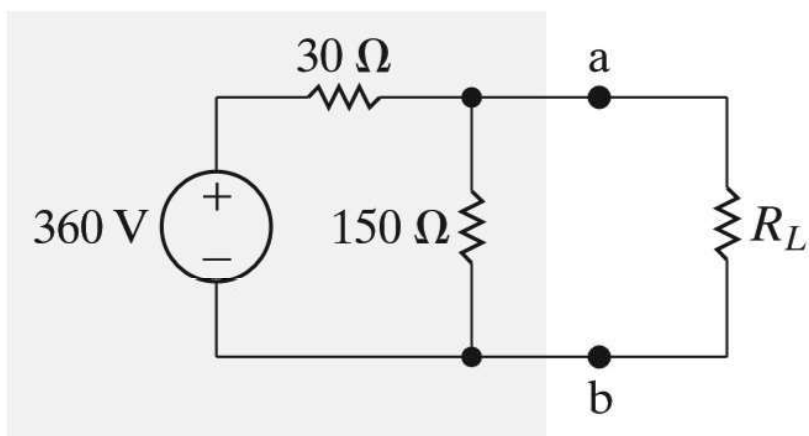
Problem 4

For the circuit shown below, find the value of R_L that results in maximum power being transferred to R_L . Calculate the maximum power that can be delivered to R_L . When R_L is adjusted for maximum power transfer, what percentage of the power delivered by the 360V source reaches R_L ?




1(d)

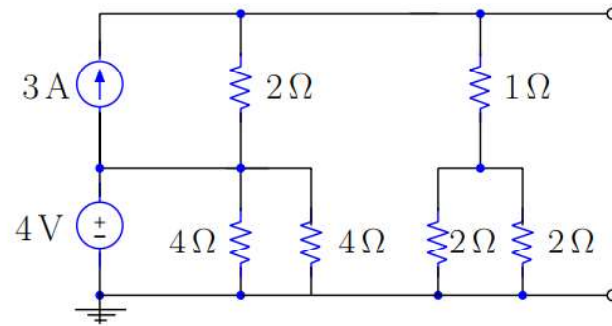(d) (10 pt) Reduce the following circuit to its Thevenin Equivalent, that is find V_T , R_T .




2(b)

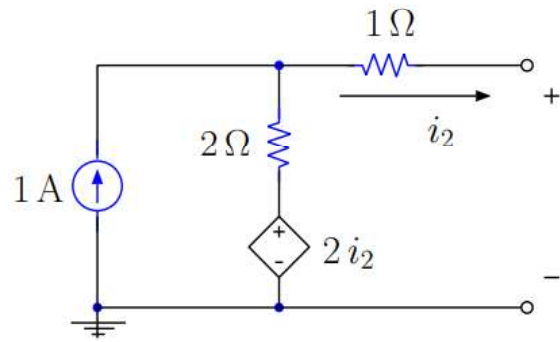(b) (15pt) Find the Thevenin Equivalent Circuit.



3. Problem 3 (25 points)

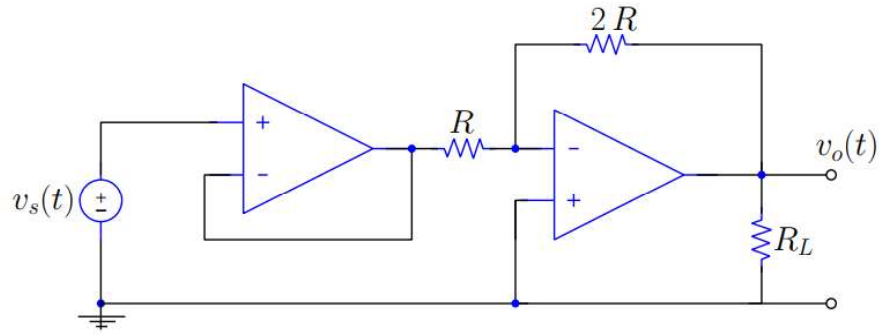- (a) (19 pt) Analyze the following circuit and find v_o/v_s . Use the ideal op-amp approximations.



- (b) Find the power absorbed/supplied in R_L if

- i. (2pt) $R_L = 3\Omega$

$p =$


- ii. (2pt) $R_L = 0\Omega$

$p =$

- iii. (2pt) $R_L = \infty\Omega$

$p =$

Analyze the following bridge circuit

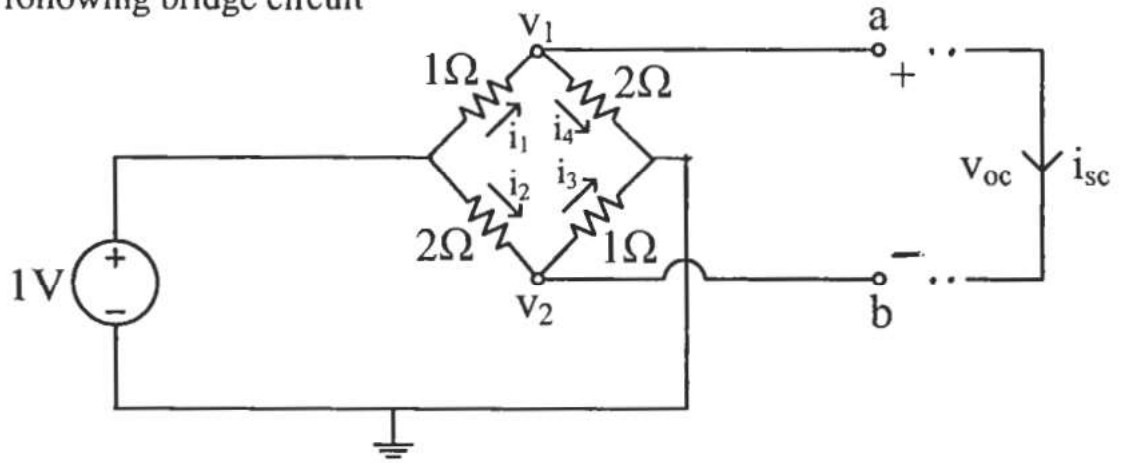

(a) The terminal v_1 and v_2 are open. Calculate v_1 , v_2 , and v_{oc} .


(b) The terminals v_1 and v_2 are shorted together calculate i_1 , i_2 , i_3 , i_4 , and i_{sc} .

(c) Compute the Thevenin resistance of the circuit between a and b.

(d) Draw and label Thevenin and Norton equivalent circuits between a and b.


3

Consider the following op-amp circuit.

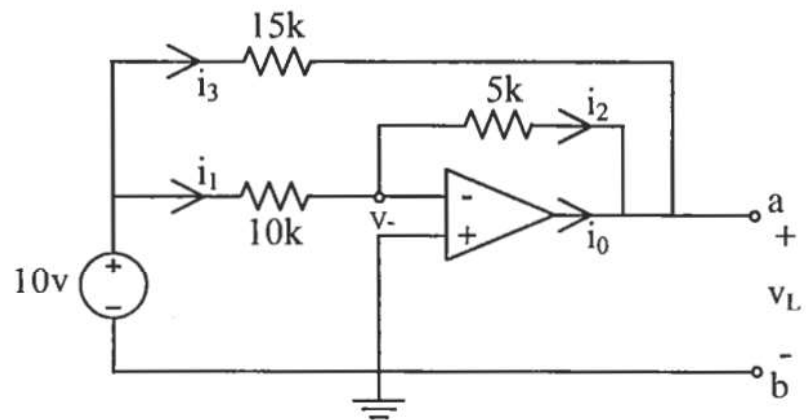

(a) Find v_- , i_1 , i_2 , i_3 , i_0 , and v_L .

(b) If you connect $R_L = 5k\Omega$ between a and b, what is v_L and i_0 ?

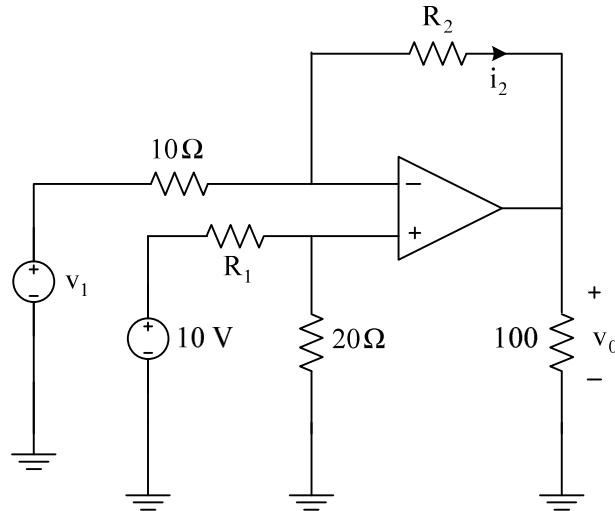Problem 3 (25 points)

All parts of this problem refer to the circuit shown above, but **all parts are independent**. Your answer to each part should **not depend** on your answer to any other part. In all parts, assume that the op amp is an ideal op amp.

- a)** (10 points) **Goal of Part (a):** you want the current i_2 to have the value $i_2 = (0.1v_1 - 0.8)$ amperes. Find a value of R_1 that will achieve this goal.

$R_1 =$ _____

- b)** (10 points) **Goal of Part (b):** you want the output voltage, v_0 , to depend on the input voltage, v_1 , according to some relationship whose slope is $\frac{dv_0}{dv_1} = -b$ for some constant b . Find R_2 in terms of b .

$R_2 =$ _____

Problem 3 (cont.)


- c)** (5 points) **Goal of Part (c):** now suppose that the 100Ω resistor is changed to a 1Ω resistor.

Because the op-amp is ideal, changing the 100Ω resistor has no effect on the current i_2 . Which one of the ideal op amp properties guarantees that i_2 is independent of the value 100Ω ? State the property.

Changing the 100Ω resistor to 1Ω has no effect on the value of i_2 because:

(Problem 3 cont'd)

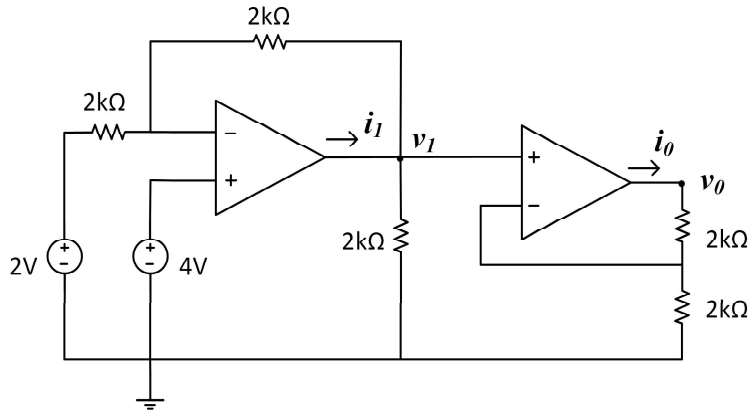- (b) In the following circuit, assuming linear operation and ideal op-amp approximation, determine the node voltages v_0 , v_1 , and the currents i_0 , i_1 .



$$v_0 = \underline{\hspace{2cm}}$$


$$v_1 = \underline{\hspace{2cm}}$$

$$i_0 = \underline{\hspace{2cm}}$$

$$i_1 = \underline{\hspace{2cm}}$$

(Problem 3 cont'd)

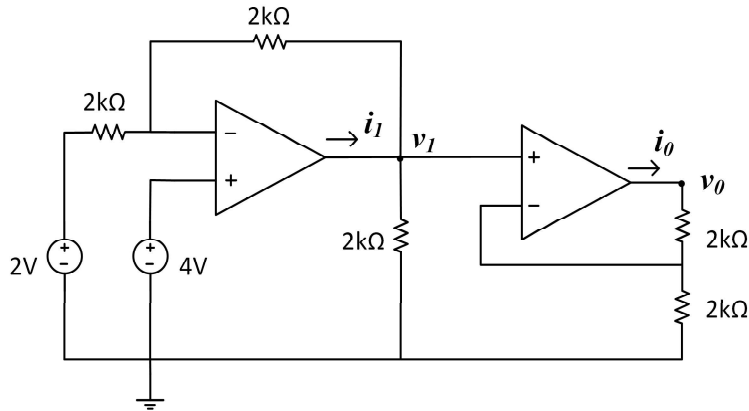- (b) In the following circuit, assuming linear operation and ideal op-amp approximation, determine the node voltages v_0 , v_1 , and the currents i_0 , i_1 .



$$v_0 = \underline{\hspace{2cm}}$$

$$v_1 = \underline{\hspace{2cm}}$$

$$i_0 = \underline{\hspace{2cm}}$$

$$i_1 = \underline{\hspace{2cm}}$$