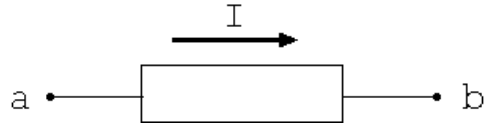


Lecture 1, Monday, January 18, 2022


- *Current*: amount of net electrical charge per unit time passing in the direction of arrow.



$$I = \frac{dq}{dt} \begin{cases} > 0 \\ = 0 \\ < 0 \end{cases} \begin{array}{l} \\ \\ \text{going in opposite direction} \end{array}$$

– Units: Amperes: $A = \frac{C}{s}$

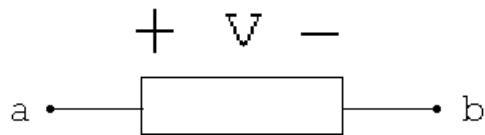- *Voltage*: energy gain per Coulomb moved from \ominus terminal to \oplus terminal, or energy loss per Coulomb moved from \oplus terminal to \ominus terminal.



$$V = \frac{dW}{dq} \begin{cases} > 0 \\ = 0 \\ < 0 \end{cases} \begin{array}{l} \\ \\ \text{energy is lost, not gained} \end{array}$$

– Units: Volts: $V = \frac{J}{C}$


- Assignment of polarities and current directions
 - Can choose current directions any way we want
 - Can choose voltage polarities any way we want
 - Standard reference system (SRS) uses current going into \oplus terminal

All our equations will assume the SRS assignment

continued on next page....


Lecture 1, continued from previous page...

- *Series* element configuration

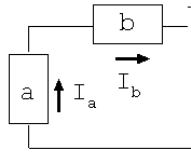

- elements share one node, nothing else connected between them
- elements have the same current

- *Parallel* element configuration

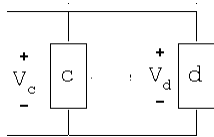

- elements share same two nodes
- elements have same voltage