
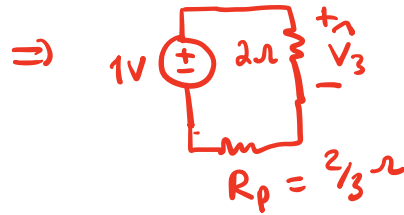


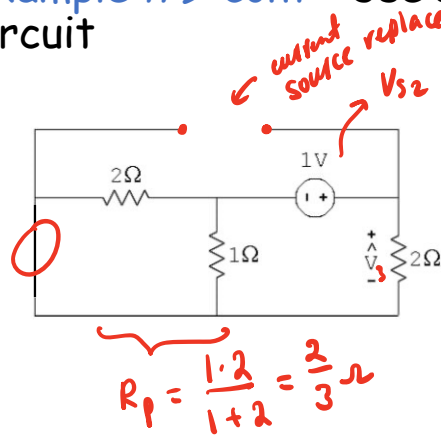- Example #9-cont: Use superposition to determine \hat{V} in this circuit



Voltage division :


$$\hat{V}_3 = 1 \frac{2}{2 + 2/3} = \frac{3}{4} V$$

↑
contribution
from 1V source

$$\begin{aligned} \Rightarrow \hat{V} &= \hat{V}_1 + \hat{V}_2 + \hat{V}_3 = \\ &= \frac{1}{2} - 1 + \frac{3}{4} = \frac{1}{4} V \end{aligned}$$

- Thevenin and Norton equivalent circuits

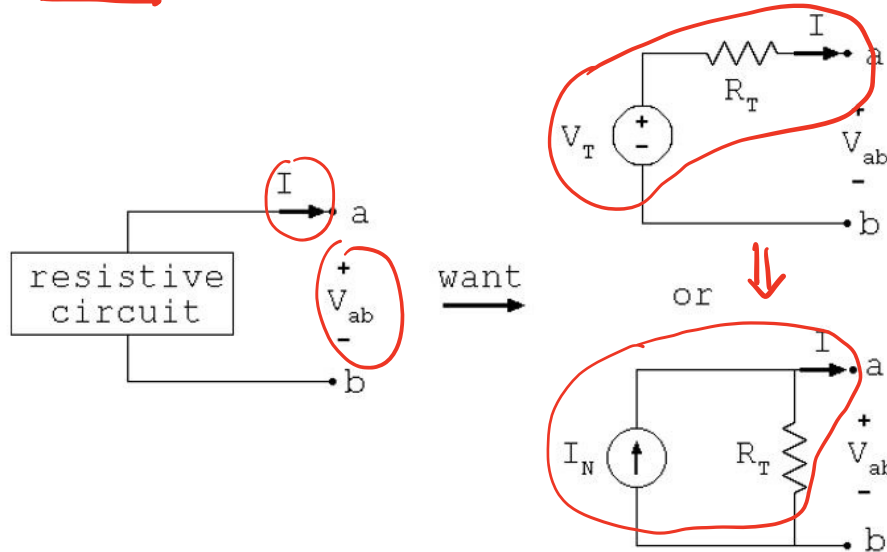Can we model any resistive circuit using a simple circuit?




$$I_N = \frac{V_T}{R_T} \Rightarrow$$

$$R_T = \frac{V_T}{I_N}$$

- Can we do this?
- How do we do this?

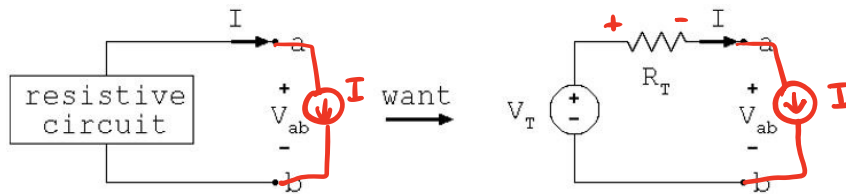- Thevenin and Norton equivalent circuits



By superposition:

$$V_{ab} = K_1 V_{S1} + K_2 V_{S2} + \dots + \hat{K}_1 I_{S1} + \underbrace{+ \hat{K}_2 I_{S2} + \dots + \textcircled{A} \cdot \textcircled{I}}_{\text{Norton current } I_N}$$

$$\text{KVL: } -V_T + R_T \cdot I + V_{ab} = 0$$


$$V_{ab} = \textcircled{V_T} - \textcircled{R_T} \cdot \textcircled{I}$$

$$\Downarrow R_T = -A$$

V_T : Thevenin's voltage (if no independent sources, $V_T = 0$ and $I_N = 0$)
 R_T : Thevenin's resistance
 I_N : Norton's current

- Thevenin and Norton equivalent circuits


- How to get V_T ?

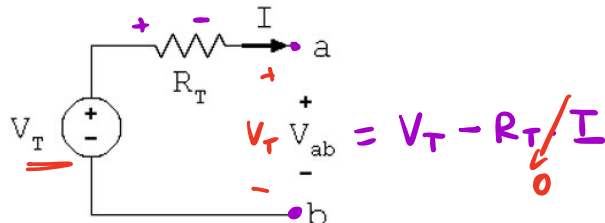

V_T - open circuit voltage

KVL: $-V_T + R_T \cdot I + V_{ab} = 0$


- How to get I_N ?

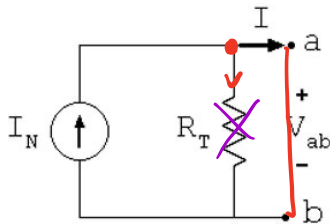

KCL: $I_N = \frac{V_{ab}}{R_T} + I$

I_N : short-circuit current

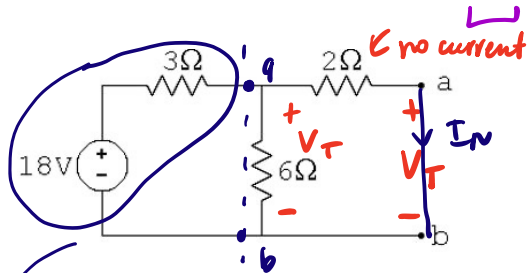
- Example #10: Obtain V_T and I_N for the following circuit



Voltage division:

$$V_T = 18 \left(\frac{6}{6+3} \right) = 12V$$

source transformation:

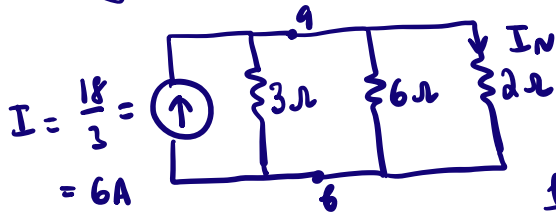

$$I = \frac{18}{3} = 6A$$

$$\frac{1}{R_p} = \frac{1}{3} + \frac{1}{6} + \frac{1}{2} = 1\Omega$$

Current division:

$$I_N = I \left(\frac{R_p}{2} \right) = 3A$$

Find V_T -?



a) $-6V$

b) $6V$

c) $-12V$

d) $12V$



e) I want my quiz to be 0 :-)

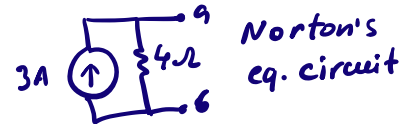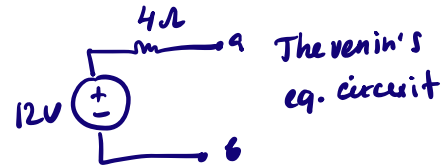


$$R_T = \frac{V_T}{I_N} = \frac{12}{3} = 4\Omega$$

- **Example #10-cont:** Obtain V_T and I_N for the following circuit

- How to get R_T ?

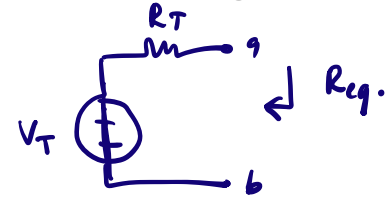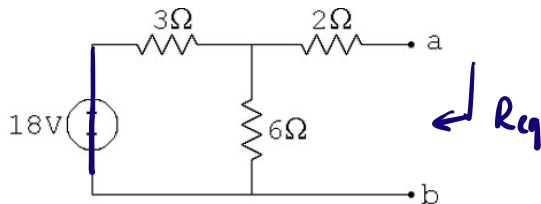


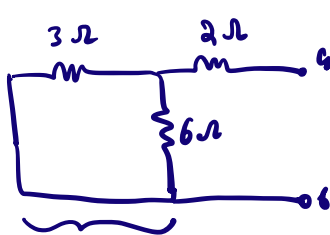- **Source suppression:** remove all independent sources:



in || \Rightarrow


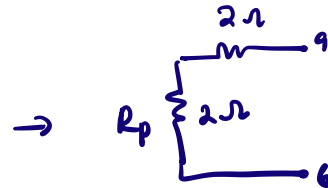
$$R_p = \frac{3 \cdot 6}{3 + 6} = \frac{18}{9} = 2\Omega$$



$$\Rightarrow R_{eq} = 2 + 2 = 4\Omega = R_T$$

- Test signal method

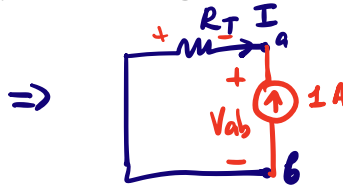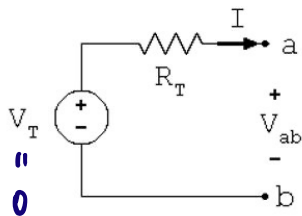- What if can't simplify to a single resistor?



KVL:

$$R_T \cdot I + V_{ab} = 0$$

$$R_T = -\frac{V_{ab}}{I} \quad \ominus$$

Source suppression



check if you can reduce to a single resistor

yes
↓
done 😊

no
↓
inject 1A into a terminal a
↓
obtain V_{ab}
↳ $R_T = V_{ab} \text{ in } \Omega \text{ (not V)} \rightarrow \text{done 😊}$

$$I = -1A$$

$$\ominus \frac{-V_{ab}}{-1} = V_{ab}$$



we can get R_T by obtaining V_{ab} , and it will be numerically equal to R_T .