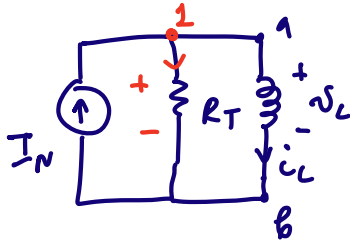


• What about inductors?



$$\text{KCL @ (1): } I_N = \frac{v_L}{R_T} + i_L =$$

$$= \frac{L}{R_T} \frac{di_L}{dt} + i_L \quad \left| \times \frac{R_T}{L} \right.$$

$$v_L = L \frac{di_L}{dt}$$

↓
in DC steady-state
inductor acts like
Short

$$\frac{di_L}{dt} + \underbrace{\left(\frac{R_T}{L} \right)}_{\text{"a"}} i_L = \frac{R_T}{L} I_N \quad \text{for } t > 0 \quad \Rightarrow \quad \tau = \frac{L}{R_T}$$

first order ODE with const. coeff.
and const. input

↓
solution should be in this form:

$$i_L(t) = B + A e^{-at} = B + A e^{-t/\tau} \quad a = \frac{1}{\tau}$$

$$i_L(\infty) = B$$



$$i_L(0^+) = i_L(0^-) = B + A$$

• Example #16:

- Consider the circuit below.
- Assume the switch has been in position A for a long time and it switches to position B at time $t = 0$

- Determine $i_L(t)$ for $t > 0$
- Determine $i_{ZS}(t)$ and $i_{ZI}(t)$

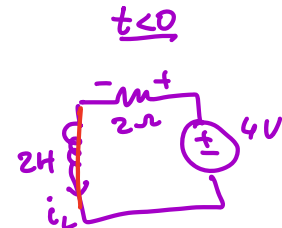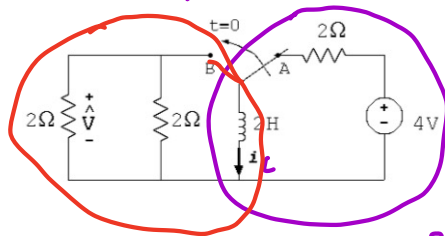↓ in DC steady-state \Rightarrow
inductor is a short



$$i_L(0^-) = \frac{4}{2} = 2 \text{ A}$$



$$i_L(t) = B + A e^{-t/\tau}$$


$$i_L(\infty) = B = 0 \text{ (no source)}$$

$$i_L(0^+) = i_L(0^-) = 2 \text{ A}$$

$$i_L(t) = i_L(0^-) e^{-t/2} \text{ A}$$

$$i_{ZS}(t) = 0 \text{ (force } i_L(0^-) \text{ to be 0)}$$
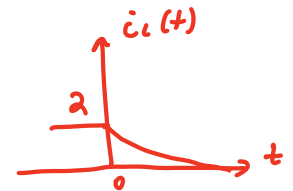
$$i_{ZI}(t) = i_L(0^-) e^{-t/2} = 2 e^{-t/2} \text{ A}$$




$$\text{Find } \tau: R_T = \frac{2 \cdot 2}{2 + 2} = 1 \Omega$$

$$\tau = \frac{L}{R_T} = \frac{2}{1} = 2 \text{ s}$$

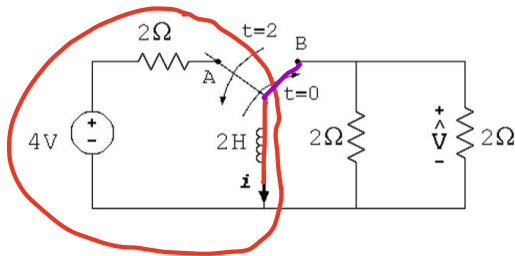• Example #17:


- Consider the circuit below.
- Assume the switch has been in position A for a long time and it switches to position B at time $t = 0$
- Determine and sketch $i_L(t)$



$$t < 0$$

$$i_L(0^-) = \frac{4}{2} = 2A$$

$$0 < t < 2$$

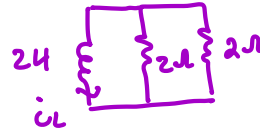

Find τ :

$$\tau = \frac{L}{R_T} = \frac{2}{1} = 2s$$

$$R_T = \frac{2 \cdot 2}{2 + 2} = 1\Omega$$


$$i_L(t) = B + Ae^{-t/\tau}$$

$$i_L(0) = B = 0$$

$$i_L(0^+) = i_L(0^-) = A = 2$$

$$i_L(t) = 2e^{-t/2} A$$

• Example #17-cont:

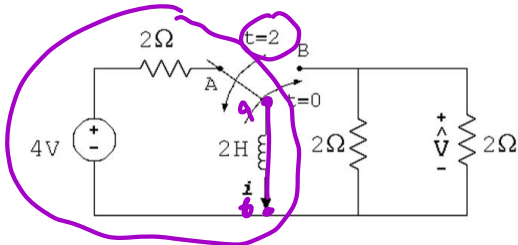

Find \hat{v} :

$$\hat{\tau} = \frac{L}{R_T} = \frac{2}{2} = 1s$$

$$R_T = 2\Omega$$

$t > 2$

$$i_L(t) = \hat{B} + \hat{A} e^{-t/\hat{\tau}}$$

$$i_L(\infty) = \hat{B} = \frac{4}{2} = 2A$$

$$? i_L(2^+) = i_L(2^-) = \hat{B} + \hat{A} e^{-2/\hat{\tau}} =$$

$$= 2 + \hat{A} e^{-2/\hat{\tau}} = 2 + \hat{A} e^{-2} = 2e^{-1}$$

↓

$$\hat{A} = (2e^{-1} - 2)e^2$$

$$i_L(t) = 2 + (2e^{-1} - 2)e^2 \cdot e^{-t} =$$


$$= 2 + 2(\tilde{e}^{-1} - 1) \tilde{e}^{-(t-2)} A$$

$$\underline{0 < t < 2}$$


$$i_L(t) = 2e^{-t/2} \Rightarrow$$

$$i_L(2^-) = 2e^{-2/2} = 2e^{-1}$$

• Example #17-cont:

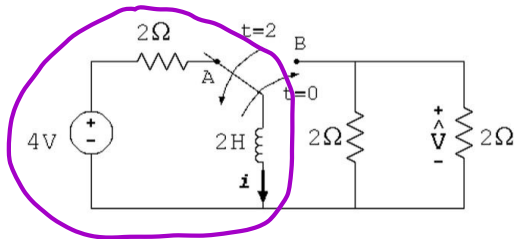
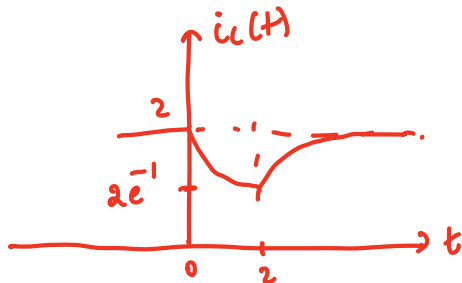
$$i_L(t) = \begin{cases} 2A & \underline{t < 0} \\ 2e^{-t/2} A & \underline{0 < t < 2} \\ 2 + 2(e^{-1} - 1)e^{-(t-2)} A & \underline{t > 2} \end{cases}$$



Alternative:

Reference
to $t=2$

$$\underline{t > 2} \quad i_L(t) = \hat{B} + \hat{A} e^{-\frac{(t-2)}{\tau}} \quad \hat{\tau} = 1$$

$$i_L(\infty) = \hat{B} = \frac{4}{2} = 2 \quad \text{same}$$


$$i_L(2+) = \hat{B} + \hat{A} = 2 + \hat{A} = 2e^{-1}$$

$$\hat{A} = 2e^{-1} - 2 = 2(e^{-1} - 1) \quad \text{different}$$

$$\underline{i_L(t) = 2 + 2(e^{-1} - 1)e^{-(t-2)} A}$$

- Example #17-cont:

- Determine and sketch $i_L(t)$

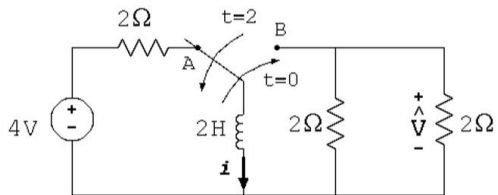

- Solution to first-order ODE with time-varying sources

- Recall that if the input is constant, i.e. $f(t) = K$,

$$K = \frac{dy}{dt} + ay,$$

↑
constant

then

$$y(t) = y_p(t) + y_h(t) = B + Ae^{-at}$$

y_p y_h

- If the input is not constant, then

$$f(t) = \frac{dy}{dt} + ay,$$

is still the first-order ODE with constant coefficients

- The homogeneous solution is the same no matter what the input is:

$$y_h(t) = Ae^{-at}$$

- However, the particular solution changes depending on the input

y_h solves
 $0 = \frac{dy_h}{dt} + ay_h$
 ↪ input has
 no effect on
 hom. solution

- Solution to first-order ODE with time-varying sources-cont.

$$y_p(t) = \begin{cases} B & \text{if } f(t) = K \text{ -constant} \\ Be^{-pt} & \text{if } f(t) = Ke^{-pt}, a \neq p \\ Bte^{-at} & \text{if } f(t) = Ke^{-at}, p=a \\ H \cos(\omega t + \psi) & \text{if } f(t) = K \cos(\omega t + \theta) \end{cases}$$

$y_h = Ae^{-at}$

same!