

ECE 210 (AL2) - ECE 211 (E)

Chapter 5


Frequency Response $H(\omega)$ of LTI Systems

Olga Mironenko
University of Illinois
Spring 2022

Chapter objectives

- Understand the meaning and application of an LTI system's frequency response
- Be able to obtain the frequency response of an LTI system
- Know the properties of the frequency response of an LTI system
- Use the frequency response of an LTI system obtain the system's response to co-sinusoidal inputs
- Use the frequency response of an LTI system obtain the system's response to multifrequency co-sinusoidal inputs

• Example #1

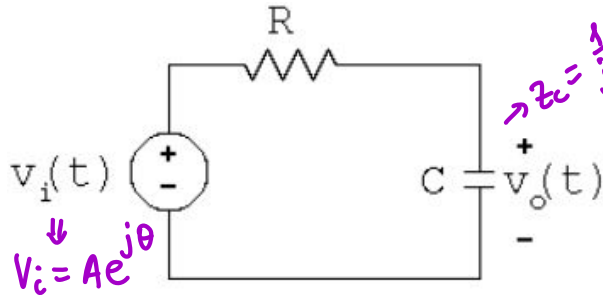

- Let $v_i(t) = A \cos(2t + \theta)$
- Determine $v_o(t)$

$$\rightarrow Z_C = \frac{1}{j\omega C} = \frac{1}{j2C}$$


$$V_o = V_i \frac{\frac{1}{j2C}}{R + \frac{1}{j2C}} = V_i \frac{1}{j2RC + 1} =$$

$$= \frac{|V_i| e^{j\angle V_i}}{\sqrt{1^2 + (2RC)^2} e^{j \tan^{-1}(\frac{2RC}{1})}}$$

$$V_o = \frac{|V_i|}{\sqrt{1 + 4R^2C^2}} e^{j(\angle V_i - \tan^{-1}(2RC))}$$

$$v_o(t) = \frac{A}{\sqrt{1 + 4R^2C^2}} \cos(2t + \theta - \tan^{-1}(2RC))$$

• Example #1

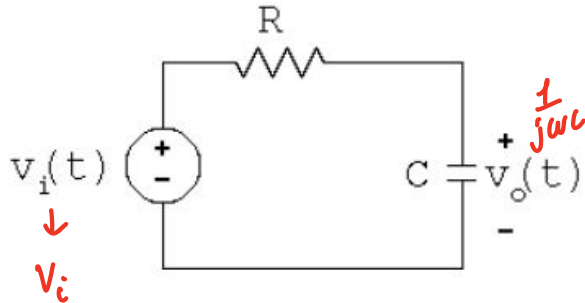

$$V_o = \frac{V_i \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = V_i \frac{1}{j\omega RC + 1} = V_o$$

$H(\omega)$ frequency response

- What if we change the frequency of the input?

$$V_o = \frac{|V_i|}{\sqrt{1 + \omega^2 R^2 C^2}} e^{j(\phi V_i - \tan^{-1}(\omega RC))}$$

$$v_{o,ss}(t) = \frac{|V_i|}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi V_i - \tan^{-1}(\omega RC)) V$$

phase response $\phi H(\omega)$

$$H(\omega) = |H(\omega)| e^{j\phi H(\omega)}$$

↓ amplitude response $|H(\omega)|$

- Frequency response of LTI systems

$$V_o = V_i H(\omega)$$

\swarrow output phasor
 \nwarrow input phasor

- Frequency response $H(\omega)$

$$V_i = |V_i| e^{j\angle V_i}$$

$$V_o = |V_i| |H(\omega)| e^{j(\angle V_i + \angle H(\omega))}$$

real signal \rightarrow LTI \rightarrow real signal

$$|V_i| |H(\omega)| \cos(\dots)$$

$$v_i(t) = |V_i| \cos(\omega t + \angle V_i)$$

$$v_o(t) = |V_i| |H(\omega)| \cos(\omega t + \angle V_i + \angle H(\omega))$$

• Frequency response of LTI systems-cont

$$v_o(t) = |V_i| |H(\omega)| \cos(\omega t + \angle V_i + \angle H(\omega))$$

• Amplitude response $|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

• Phase response $\angle H(\omega)$

$$\frac{e^{j0}}{e^{j \tan^{-1}(\omega RC)}}$$

$$\angle H(\omega) = -\tan^{-1}(\omega RC)$$

