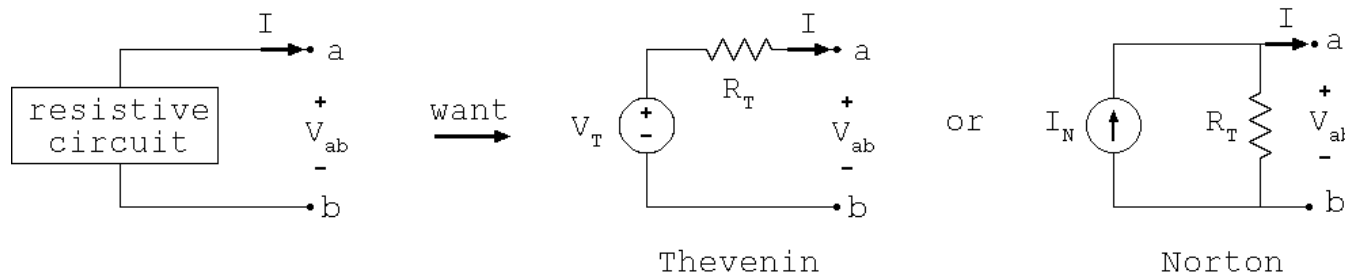


## Lecture 8, Monday, January 31, 2022

- Thevenin and Norton equivalent circuits



- Thevenin's voltage,  $V_T$ , is open-circuit voltage
- Norton's current,  $I_N$ , is short-circuit current
- $V_T$  and  $I_N$  are a linear combination of the independent sources in circuit
  - \* If there are no independent sources, then  $V_T = I_N = 0$
- Thevenin's resistance,  $R_T$ , is equivalent resistance
  - \* Remove all independent sources
  - \* If can simplify into a single resistor, that is  $R_T$
  - \* If cannot, then use *test signal* method:
    - inject 1A into terminal  $a$
    - measure the voltage from terminal  $b$  to  $a$
    - divide that voltage by 1A to get  $R_T$

**continued on next page....**

**Lecture 8, continued from previous page...**

- \* Even though the test signal method adds some steps that  $I_N$  would not need, the resulting circuit after source suppression might be significantly simpler to solve.
- Also,

$$V_T = R_T I_N$$