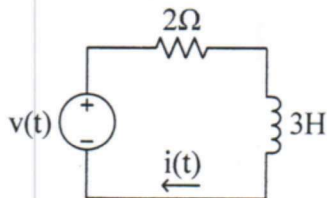


### Problem 3

- (a) The circuit below has frequency response  $H(\omega) = \frac{I}{V}$ .




$$V = IZ \Rightarrow \frac{I}{V} = \frac{1}{Z}$$

$$Z = 2 + j3\omega$$

i) Determine  $H(\omega)$ :  $\frac{1}{2 + j3\omega}$


ii) Determine the maximum value for  $|H(\omega)|$ :  $\frac{1}{2}$  at  $\omega = 0$

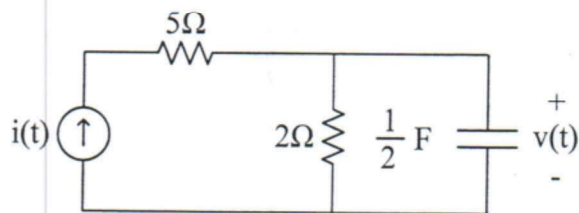- (b) The circuit below has frequency response  $H(\omega) = \frac{V}{I}$ .



$$V = IZ \Rightarrow \frac{V}{I} = Z$$

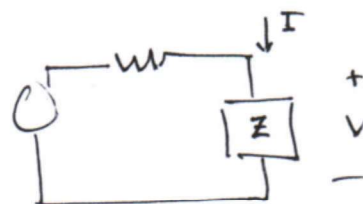i) Determine  $H(\omega)$ :  $\frac{2}{1 + j\omega}$



ii) Determine  $|H(\omega)|$  as  $\omega \rightarrow \infty$ : 0

$$Z = \frac{2 \cdot \frac{1}{\frac{1}{2}j\omega}}{2 + \frac{1}{j\frac{1}{2}\omega}}$$

iii) Determine  $\angle H(\omega)$  as  $\omega \rightarrow \infty$ :  $-\frac{\pi}{2}$

$$\lim_{\omega \rightarrow \infty} \angle \frac{2}{1 + j\omega} = \lim_{\omega \rightarrow \infty} \angle 2 - \angle 1 + j\omega = 0 - \frac{\pi}{2}$$

$$= \frac{2}{1 + j\omega}$$

(c) An LTI system with input  $f(t)$  and output  $y(t)$  is described by the ODE

$$\frac{d^2 y}{dt^2} + 2 \frac{dy}{dt} + 3y(t) = f(t)$$

$$(j\omega)^2 Y + j2\omega Y + 3Y = F$$

The frequency response for the system  $H(\omega) = \frac{Y}{F}$ .

$$\frac{Y}{F} = \frac{1}{(j\omega)^2 + j2\omega + 3}$$

i) Determine  $H(\omega)$ :  $\frac{1}{-\omega^2 + 3 + j2\omega}$

ii) Determine the value of  $\omega$  ( $\omega > 0$ ) such that  $\angle H(\omega) = -\frac{\pi}{4}$ :  $1$

$$\angle H = -\angle (-\omega^2 + 3 + j2\omega)$$

~~For  $\angle H = -\frac{\pi}{4}$ ,  $-\omega^2 + 3 = j2\omega$~~   
 ~~$\text{Re}\{\text{denominator}\} = \text{Im}\{\text{denominator}\}$~~

$$\angle H = -\frac{\pi}{4} \text{ when } \angle \text{denominator} = \frac{\pi}{4}$$


$$\text{when } \text{Re}\{\text{denominator}\} = \text{Im}\{\text{denominator}\}$$

$$3 - \omega^2 = 2\omega \Rightarrow \omega = 1$$

1. Problem 1 (25 points)

These problems are intended to be quick and easy:

(a) For the following circuit.

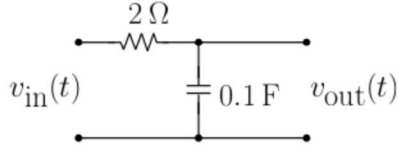

(3 pt)

i. Find the frequency response  $H(\omega)$ .

Sol:

Phasor voltage divider:  $H(\omega) = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega \cdot 0.2}$

(1 pt)

ii. Is  $H(\omega)$  the frequency response of a high pass, low pass or a band pass filter?

Sol:

Lowpass ( $H(0) = 1$ ,  $H(\omega \rightarrow \infty) = 0$ , monotonically decreasing)

(3 pt)

iii. If  $v_{in}(t) = 2 + \cos(5t + \frac{\pi}{4})$ , then  $v_{out}(t) = ?$

Sol:


$v_{in}(t)$  composed of two co-sinusoidal components with frequencies 0 and 5:

$\omega_o$	$V_{in}$ phasor	$H(\omega_o)$	$V_{out}$ phasor = $V_{in}H(\omega_o)$	$v_{out}(t, \omega_o)$
0	$2e^{j0}$	1	2	2
5	$1e^{j\frac{\pi}{4}}$	$\frac{1}{1+j} = \frac{e^{-j\frac{\pi}{4}}}{\sqrt{2}}$	$\frac{1}{\sqrt{2}}e^{j(\frac{\pi}{4}-\frac{\pi}{4})} = \frac{1}{\sqrt{2}}$	$\frac{1}{\sqrt{2}}\cos(5t + 0)$

$\therefore v_{out}(t) = 2 + \frac{1}{\sqrt{2}}\cos(5t)$

(2 pt)

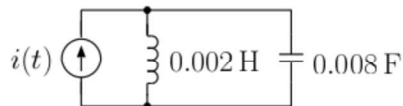(b) What is the resonance frequency of the following circuit.



Sol:

$\omega_{\text{resonance}} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{16 \cdot 10^{-6}}} = \frac{1}{4 \cdot 10^{-3}} = 250 \frac{\text{rad}}{\text{sec}}.$

Also,

total impedance:  $Z = Z_L \parallel Z_C = \frac{1}{\frac{1}{j\omega L} + j\omega C} = \frac{j\omega L}{1 - \omega^2 LC}.$


Then  $Z \rightarrow \infty$ , when  $\omega \rightarrow \frac{1}{\sqrt{LC}} = 250 \frac{\text{rad}}{\text{sec}}.$

### Problem 3 (25 points)

All parts of this problem are independent.

- a) (5 points) In the circuit below,  $H(\omega) = V(\omega)/I_s(\omega)$ . Find  $H(\omega)$ . Your answer may include the variables,  $R$ ,  $C$ ,  $L$  and  $\omega$ .

$$Z_{\text{equivalent}} = \frac{1}{j\omega C} + \frac{j\omega L R}{j\omega L + R}$$
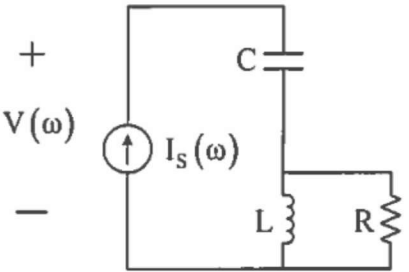
$$H(\omega) = \frac{V(\omega)}{I_s(\omega)} = Z_{\text{equivalent}} = \frac{1}{j\omega C} + \frac{j\omega L R}{j\omega L + R}$$


$$H(\omega) = \frac{1}{j\omega C} + \frac{j\omega L R}{j\omega L + R}$$

- b) A particular circuit is characterized by  $H(\omega) = \frac{15j\omega}{25j\omega + (1 - \omega^2 64)}$

- i) (4 points) What is the frequency  $\omega_p$ , at which  $|H(\omega)|$  is maximum?

$$|H(\omega)| = \frac{15\omega}{\sqrt{(25\omega)^2 + (1 - \omega^2 64)^2}}$$

$$\omega_p = \frac{1}{8}$$

$|H(\omega)|$  will maximize when  $(1 - \omega^2 64)^2$  is at its minimum which is 0.  
 $1 - \omega^2 64 = 0 \quad \omega^2 64 = 1$

$$\Rightarrow \omega_p = \frac{1}{8}$$

- ii) (4 points) What is  $|H(\omega_p)|$ ?

$$|H(\omega_p)| = \frac{15\omega}{25\omega} = \frac{3}{5}$$

$$|H(\omega_p)| = \frac{3}{5}$$

**Problem 3 (continued)**

c) A circuit has input  $f(t)$ , output  $y(t)$ , and frequency response  $H(\omega)$  given by

$$H(\omega) = \frac{a + j\omega b}{c + j\omega d}$$

You may answer each of the following sub-parts in terms of the variables  $a$ ,  $b$ ,  $c$ , and  $d$  if you wish. You may assume that  $a$ ,  $b$ ,  $c$ , and  $d$  are all positive real constants.

i) (4 points) If  $f(t) = 6 \cos(35t)$ , then  $y(t) = A \cos(35t + \theta)$  for what value of  $A$ ?

$$A = 6 \times |H(\omega)| = \frac{6\sqrt{a^2 + (35b)^2}}{\sqrt{c^2 + (35d)^2}}$$

ii) (4 points) If  $f(t) = 6 \cos(35t)$ , then  $y(t) = A \cos(35t + \theta)$  for what value of  $\theta$ ?

$$\theta = \tan^{-1}\left(\frac{35b}{a}\right) - \tan^{-1}\left(\frac{35d}{c}\right)$$

$$\theta = \angle H(\omega) + \angle f(t) = \angle H(\omega) + 0$$

$$= \tan^{-1}\left(\frac{35b}{a}\right) - \tan^{-1}\left(\frac{35d}{c}\right)$$

iii) (4 points) If  $f(t) = 10$ , what is  $y(t)$ ?

$$\omega = 0$$

$$H(0) = \frac{a + j0b}{c + j0d} = \frac{a}{c}$$

$$y(t) = 10 \frac{a}{c}$$

$$|y(t)| = |H(0)| \cdot |f(t)| = 10 \frac{a}{c}$$


$$\angle y(t) = \angle f(t) + \angle H(0) = \angle f(t) = 0$$

$$y(t) = 10 \frac{a}{c}$$

### Problem 3

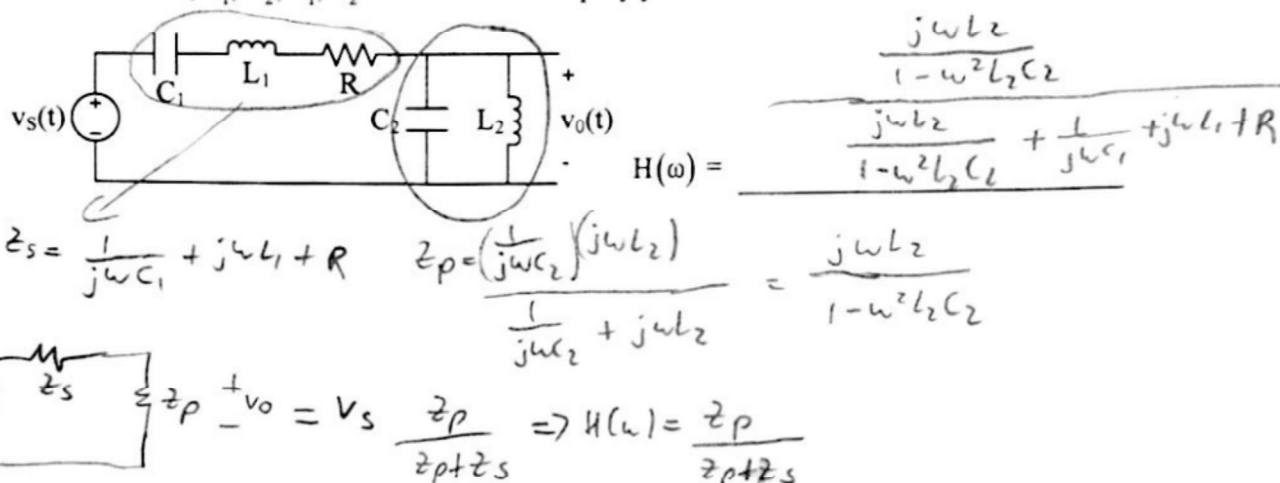(a) Determine the frequency response  $H(\omega) = \frac{V_o(\omega)}{V_s(\omega)}$  of the following circuit. Give the answer

in terms of  $\omega$ ,  $C_1$ ,  $C_2$ ,  $L_1$ ,  $L_2$  and  $R$ . Do not simplify your answer.



(b) A linear system with the input  $f(t)$  and output  $y(t)$  is described by ODE

$$3 \frac{d^2 y}{dt^2} + 2 \frac{dy}{dt} + y(t) = 2 \frac{df}{dt} + f(t)$$

Determine the frequency response  $H(\omega) = \frac{Y(\omega)}{F(\omega)}$  of the system.

$$\frac{d}{dt} \rightarrow j\omega \Rightarrow 3(j\omega)^2 Y + 2(j\omega)Y + Y = 2(j\omega)F + F$$

$$Y[-3\omega^2 + 2j\omega + 1] = F(2j\omega + 1)$$

$$\frac{Y}{F} = \frac{1 + j2\omega}{1 - 3\omega^2 + j2\omega} \quad H(\omega) = \frac{1 + j2\omega}{1 - 3\omega^2 + j2\omega}$$

(c) Given an input  $f(t) = 2 \cos \omega_1 t + \sin(\omega_2 t + \theta_2)$  and  $H(\omega) = \frac{1 + j\omega}{2 + j\omega}$  determine the steady-state response  $y_{ss}(t)$  of the system  $H(\omega)$ .

$$|H(\omega)| = \sqrt{\frac{1^2 + \omega^2}{2^2 + \omega^2}} = \sqrt{\frac{1 + \omega^2}{4 + \omega^2}}$$

$$\angle H(\omega) = \tan^{-1}\left(\frac{\omega}{1}\right) - \tan^{-1}\left(\frac{\omega}{2}\right)$$

$$y_{ss}(t) = 2 \sqrt{\frac{1 + \omega_1^2}{4 + \omega_1^2}} \cos(\omega_1 t + \tan^{-1}(\omega_1) - \tan^{-1}(\frac{\omega_1}{2}))$$

$$+ \sqrt{\frac{1 + \omega_2^2}{4 + \omega_2^2}} \sin(\omega_2 t + \theta_2 + \tan^{-1}(\omega_2) - \tan^{-1}(\frac{\omega_2}{2}))$$