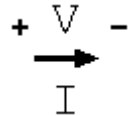



Lecture 5, Tuesday, January 25, 2022

- Node-voltage method


1. Identify all nodes and label their node voltages $\mathbf{V}_1, \mathbf{V}_2, \dots, \mathbf{V}_n$ plus a reference.
2. Assign current directions and polarities to all elements (use SRS for simplicity).



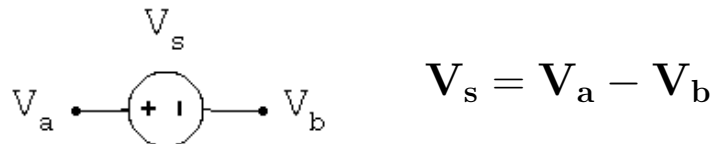3. Use voltage sources to obtain equations between their node voltages.



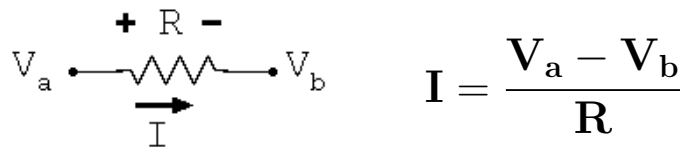4. Use KCL on remaining nodes to get a total of \mathbf{n} equations in terms of the node voltages.



5. Solve equations.

- Supernode: combine the two nodes of a voltage source into a single *supernode*. This avoids introducing an additional variable for the current through the voltage source. Only works on voltage sources.


continued on next page....

Lecture 5, continued from previous page...


- Loop-current method

1. Assign loop currents $\mathbf{I}_1, \mathbf{I}_2, \dots, \mathbf{I}_n$.

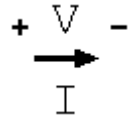
2. Assign current directions and polarities to all elements (use SRS for simplicity).



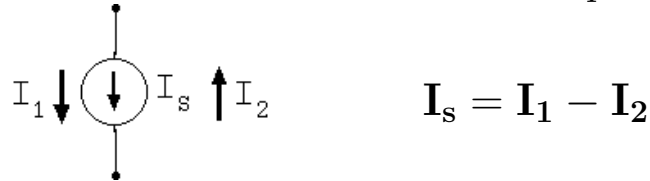3. Use Current sources to obtain equations between their loop currents.



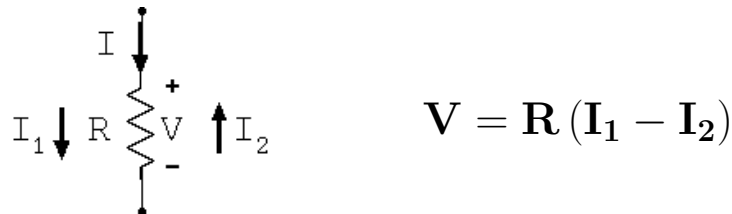4. Use KVL on remaining loops to get a total of \mathbf{n} equations in terms of the loop currents.



5. Solve equations.