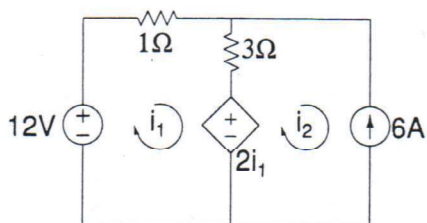


2. (25 pts) The two parts in this problem are unrelated.

(a) Find the loop currents i_1 and i_2 in the following circuit.



$$i_1 = \underline{-1A}$$

$$i_2 = \underline{-6A}$$

1st loop: $12 - 1 \cdot i_1 - 3(i_1 - i_2) - 2i_1 = 0$
 $12 - 6i_1 + 3i_2 = 0$


$$6i_1 - 3i_2 = 12$$

$$6i_1 - 3(-6) = 12$$

$$6i_1 = 12 - 18$$

$$i_1 = -\frac{6}{6} = -1A$$

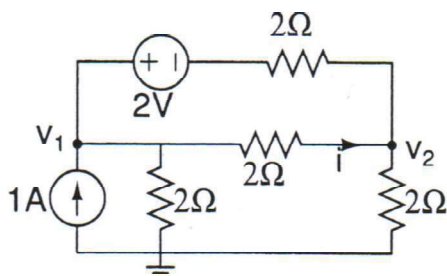(b) Find the node voltages v_1 , v_2 and the current i in the following circuit.



$$v_1 = \underline{8/5V}$$

$$v_2 = \underline{2/5V}$$


$$i = \underline{3/5A}$$

1st node: $\frac{v_1}{2} + \frac{v_1 - v_2}{2} + \frac{v_1 - 2 - v_2}{2} = 1 \rightarrow \frac{3v_1}{2} - v_2 = 2$

2nd node: $\frac{v_2}{2} + \frac{v_2 - v_1}{2} + \frac{v_2 - (v_1 - 2)}{2} = 0 \rightarrow \frac{3v_2}{2} - v_1 = -1$

$$i = \frac{v_1 - v_2}{2} = \frac{8/5 - 2/5}{2} = \frac{6/5}{2} = 3/5A$$

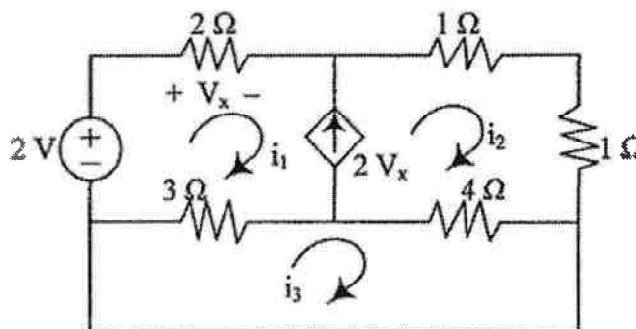4. (15 points) For the following circuit:



(a) (2 pts) What is V_x in terms of loop current i_1 ?

via Ohm's Law: $V_x = 2i_1$

$$V_x = 2i_1$$

(b) (3 pts) What is loop current i_2 in terms of loop current i_1 ?

via part (a)


$$2V_x = i_2 - i_1$$

$$= 2(2i_1)$$

$$\Rightarrow i_2 = 4i_1 + i_1 = 5i_1$$

$$i_2 = 5i_1$$

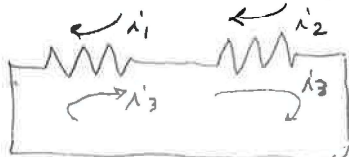
(c) (5 pts) Write the KVL equation for loop 3 in terms of i_1 , i_2 and i_3 .



equation: $3(i_3 - i_1) + 4(i_3 - i_2) = 0$

(d) (5 pts) Write one additional KVL equation for the circuit in terms of i_1 , i_2 and i_3 , which makes it possible to solve for these three variables. You are not required to solve the system.

superloop
spanning
current
source:

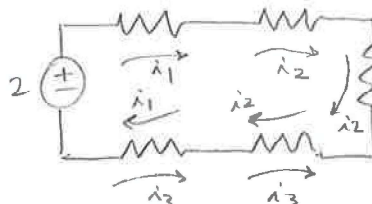


$$2 = 2i_1 + i_2 + i_2 + 4(i_2 - i_3) + 3(i_1 - i_3)$$

$$2 = 5i_1 + 6i_2 - 7i_3$$

- or -


outer
current
loop:

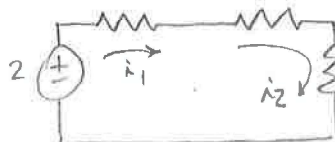

$$2 = 2i_1 + 2i_2$$

equation: $2 = 5i_1 + 6i_2 - 7i_3$ - or - $2 = 2i_1 + 2i_2$

(a) (10pt) Find v_1 , v_2 , v_3 .

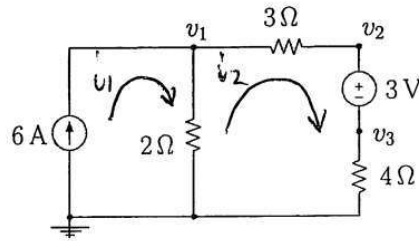

Loop method

① $i_1 = 6$

② $2(i_2 - i_1) + 3i_2 + 3 + 4i_2 = 0$ (in terms of voltage drops)

$i_2(2+3+4) = 2i_1 - 3 = 12 - 3 = 9$

$i_2 = \frac{9}{9} = 1$

So

$v_3 = 4i_2 = 4$

$v_2 = v_3 + 3 = 7$

$v_1 = v_2 + 3i_2 = 7 + 3 = 10$


Node method

① v_1 : $6 = \frac{v_1}{2} + \frac{v_1 - v_2}{3} : 5v_1 - 2v_2 = 36$

② v_2 : $\frac{v_1 - v_2}{3} = \frac{v_3}{4} : 4v_1 - 7v_2 = -9$

③ v_3 : $v_3 = v_2 - 3$

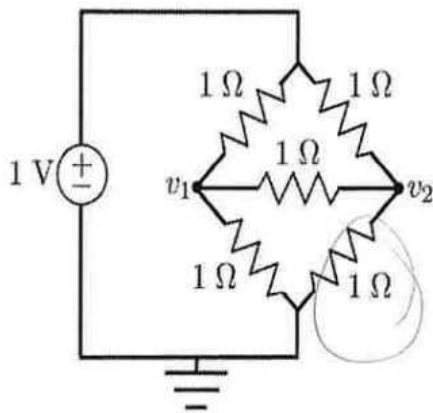3. (10 pts) Write, but do not solve, two node equations in order to solve for v_1 and v_2 . Fill in your final answer in the space provided, but be sure to show your work.




Answer:

$$(\underline{3})v_1 + (\underline{-1})v_2 = (\underline{1})$$

$$(\underline{-1})v_1 + (\underline{3})v_2 = (\underline{1})$$

@ v_1 :

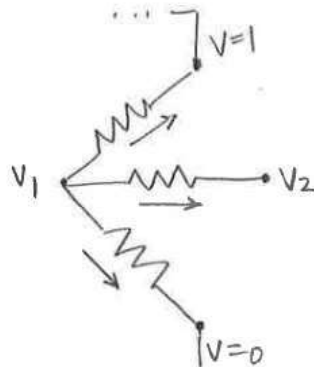


$$\frac{(v_1 - 1)}{1} + \frac{(v_1 - v_2)}{1} + \frac{(v_1 - 0)}{1} = 0$$

$$\text{so } v_1 - 1 + v_1 - v_2 + v_1 = 0$$

$$\Rightarrow 3v_1 - v_2 = 1$$

@ v_2 :

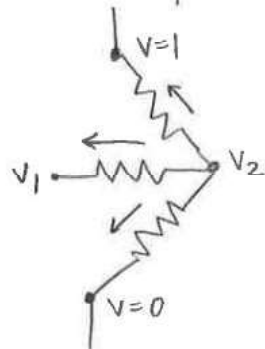


$$\frac{(v_2 - 1)}{1} + \frac{(v_2 - v_1)}{1} + \frac{(v_2 - 0)}{1} = 0$$

$$\text{so } v_2 - 1 + v_2 - v_1 + v_2 = 0$$

$$\Rightarrow 3v_2 - v_1 = 1$$

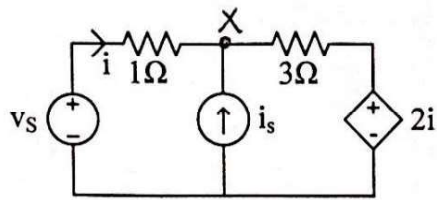(a) The current i in the following circuit can be expressed as $i = K_1 v_s + K_2 i_s$. Find the values of K_1 and K_2 if $v_s = 12V$, $i_s = 6A$.



$$\text{KCL: } x - \frac{2i}{3} - i_s + x - v_s = 0 \rightarrow$$

$$v_s - x = i \rightarrow v_s - i = x$$

$$v_s - \frac{2i}{3} - i_s + v_s - i - v_s = 0$$

$$K_1 = \underline{\underline{1/6}}$$

$$\frac{v_s}{3} - i - i_s - i = 0$$



$$\frac{v_s}{3} - i_s = 2i \rightarrow i = \underline{\underline{\frac{1}{6} v_s - \frac{1}{2} i_s}}$$

$$K_2 = \underline{\underline{-\frac{1}{2}}}$$

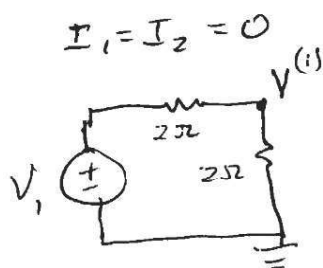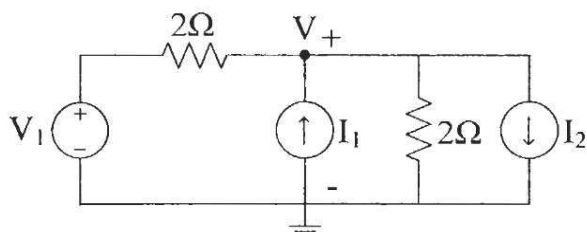(a) In the following circuit, using the principle of linearity and superposition, we can write the node voltage V as


$$V = AV_1 + BI_1 + CI_2$$

Use source suppression to find the constants A , B , and C .




$$V^{(1)} = V_1 / 2$$

so $A = 1/2$

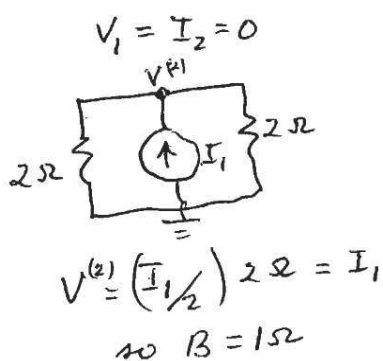

$$V^{(2)} = (I_1 / 2) \cdot 2\Omega = I_1$$

so $B = 1\Omega$

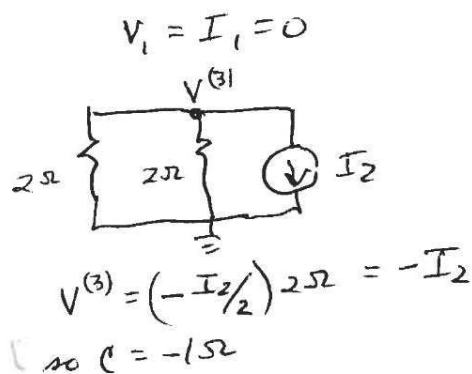

$$V^{(3)} = (-I_2 / 2) \cdot 2\Omega = -I_2$$

so $C = -1\Omega$

$$A = \underline{1/2}$$

$$B = \underline{1\Omega}$$

$$C = \underline{-1\Omega}$$

(a) Use the loop method to find the current i_s . Assume that


(10) v_s , R_i , R_f , and g_m are known.

$$\text{KVL: } -v_s + R_i i_s + R_f (i_s + g_m R_i i_s) = 0$$

$$v_s = (R_i + R_f + g_m R_i R_f) i_s$$


$$i_s = \frac{v_s}{R_i + R_f + g_m R_i R_f}$$

Note: equivalent input resistance

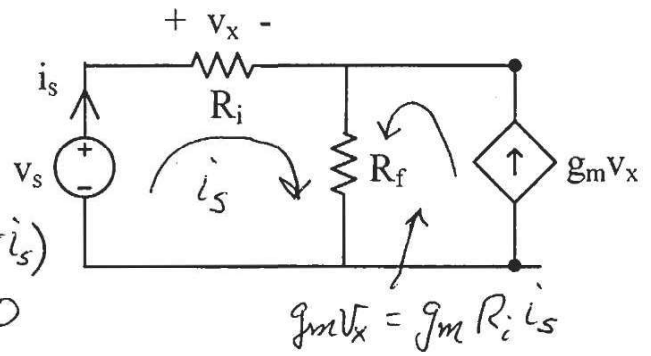

(15)

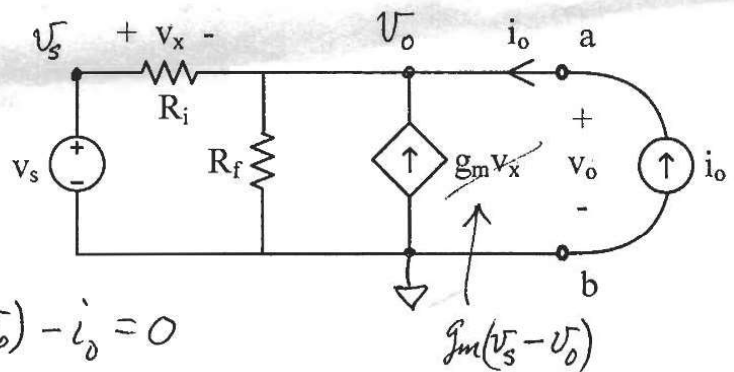- (b) Use the node method to find v_o as a function of the independent sources v_s and i_o . At terminals a-b what is the equivalent resistance and the open circuit voltage.



$$\frac{v_o - v_s}{R_i} + \frac{v_o}{R_f} - g_m(v_s - v_o) - i_o = 0$$

becomes

$$\left(\frac{1}{R_i} + \frac{1}{R_f} + g_m \right) v_o = i_o + \frac{v_s}{R_i} + g_m v_s$$

$$v_o = \underbrace{\frac{1}{\frac{1}{R_i} + \frac{1}{R_f} + g_m}}_{R_T} \cdot i_o + \underbrace{\left(\frac{1 + g_m R_i}{1 + \frac{R_i}{R_f} + g_m R_i} \right)}_{V_T} v_s$$

