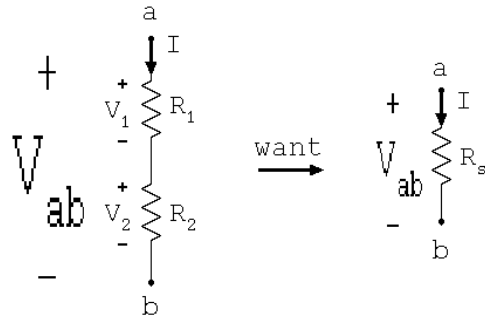


Lecture 4, Monday, January 24, 2022

- Circuit analysis

- Resistors in series and voltage division



- * $R_s = R_1 + R_2$


- If n resistors in series: $R_s = R_1 + R_2 + \dots + R_n$

- * $V_{R_i} = \frac{R_i}{R_s} V_{ab}$

- Voltage in each resistor is proportional to own resistance

- The larger the resistance, the larger portion of V_{ab} it gets

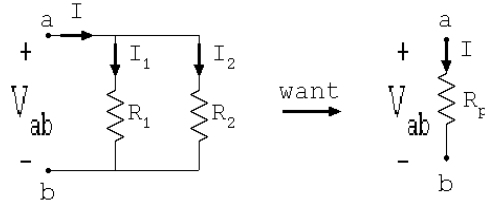- Resistors in parallel and current division



- * $R_p = \frac{R_1 R_2}{R_1 + R_2}$

- If n resistors in parallel: $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$

- * $I_{R_i} = \frac{R_p}{R_i} I$



- Current in resistor is inversely proportional to own resistance

- The smaller the resistance, the larger portion of I it gets

continued on next page....


Lecture 4, continued from previous page...

– Source combinations

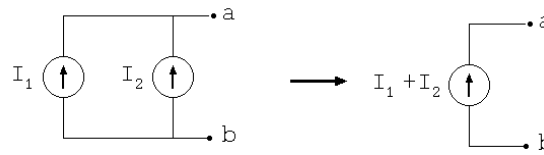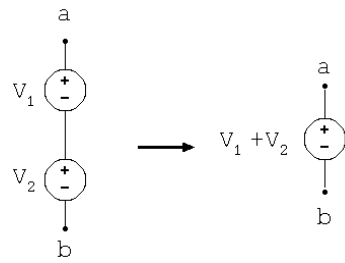

- * Voltage sources in series
add/subtract
- * Current sources in parallel
add/subtract

• Source transformations

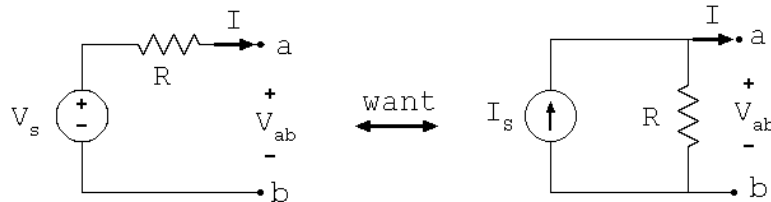

- * $V_s = RI_s$
- * Pay attention to series/parallel
- * Avoid transforming parts of circuit where:
 - * dependency exists
 - * we are solving for.