

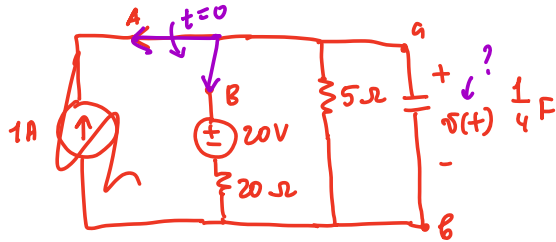


Extra example:

05/03/2022

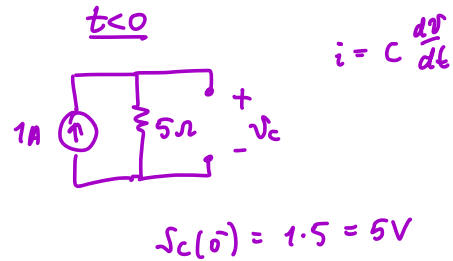

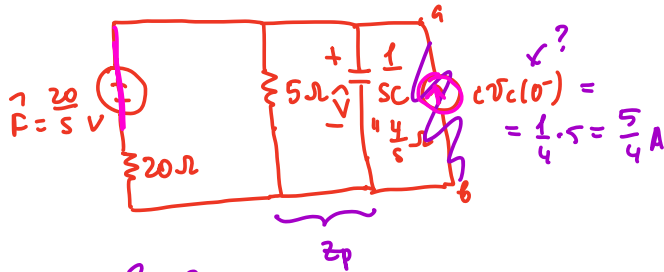a) Draw eq. circuit in s-domain for  $t > 0$



b)  $\hat{V} = ?$

Superposition:

$$\text{only } F = \frac{20}{s} V \Rightarrow \hat{V}_{zs} = F \left( \frac{Z_p}{Z_p + 20} \right) = \frac{4}{s(1+s)}$$

$$\text{only } \frac{5}{4} A : \Rightarrow \hat{V}_{zI} = \frac{5}{4} A \cdot Z_p = \frac{5}{1+s}$$

$$\frac{1}{Z_p} = \frac{1}{20} + \frac{2}{4} + \frac{1}{5}$$

$$\hat{V} = \frac{4}{s(1+s)} + \frac{5}{1+s} = \frac{4+5s}{s(1+s)}$$

c)  $v(t)$ ,  $t > 0$

$$\hat{V} = \frac{4+5s}{s(1+s)} = \frac{A_1}{s} + \frac{A_2}{1+s} = \frac{4}{s} + \frac{1}{1+s}$$

$\downarrow \mathcal{L}^{-1}$

$$v(t) = 4u(t) + e^{-t}u(t) \quad V$$

d) Plot  $v(t)$  for  $t > -1s$

