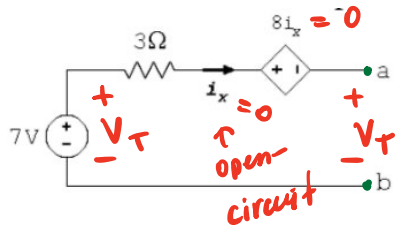


- **Example #13:** Obtain the available power,  $P_a$  for the following circuit




$$P_a = \frac{V_T^2}{4R_T} = \frac{7^2}{4 \cdot 11} = \frac{49}{44} \text{ W}$$

$$V_T = 7V$$

↑ only get this much  
if  $R_L = R_T = 11\Omega$   
↑ matched load

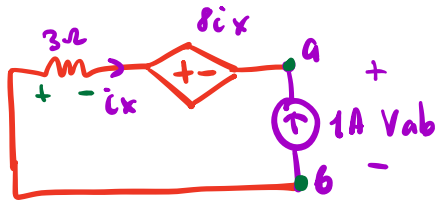For  $R_T$ , let's do  
test signal method:



$$\text{KVL: } +3i_x + 8i_x + V_{ab} = 0$$

$$V_{ab} = -11i_x = 11V \Rightarrow R_T = 11\Omega$$

## Summary

- Series and parallel resistor configurations
- Voltage and current division
- Sources transformations
- Node-voltage method
  - Supernode
- Loop current method
  - Superloop
- Linearity and superposition
- Thevenin and Norton equivalent circuits
  - Test signal method
- Available power