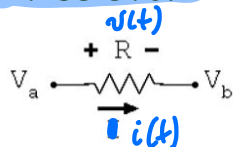


• V-I relationships in phasors

• Resistor



$$v(t) = R \cdot i(t)$$


↓ phasors

$$\boxed{V = R \cdot I} \quad \text{Ohm's law}$$

$$|V|e^{j\theta_v} = R \cdot |I|e^{j\theta_i}$$

V and I are in-phase
(V and I have the same angle)

• Inductor

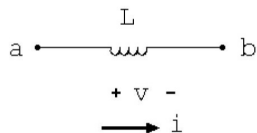


$$v(t) = L \frac{di}{dt}$$

↓ phasors

$$V = Lj\omega I = (j\omega L) I = V$$

$$\boxed{V = Z \cdot I}$$


$$|V|e^{j\theta_v} = \omega L |I|e^{j\theta_i} \cdot e^{j\pi/2}$$

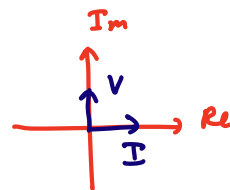

voltage leads
(ahead of) current by $\pi/2$

or
current lags
(behind) voltage¹¹
by $\pi/2$

• Capacitor

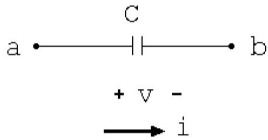

$$i = C \frac{dv}{dt}$$

↓ phasors


$$I = C j\omega V \Rightarrow \underbrace{\frac{1}{j\omega C}} I = V$$

$$Z = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$\boxed{V = Z I}$$

$$|V| e^{j\theta_V} = \frac{1}{\omega C} |I| e^{j\theta_I} \cdot e^{-j\pi/2}$$

$$\frac{1}{j} = -j$$

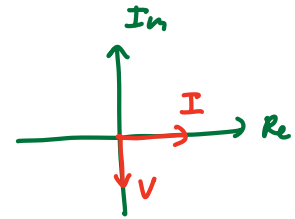

Voltage lags current by $\pi/2$

or
current leads voltage
by $\pi/2$

- V-I relationships in phasors - cont.

$$\text{Impedance, } Z = \begin{cases} R \\ j\omega L = X_L \\ \frac{1}{j\omega C} = \frac{-j}{\omega C} = -X_C \end{cases}$$

resistor ← purely resistive
inductor } purely reactive
capacitor }


"X_C"

More generally:

$$Z = \underbrace{\text{Re}\{Z\}}_{\text{resistance}} + \underbrace{\text{Im}\{Z\}}_{\text{reactance}} = R + jX$$

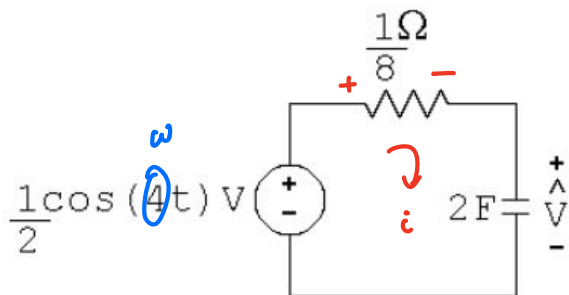• Example #4

- Determine $\widehat{v}_{ss}(t)$ using phasors:



$$\frac{d\vec{v}}{dt} \rightarrow j\omega \hat{v}$$

$$\vec{v}_{ss}(t) = \frac{1}{2\sqrt{2}} \cos(4t - \pi/4) \text{ V}$$

$$KVL: -\frac{1}{2} \cos(4t) + \frac{1}{8} \cdot i + \vec{v} = 0 \quad \leftarrow i_c = C \frac{d\vec{v}}{dt}$$

$$-\frac{1}{2} \cos(4t) + \frac{1}{8} \left(C \frac{d\vec{v}}{dt} \right) + \vec{v} = 0$$

$$-\frac{1}{2} \cos(4t) + \frac{1}{4} \frac{d\vec{v}}{dt} + \vec{v} = 0$$

↓ phasors

$$\frac{1}{2} \cos(4t + \pi)$$

$$\frac{1}{2} e^{j\pi} = -\frac{1}{2}$$

$$-\frac{1}{2} + \frac{1}{4} j\omega \hat{v} + \hat{v} = 0$$

$$-\frac{1}{2} + j\hat{v} + \hat{v} = 0$$

$$\hat{v} = \frac{1/2}{1+j} = \frac{1/2 e^{j0}}{\sqrt{1^2+1^2} e^{j\pi/4}} =$$

time



$$= \frac{1}{2\sqrt{2}} e^{-j\pi/4} \text{ V}$$