

## Lecture 14, Wednesday, February 9, 2022

- First order ODE with constant coefficients and constant input:

- Solution for  $t > 0$ :

$$y(t) = \underbrace{\frac{K}{a}}_{= y_p(t)} + \underbrace{\left(y(0^+) - \frac{K}{a}\right) e^{-at}}_{= y_h(t)}$$

- $y_p(t)$  is the particular solution, specific to constant inputs

- $y_h(t)$  is the homogeneous solution

- \* satisfies the ODE = 0


- \* is needed to match the initial state of the output

- solution increases/decreases exponentially from  $y(0^+)$  to  $\frac{K}{a}$

- For the RC circuit,  $K = \frac{V_s}{RC}$ ,  $a = \frac{1}{RC}$  and  $y(0^+) = v_c(0^+) = v_c(0) = v_c(0^-)$

$$v_c(t) = V_s + (v_c(0^-) - V_s) e^{-\frac{t}{RC}}$$

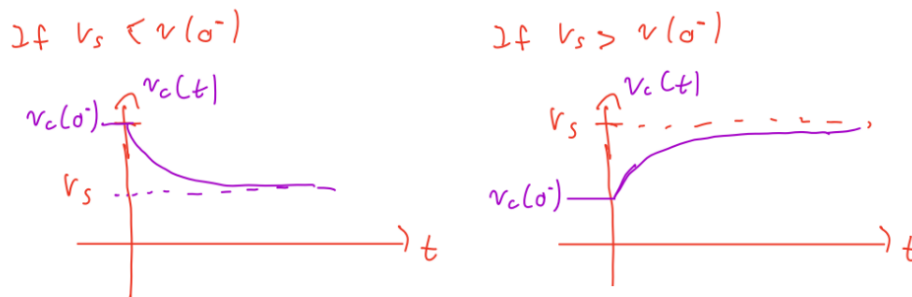- solution increases/decreases exponentially from  $v_c(0^-)$  to  $V_s$



continued on next page....

## Lecture 14, continued from previous page...

- $RC = \tau$  is called the time-constant
- The larger the value of  $\tau$ , the slower the exponential term decays
- A simple way to solve for  $v_c(t)$  for  $t > 0$  is to consider

$$* v_c(t) = B + Ae^{-\frac{t}{\tau}}$$

$$* v_c(\infty) = V_T = B$$

$$* v_c(0^+) = v_c(0^-) = B + A$$

$$* \tau = R_TC$$

- In a general first order ODE with constant coefficients and constant input

$$y(t) = y_{ZS}(t) + y_{ZI}(t) = \underbrace{\frac{K}{a} (1 - e^{-at})}_{= y_{ZS}} + \underbrace{y(0^+) e^{-at}}_{= y_{ZI}}$$

- Therefore, the system is linear